

## Review Questions

### Q1. [Rizzoni Problem 2.13]

Use KCL to determine the unknown currents in the following circuit given that  $I_0 = -2\text{A}$ ,  $I_1 = -4\text{A}$ ,  $I_S = 8\text{A}$  and  $V_S = 12\text{V}$ .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

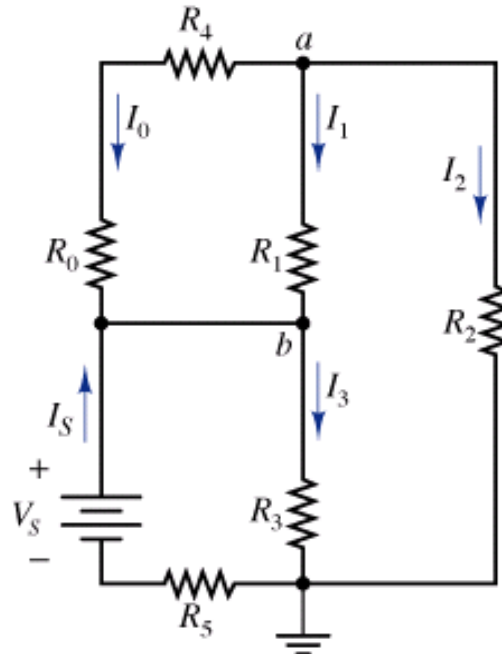


Figure P2.13

### Q2. [Rizzoni Problem 2.24]

Apply KVL to Figure P2.24 to find the power dissipated or supplied for each element. Hence determine the amount of power dissipated and supplied overall.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

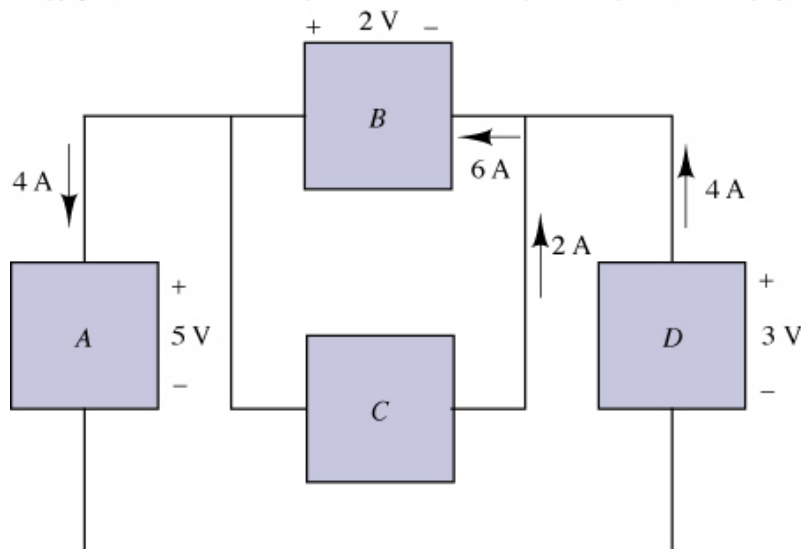


Figure P2.24

**Q3. [Alexander Problem 2.12]**

With reference to the circuit in Fig 2.76, find  $v_1$ ,  $v_2$ , and  $v_3$  by applying KVL.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

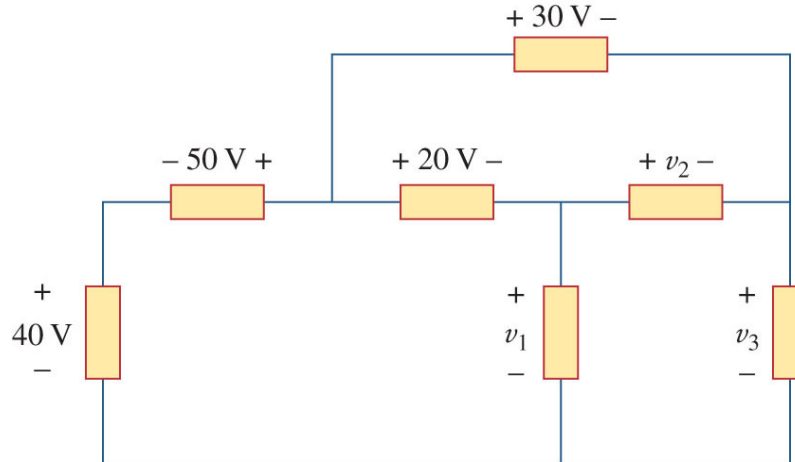


Figure 2.76

**Q4. [Rizzoni Problem 2.21]**

In the circuit of Figure P2.21, determine the power absorbed by the resistor  $R$  and the power delivered by the current source.

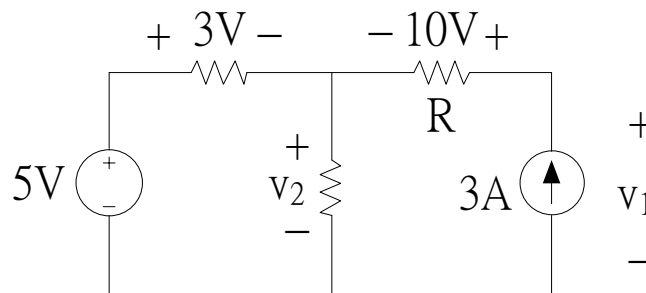


Figure P2.21

**Q5. [Modified from Rizzoni Problem 2.49]**

For the circuit shown in Figure P2.49, find the equivalent resistance across the terminals. Let  $R_1 = 5\ \Omega$ ,  $R_2 = 6\ \Omega$ ,  $R_3 = 4\ \Omega$ ,  $R_4 = 10\ \Omega$ ,  $R_5 = 7\ \Omega$  and  $R_6 = 10\ \Omega$ .

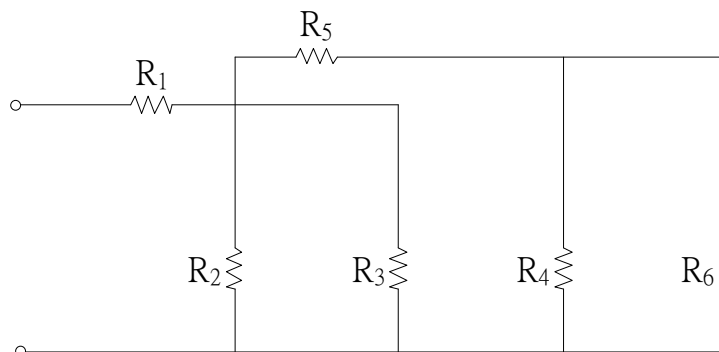


Figure P2.49

**Intermediate Level****Q6. [Rizzoni Problem 2.47]**

Find the equivalent resistance between terminals  $a$ - $b$  in the circuit of Figure P2.47.

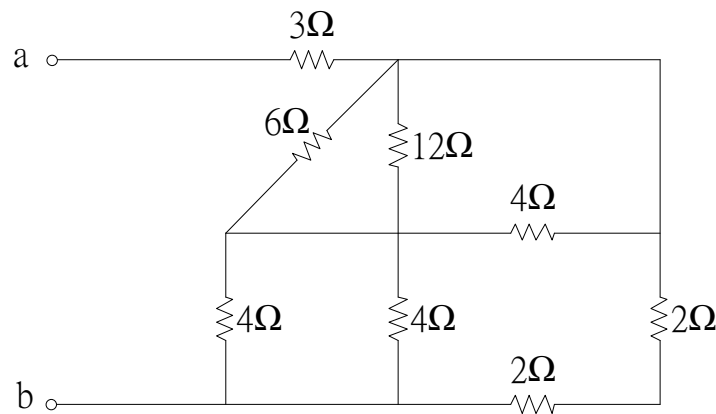


Figure P2.47

**Q7. [Rizzoni Problem 2.64]**

In the circuit of Figure P2.64, find the equivalent resistance:

- Across  $a$ - $b$  when (i) terminals  $c$ - $d$  are open and (ii) when terminals  $c$ - $d$  are shorted together.
- Across  $c$ - $d$  when (i) terminals  $a$ - $b$  are open and (ii) when terminals  $a$ - $b$  are shorted together.

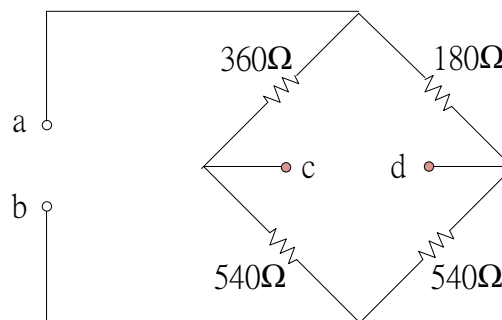


Figure P2.64

**Q8. [Alexander Problem 2.18]**

Apply KVL and Ohm's law to find  $I$  and  $V_{ab}$  in the circuit of Fig 2.82.

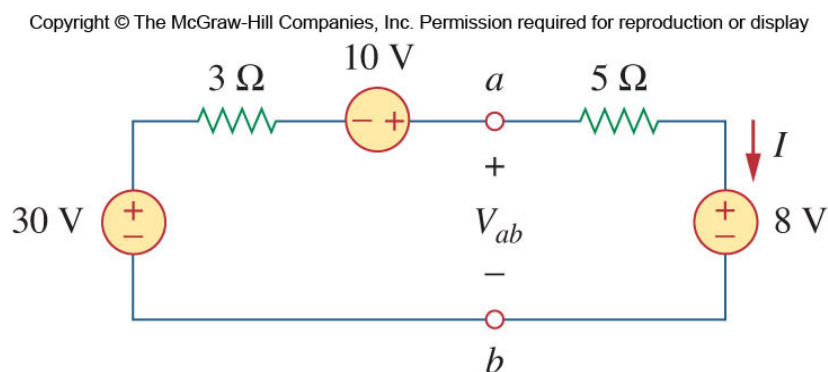


Figure 2.82

**Q9. [Rizzoni Problem 2.46]**

In the circuit shown in Figure P2.46, the power absorbed by the  $15\Omega$  resistor is  $15\text{W}$ . Find  $R$ . (Hint: Find the voltage across the  $15\Omega$  resistor. Then find the equivalent resistance across the terminals of  $15\Omega$ . If we denote this resistance by  $R_{eq}$ , next use voltage divider rule with  $R$  and  $R_{eq}$  in series).

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

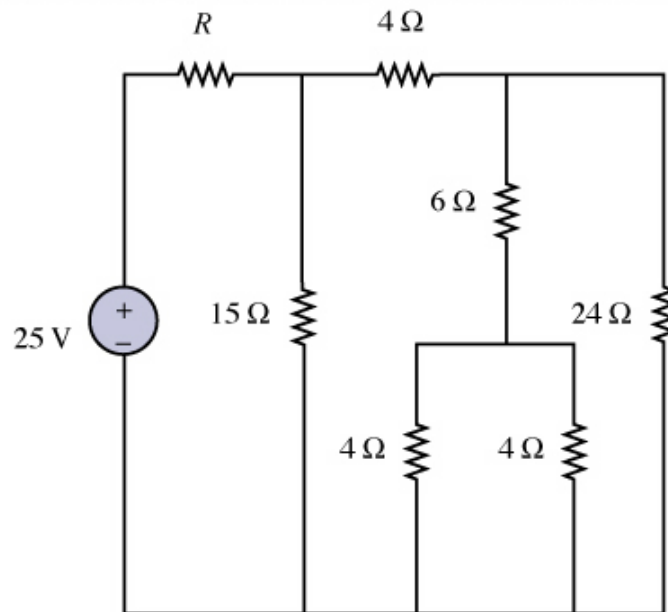


Figure P2.46

**Numerical solutions****Q1. [Rizzoni Problem 2.13]**

$$I_2 = 6\text{ A}, I_3 = 2\text{ A}$$

**Q2. [Rizzoni Problem 2.24]**

$$A = 20\text{ W (dissipating)}, B = 12\text{ W (generating)}, C = 4\text{ W (dissipating)}, D = 12\text{ W (generating)}$$

**Q3. [Alexander Problem 2.12]**

$$\text{Unknown voltage differences: } v_1 = 70\text{ V}, v_2 = 10\text{ V}, v_3 = 60\text{ V}$$

**Q4. [Rizzoni Problem 2.21]**

$$\text{Power consumed by resistor R: } 30\text{ W}$$

$$\text{Power supplied by current source: } 36\text{ W}$$

$$\text{Hint: You would need to find } V_1 \text{ and } V_2 \text{ first by applying KVL around any mesh or loop (} V_1 = 12\text{ V, } V_2 = 2\text{ V)}$$

**Q5. [Modified from Rizzoni Problem 2.49]**

$$7\ \Omega$$

**Q6. [Rizzoni Problem 2.47]**

$$5\ \Omega$$

**Q7. [Rizzoni Problem 2.64]**

$$\text{Part (a)(i) } 400\ \Omega$$

$$\text{Part (a)(ii) } 390\ \Omega$$

$$\text{Part (b)(i) } 360\ \Omega$$

$$\text{Part (b)(ii) } 351\ \Omega$$

**Q8. [Rizzoni Alexander Problem 2.18]**

$$I = 4\text{ A}$$

$$V_{ab} = 28\text{ V}$$

**Q9. [Rizzoni Problem 2.46]**

$$R = 4\ \Omega$$