

# Content

---

Alexander & Sadiku,  
“Fundamentals of Electric Circuits”  
7<sup>th</sup> Edition Chapters 9 &10

## 1) Analysis with single source

- Methodology [Section 10.1]
- Two examples

## 2) Analysis with multiple sources (single frequency)

- Nodal analysis [Section 10.2] (1 example)
- Mesh analysis [Section 10.3] (1 example)

## 3) Analysis by superposition (multiple frequencies)

- Circuits containing DC sources and AC sources of a single frequency (1 example)
- Circuits containing multiple AC sources with different frequencies (1 example)

## 4) AC Power: Instantaneous vs. Average

# General methodology

- 1) Transform the circuit to the frequency domain
  - Transform AC sources from time domain sinusoids to phasor form
  - Work out impedances for a given frequency  $\omega$
- 2) Solve the problem using circuit techniques
- 3) Transform phasor form solutions back to time domain

$$v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow V = V_m \angle \phi$$

(Time-domain representation)                      (Phasor-domain representation)

**TABLE 9.3**


Impedances and admittances of passive elements.

Element	Impedance	Admittance
$R$	$Z = R$	$Y = \frac{1}{R}$
$L$	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
$C$	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

# 1A) Single source analysis example 1
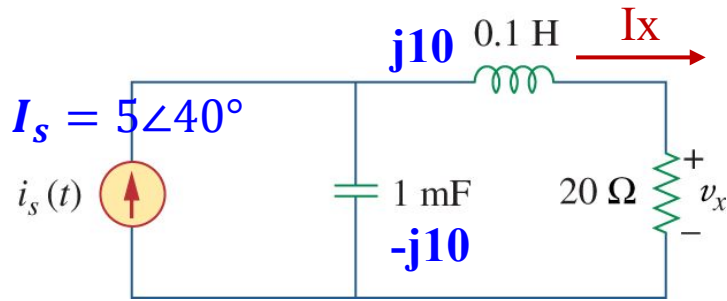
## Alexander 9.50

Given that  $i_s(t) = 5 \cos(100t + 40^\circ)$ , determine  $v_x(t)$



**Step 1a: Transform source to phasor**

$$i_s(t) = 5 \cos(100t + 40^\circ) \rightarrow I_s = 5 \angle 40^\circ, \omega = 100 \frac{\text{rad}}{\text{s}}$$

**Step 1b: Work out the impedance values**

$$1 \text{ mF} \rightarrow -j/(100 * 0.001) = -j10$$

$$0.1 \text{ H} \rightarrow j100 * 0.1 = j10$$

**Step 2: Solve using circuit analysis methods**

Using current divider rule,

$$I_x = \left( \frac{-j10}{-j10 + j10 + 20} \right) (5 \angle 40^\circ) = (-j0.5)(5 \angle 40^\circ) = 2.5 \angle -50^\circ$$

$$V_x = 20 I_x = 50 \angle -50^\circ$$


**Step 3: Transform back to time domain**

$$V_x = 50 \angle -50^\circ, \omega = 100 \frac{\text{rad}}{\text{s}} \rightarrow v_x(t) = 50 \cos(100t - 50^\circ) \text{ V}$$

# 1B) Single source analysis example 2

## Alexander 9.42

Determine  $v_o(t)$

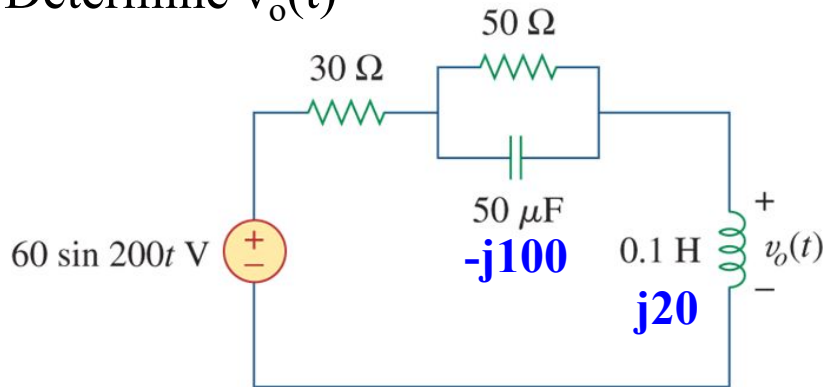

**Step 1a: Transform source to phasor**

$$60 \sin(200t) \rightarrow 60 \angle -90^\circ, \omega = 200 \frac{\text{rad}}{\text{s}}$$

$$60 \cos(200t - 90^\circ)$$

**Step 1b: Work out the impedance values**

$$50 \mu\text{F} \rightarrow -j/(200 * 50 * 10^{-6}) = -j100$$

$$0.1 \text{ H} \rightarrow j200 * 0.1 = j20$$

**Step 2: Solve using circuit analysis methods**

$$50 \parallel -j100 = \frac{(50)(-j100)}{(50 - j100)} = 40 - j20$$

Using voltage divider role,

$$V_o = \left( \frac{j20}{40 - j20 + 30 + j20} \right) (60 \angle -90^\circ) = 17.14 \angle 0^\circ$$

**Step 3: Transform back to time domain**


$$V_o = 17.14 \angle 0^\circ, \omega = 200 \frac{\text{rad}}{\text{s}} \rightarrow v_x(t) = 17.14 \cos(200t) \text{ V}$$

# 2A) Single freq multiple sources example 1

Focus only on STEP 2 (solving by circuit techniques) in this example

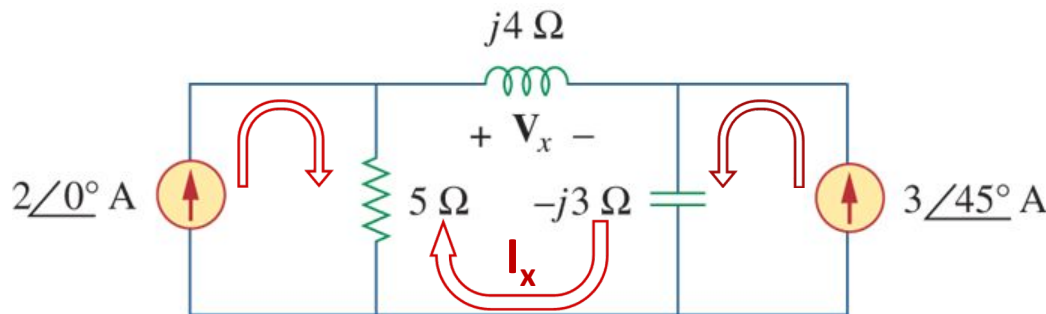**Alexander 10.16**

Use **MESH CURRENT ANALYSIS** to find  $V_x$



Applying KVL around mesh  $I_x$ :

$$I_x(j4 - j3 + 5) - (2\angle 0^\circ)(5) + (3\angle 45^\circ)(-j3) = 0$$


$$\Rightarrow I_x = 1.437\angle 48.94^\circ \text{ A}$$

$$V_x = (1.437\angle 48.94^\circ)(j4) = 5.749\angle 138.94^\circ \text{ V}$$

# 2B) Single freq multiple sources example 2
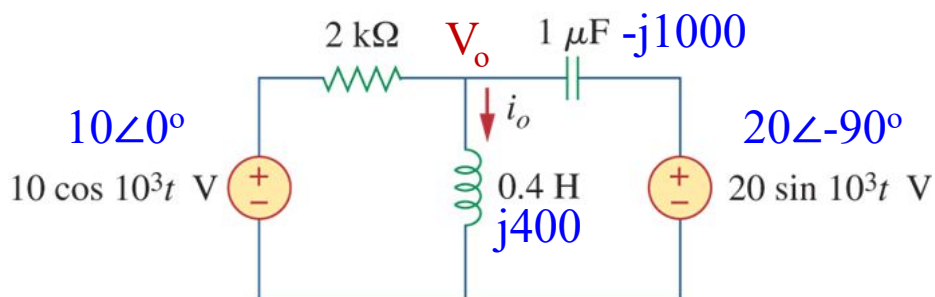
## Alexander 10.26

Use nodal voltage analysis to find  $i_o(t)$



### Step 1a: Transform source to phasor

$$10 \cos(10^3 t) \rightarrow 10 \angle 0^\circ, \omega = 10^3 \text{ rad/s}$$

$$20 \sin(10^3 t) \rightarrow 20 \angle -90^\circ, \omega = 10^3 \text{ rad/s}$$

### Step 1b: Work out the impedance values

$$1 \mu\text{F} \rightarrow -j/(10^3 * 10^{-6}) = -j1000$$

$$0.4 \text{ H} \rightarrow j10^3 * 0.4 = j400$$

### Step 2: Solve using circuit analysis methods

Applying KCL at node  $V_o$ :

$$\frac{(10 \angle 0^\circ) - V_o}{2000} + \frac{(20 \angle -90^\circ) - V_o}{-j1000} = \frac{V_o}{j400}$$

$$\Rightarrow V_o = 15.8 \angle 71.57^\circ \text{ V}$$

$$I_o = (15.8 \angle 71.57^\circ) / j400 = 39.5 \angle -18.43^\circ \text{ mA}$$


### Step 3: Transform back to time domain

$$I_o = 39.5 \angle -18.43^\circ \text{ mA}, \omega = 10^3 \text{ rad/s} \rightarrow i_o(t) = 39.5 \cos(10^3 t - 18.43^\circ) \text{ mA}$$

# 3A) Superposition (multiple freq) example 1
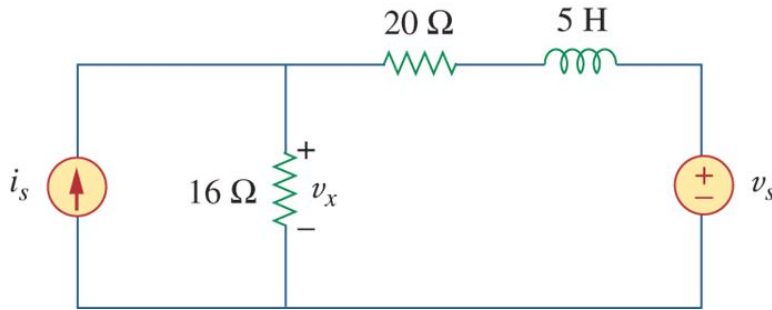
## Alexander 10.44 (Modified)

Given  $v_s(t) = 50\cos(2t)$  and  $i_s = 0.9$  A, find  $v_x(t)$




**Method: Analyze circuit one frequency at a time**

In the case, first analyze at DC then at 2 rad/s and then add up the two solutions (**superposition**)

**At DC, redraw circuit without  $v_s(t)$ :**

Replace voltage source with short circuit

Replace inductor with short circuit

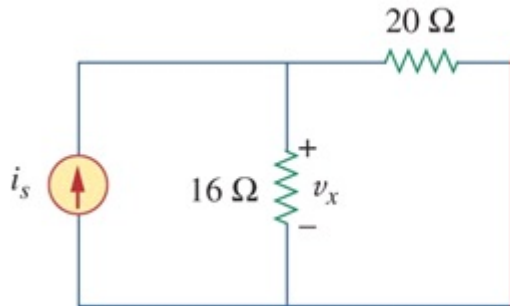


Resistance across current source =  $20 \parallel 16 = 80/9\ \Omega$

$V_x = 0.9 * 80/9 = 8\text{ V}$  (DC)


# 3A) Superposition (multiple freq) example 1
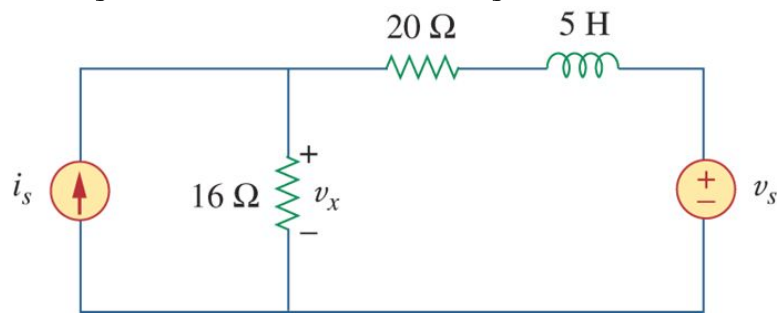
## Alexander 10.44 (Modified)

Given  $v_s(t) = 50\cos(2t)$  and  $i_s = 0.9$  A, find  $v_x(t)$



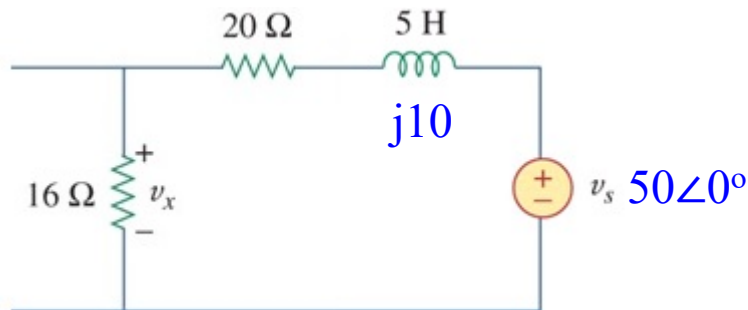At **2 rad/s**, redraw circuit without  $i_s$ :  
Replace current source with open circuit



**Final step: Add up both solutions**  
 $v_x(t) = 21.41\cos(2t - 15.52^\circ) + 8\text{ V}$

**Step 1a: Transform source to phasor**

$50\cos(2t) \rightarrow 50\angle 0^\circ$ ,  $\omega = 2\text{ rad/s}$

**Step 1b: Work out the impedance values**

$5\text{ H} \rightarrow j2 \cdot 5 = j10$

**Step 2: Solve using circuit analysis methods**

Using voltage divider rule,

$$V_x = \left( \frac{16}{16 + 20 + j10} \right) (50\angle 0^\circ) = 21.41\angle -15.52^\circ$$

**Step 3: Transform back to time domain**

$V_x = 21.41\angle -15.52^\circ$ ,  $\omega = 2\text{ rad/s}$

$\rightarrow v_x(t) = 21.41\cos(2t - 15.52^\circ)\text{ V}$

**(NEVER SKIP THIS STEP)**


Note that there are **2 terms** in the final form (one at DC and another at 2 rad/s)



# 3B) Superposition (multiple freq) example 2

Alexander 10.45


Find  $i(t)$

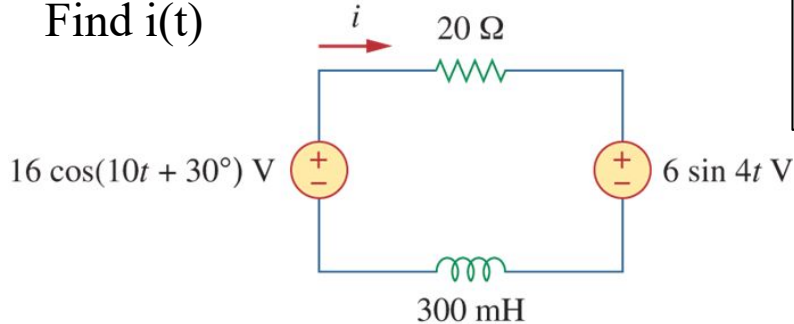

**Method: Analyze circuit one frequency at a time**  
In the case, first analyze at 4 rad/s then 10 rad/s.  
Finally, add up the two solutions (**superposition**)

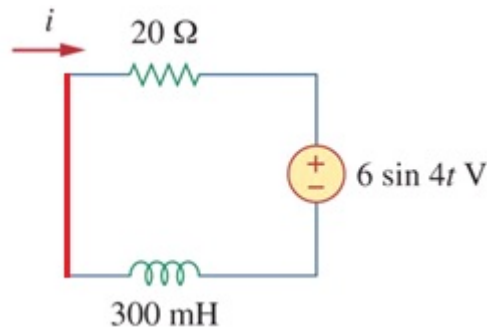**At 4 rad/s, redraw circuit without 10 rad/s source:**

Replace 10 rad/s voltage source with short circuit



**Step 1a: Transform source to phasor**

$6 \sin(4t) \rightarrow 6 \angle -90^\circ$ ,  $\omega = 4 \text{ rad/s}$

**Step 1b: Work out the impedance values**

$300 \text{ mH} \rightarrow j4 * 0.3 = j1.2$

**Step 2: Solve using circuit analysis methods**

$$\mathbf{I}^*(20 + j1.2) + 6 \angle -90^\circ = 0$$

$$\mathbf{I} = 0.2995 \angle 86.57^\circ \text{ A}$$

**Step 3: Transform back to time domain**

$$\mathbf{I} = 0.2995 \angle 86.57^\circ, \omega = 4 \text{ rad/s}$$


$$\rightarrow i(t) = 0.2995 \cos(4t + 86.57^\circ) \text{ A}$$

**NEVER SKIP THIS STEP**


# 3B) Superposition (multiple freq) example 2

Alexander 10.45

Find  $i(t)$

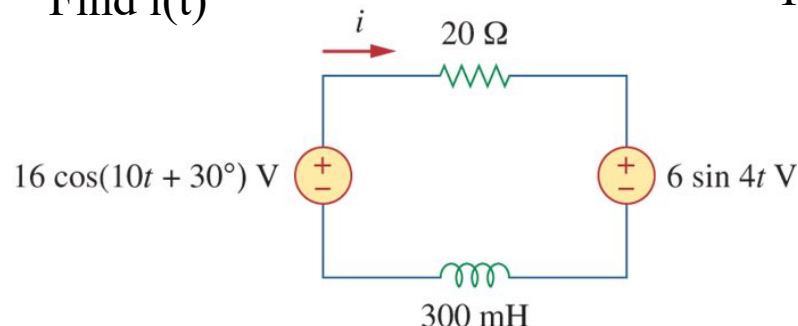

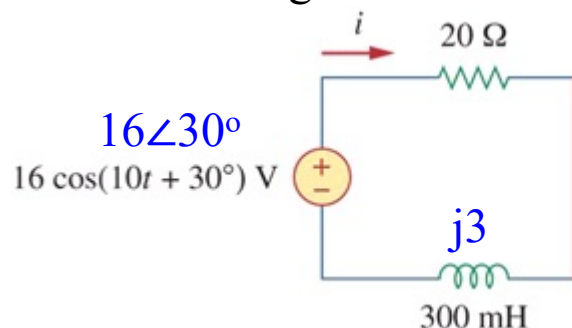At **10** rad/s, redraw circuit without 4 rad/s source:  
Replace 4 rad/s voltage source with short circuit



**Step 2: Solve using circuit analysis methods**

$$\mathbf{I}^*(20 + j3) = 16 \angle 30^\circ$$

$$\mathbf{I} = 0.7911 \angle 21.47^\circ \text{ A}$$

**Step 3: Transform back to time domain**

$$\mathbf{I} = 0.7911 \angle 21.47^\circ, \omega = 10 \text{ rad/s}$$

$$\rightarrow i(t) = 0.7911 \cos(10t + 21.47^\circ) \text{ A}$$

**Step 1a: Transform source to phasor**

$$16 \cos(10t + 30^\circ) \rightarrow 16 \angle 30^\circ, \omega = 10 \text{ rad/s}$$

**Step 1b: Work out the impedance values**

$$300 \text{ mH} \rightarrow j10 * 0.3 = j3$$

**NEVER SKIP THIS STEP**

**Final step: Add up both solutions**


$$i(t) = 0.2995 \cos(4t + 86.57^\circ) + 0.7911 \cos(10t + 21.47^\circ) \text{ A}$$

Note that there are 2 terms in the final form  
(one at 4 rad/s and another at 10 rad/s)
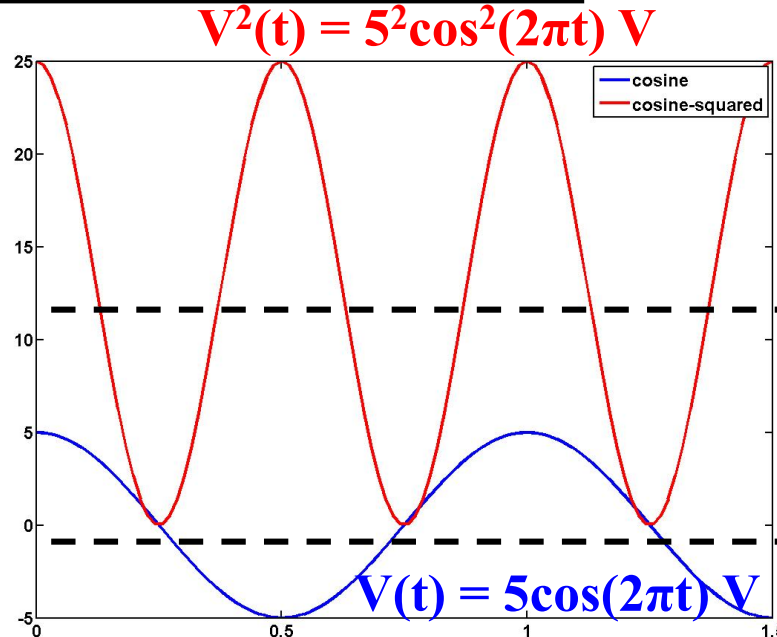
# AC Power: Instantaneous vs. Average

Although the average voltage across a resistor with a sinusoidal AC voltage across it is zero, note that the average power dissipated is not zero. Since  $P = V^2/R$ , we should consider the square of the voltage.

The following graph shows the voltage across a  $1\Omega$  resistor in blue and the corresponding square of this voltage in red. The red curve therefore shows the **INSTANTANEOUS POWER**.



The instantaneous power is clearly sinusoidal with a DC offset:

$$\begin{aligned} V^2(t) &= 5^2 * 0.5 * (1 + \cos(4\pi t)) \\ &= V_{\text{peak}}^2 * 0.5 * \cos(4\pi t) + \\ &\quad V_{\text{peak}}^2 * 0.5 \\ &= 12.5\cos(4\pi t) + 12.5 \end{aligned}$$

Mean of  $V^2 = 12.5$  (DC offset)

**Average power of  $V^2(t)$  is 12.5 W**  
**Average power of  $V^2(t) = 0.5 * V_{\text{peak}}^2$**

Mean of  $V = 0$

# Effective or RMS Value

The average power absorbed by the resistor in the ac circuit of Fig. (a) is


$$P = \frac{1}{T} \int_0^T i^2 R \, dt = \frac{R}{T} \int_0^T i^2 \, dt$$

To find the dc effective current  $I_{\text{eff}}$  (Fig. (b)) that will transfer the same power to resistor  $R$  as the sinusoid  $i(t)$ :


$$P = I_{\text{eff}}^2 R$$

Equating these two expressions of  $P$  and solving for  $I_{\text{eff}}$ , we obtain
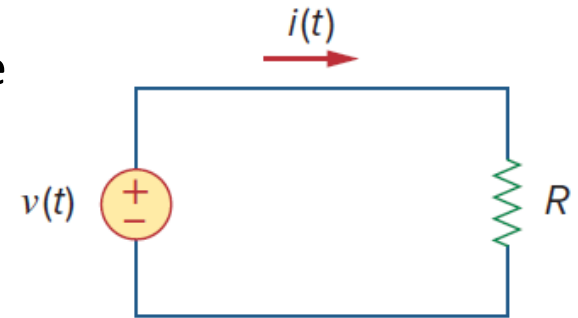
$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 \, dt}$$



(a)

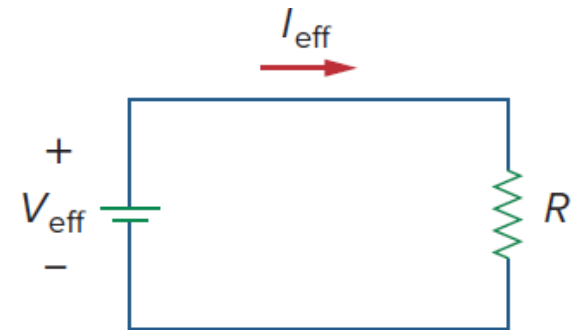

(b)

# Effective or RMS Value

---

The effective value of the voltage is found in the same way as current, i.e.,

$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

This indicates that the effective value is the square root of the mean (or average) of the square of the periodic signal. Therefore, the effective value is known as the root-mean-square (rms) value. We write

$$I_{\text{eff}} = I_{\text{rms}}, \quad V_{\text{eff}} = V_{\text{rms}}$$

For the sinusoid  $i(t) = I_m \cos \omega t$ , the effective or rms value is

$$\begin{aligned} I_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2 \omega t dt} \\ &= \sqrt{\frac{I_m^2}{T} \int_0^T \frac{1}{2} (1 + \cos 2\omega t) dt} = \frac{I_m}{\sqrt{2}} \end{aligned}$$

# Effective or RMS Value

---

Similarly, for  $v(t) = V_m \cos \omega t$ :

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

**Note:** The simple formulas for  $V_{\text{rms}}$  and  $I_{\text{rms}}$  are only valid for sinusoidal signals.

The average power absorbed by the resistor  $R$  in the previous simple circuit (Fig.(a) and (b)) can be written as

$$P = I_{\text{rms}}^2 R = \frac{V_{\text{rms}}^2}{R}$$