

**P.P.6.1**  $v = \frac{q}{C} = \frac{120 \times 10^{-6}}{4.5 \times 10^{-6}} = \mathbf{26.67 \text{ V}}$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} \times 4.5 \times 10^{-6} \times 711.1 = \mathbf{1.6 \text{ mJ}}.$$

**P.P.6.2**  $i(t) = C \frac{dv}{dt} = 10 \times 10^{-6} \frac{d}{dt} (75 \sin(2000t))$   
 $= \mathbf{1.5 \cos(2,000t) \text{ A}}.$

**P.P.6.3**  $v = \frac{1}{C} \int_0^t i dt = \frac{10^{-3}}{0.1 \times 10^{-3}} \int_0^t 50 \sin 120\pi t \, dt \text{ V}$   
 $= -\frac{500}{120\pi} \cos 120\pi t \Big|_0^t = \frac{50}{12\pi} (1 - \cos 120\pi t) \text{ V}$

$$v(t = 1\text{ms}) = \frac{50}{12\pi} (1 - \cos 0.12\pi) = \mathbf{93.14 \text{ mV}}$$

$$v(t = 5\text{ms}) = \frac{50}{12\pi} (1 - \cos 0.6\pi) = \mathbf{1.736 \text{ V}}$$

**P.P.6.4**  $i(t) = \begin{cases} 50t, & 0 < t < 2 \\ 100, & 2 < t < 6 \end{cases}$

$$v = \frac{1}{C} \int i dt = \frac{1}{10^{-3}} \int i dt \cdot 10^{-3} = \int i dt$$


For  $0 < t < 2$ ,  $v = \frac{1}{C} \int_0^t 50t \, dt = 25t^2 \times 10^3$

For  $2 < t < 6$ ,  $v = \frac{1}{C} \int_2^t 100 dt + v(2) = (100t - 0.2 + 0.1)$   
 $= (100t - 0.1) \text{ V}$

At  $t = 2\text{ms}$ ,  $v = \mathbf{100 \text{ mV}}$

At  $t = 5\text{ms}$ ,  $v = (500 - 100) \text{ mV}$   
 $= \mathbf{400 \text{ mV}}$

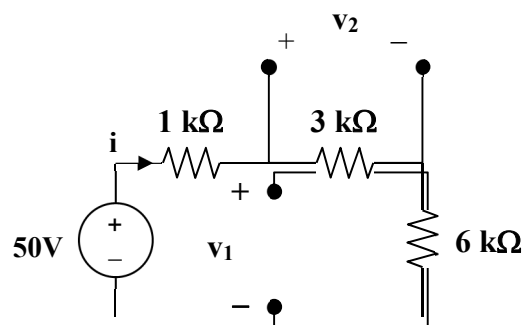**P.P.6.5** Under dc conditions, the capacitors act like open-circuits as shown below:



$$i = \frac{50}{1+3+6} = 5\text{mA}$$

$$v_1 = (3\text{k} + 6\text{k})i = 45\text{V}$$

$$v_2 = (3\text{k})i = 15\text{V}$$

$$w_1 = \frac{1}{2}C_1v_1^2 = \frac{1}{2}(20 \times 10^{-6})(45)^2 = \mathbf{20.25 \text{ mJ}}$$

$$w_2 = \frac{1}{2}C_2v_2^2 = \frac{1}{2}(30 \times 10^{-6})(15)^2 = \mathbf{3.375 \text{ mJ.}}$$

**P.P.6.6** Combining 60 and 120 $\mu\text{F}$  in series =  $\frac{60 \times 120}{180} = 40\mu\text{F}$

$$40\mu\text{F} \text{ in parallel with } 20\mu\text{F} = 40 + 20 = 60\mu\text{F}$$


$$50\mu\text{F} \text{ in parallel with } 70\mu\text{F} = 50 + 70 = 120\mu\text{F}$$

$$60\mu\text{F} \text{ in series with } 120\mu\text{F} = \frac{60 \times 120}{180} = \mathbf{40\mu\text{F}}$$

**P.P.6.7** Before we solve this, we need to assume that the initial charge on each capacitor is equal to zero.

$$60\mu\text{F} \text{ in series with } 30\mu\text{F} = \frac{60 \times 30}{90} = 20\mu\text{F}$$
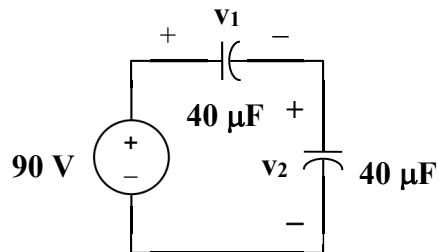
$$20\mu\text{F} \text{ in parallel with } 20\mu\text{F} = 40\mu\text{F}$$



From the Figure,  $v_1 = v_2 = 90/2 = \mathbf{45 \text{ V}}$ ;  $q_1 = 45 \times 40 \times 10^{-6} = 1.8 \text{ mC}$ ;  $q_2 = 45 \times 20 \times 10^{-6} = 0.9 \text{ mC} = q_3 = q_4$  leading to  $v_3 = 0.0009/(60 \times 10^{-6}) = \mathbf{15 \text{ V}}$  and  $v_4 = 0.0009/(30 \times 10^{-6}) = \mathbf{30 \text{ V}}$ .

**P.P.6.8** 
$$v = L \frac{di}{dt} = 10^{-3} \frac{d}{dt} (60 \cos(100t)) \cdot 10^{-3}$$
  

$$= \mathbf{-6 \sin(100t) \text{ mV}}$$

$$w = \frac{1}{2}Li^2 = \frac{1}{2} \times 10^{-3} (3600 \cos^2(100t)) \cdot 10^{-6}$$

$$= \mathbf{1.8 \cos^2(100t) \mu\text{J.}}$$

**P.P.6.9**  $i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0) = \frac{1}{2} \int_0^t 10(1-t) dt + 2$

$$= 5 \left( t - \frac{t^2}{2} \right) + 2$$


At  $t = 4$ ,  $i = 5(4 - 8) + 2 = \mathbf{-18 \text{ A}}$

$$p = vi = 10(1-t) \left[ 5t - \frac{5}{2}t^2 + 2 \right]$$

$$= 20 + 30t - 75t^2 + 25t^3$$

$w(4) = (1/2)Li(4)^2 = 0.5 \times 2 \times (-18)^2 = \mathbf{324 \text{ J}}$ .

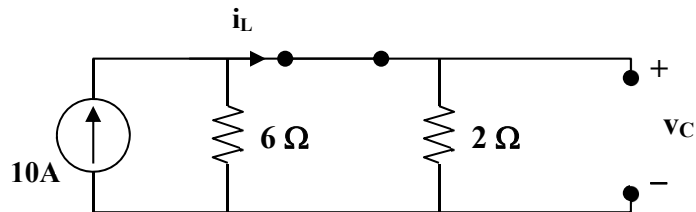**P.P.6.10** Under dc conditions, the circuit is equivalent to that shown below



$$i_L = \frac{3}{1+3}(10) = \mathbf{7.5 \text{ A}}$$

$$v_C = 2i_C = \mathbf{15 \text{ V}}$$

$$w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} (4)(15)^2 = \mathbf{450 \text{ J}}$$

$$w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (6)(7.5)^2 = \mathbf{168.75 \text{ J}}$$

**P.P.6.11** 40mH in series with 20mH = 40 + 20 = 60mH  
 60mH in parallel with 30mH = 30 x 60/(90) = 20mH  
 20mH in series with 100mH = 120mH  
 120mH in parallel with 40mH = 40 x 120/(160) = 30mH  
 30mH in series with 20mH = 50mH  
 50mH in parallel with 50mH = 25mH  
 $L_{eq} = \mathbf{25mH}$

**P.P.6.12** (a)  $i_2 = i - i_1 \longrightarrow i_2(0) = i(0) - i_1(0) = 1.4 - 0.6 = \mathbf{800 \text{ mA}}$

(b)  $v_1 = 6 \frac{di_1}{dt} = 6(0.6)(-2)e^{-2t} = -7.2e^{-2t}$

$$i_2 = \frac{1}{3} \int_0^t v_1 dt + i_2(0) = \frac{1}{3} \frac{(-7.2)}{(-2)} e^{-2t} \Big|_0^t + 0.8$$

$$= \mathbf{(-0.4 + 1.2e^{-2t}) \text{ A}}$$

$$i = i_1 + i_2 = \mathbf{(-0.4 + 1.8e^{-2t}) \text{ A}}$$

(c) From (b),

$$v_1 = \mathbf{-7.2e^{-2t} \text{ V}}$$

$$v_2 = 8 \frac{di}{dt} = 8(-2)(1.8)e^{-2t} = \mathbf{-28.8e^{-2t} \text{ V}}$$

$$v = v_1 + v_2 = \mathbf{-36e^{-2t} \text{ V}}$$