

## Practice Problem 6.1

What is the voltage across a  $4.5\text{-}\mu\text{F}$  capacitor if the charge on one plate is  $0.12\text{ mC}$ ? How much energy is stored?

**Answer:**  $26.67\text{ V}$ ,  $1.6\text{ mJ}$ .

## Practice Problem 6.2

If a  $10\text{-}\mu\text{F}$  capacitor is connected to a voltage source with

$$v(t) = 75 \sin(2,000t) \text{ V}$$

determine the current through the capacitor.

**Answer:**  $1.5 \cos(2,000t) \text{ V}$ .

## Practice Problem 6.3

The current through a  $100\text{-}\mu\text{F}$  capacitor is  $i(t) = 50 \sin 120\pi t \text{ mA}$ . Calculate the voltage across it at  $t = 1\text{ ms}$  and  $t = 5\text{ ms}$ . Take  $v(0) = 0$ .

**Answer:**  $93.14\text{ mV}$ ,  $1.736\text{ V}$ .

## Practice Problem 6.4

An initially uncharged  $1\text{-mF}$  capacitor has the current shown in  Fig. 6.11 across it. Calculate the voltage across it at  $t = 2\text{ ms}$  and  $t = 5\text{ ms}$ .




Figure 6.11

For  Practice Prob. 6.4.

**Answer:**  $100\text{ mV}$ ,  $400\text{ mV}$ .

## Practice Problem 6.5

Under dc conditions, find the energy stored in the capacitors in  Fig. 6.13.

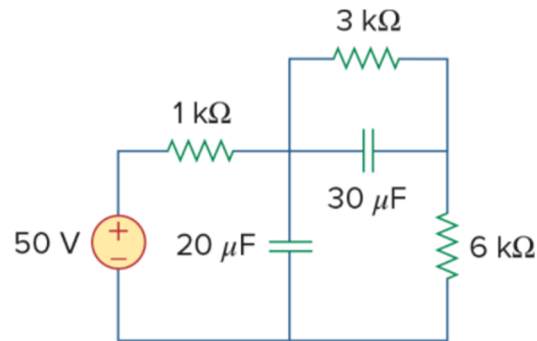



Figure 6.13

For  Practice Prob. 6.5.

**Answer:** 20.25 mJ, 3.375 mJ.

## Practice Problem 6.6

Find the equivalent capacitance seen at the terminals of the circuit in  Fig. 6.17.

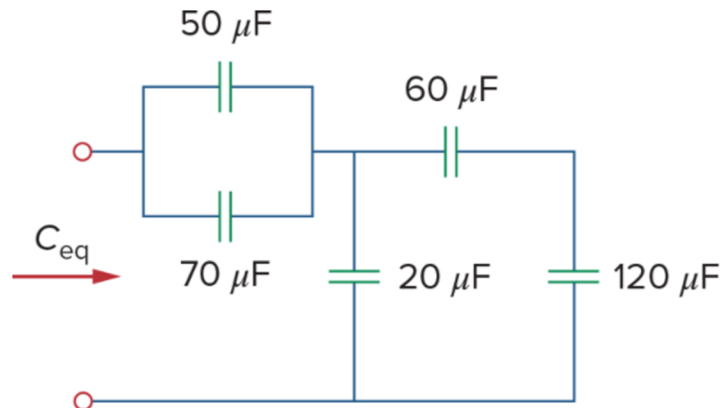



Figure 6.17

For  Practice Prob. 6.6.

## Practice Problem 6.7

Find the voltage across each of the capacitors in  Fig. 6.20.

**Answer:**  $v_1 = 45$  V,  $v_2 = 45$  V,  $v_3 = 15$  V,  $v_4 = 30$  V.

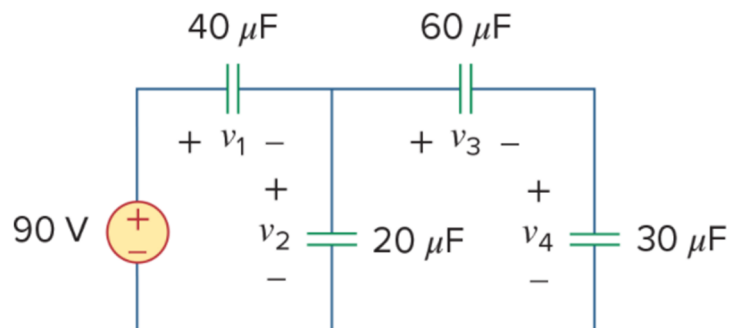


Figure 6.20

For  Practice Prob. 6.7.

### Practice Problem 6.8

If the current through a 1-mH inductor is  $i(t) = 60 \cos(100t)$  mA, find the terminal voltage and the energy stored.

**Answer:**  $-6 \sin(100t)$  mV,  $1.8 \cos^2(100t)$   $\mu$ J.

### Practice Problem 6.9

The terminal voltage of a 2-H inductor is  $v = 10(1 - t)$  V. Find the current flowing through it at  $t = 4$  s and the energy stored in it at  $t = 4$  s. Assume  $i(0) = 2$  A.

**Answer:**  $-18$  A, 324 J.

### Practice Problem 6.10

Determine  $v_C$ ,  $i_L$ , and the energy stored in the capacitor and inductor in the circuit of [Fig. 6.28](#) under dc conditions.

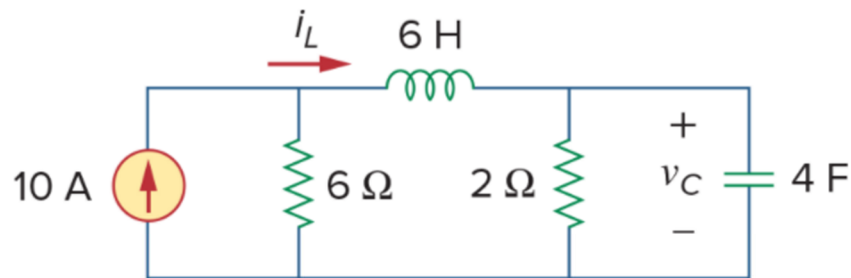


Figure 6.28

For [Practice Prob. 6.10](#).

**Answer:** 15 V, 7.5 A, 450 J, 168.75 J.

### Practice Problem 6.11

Calculate the equivalent inductance for the inductive ladder network in [Fig. 6.32](#).

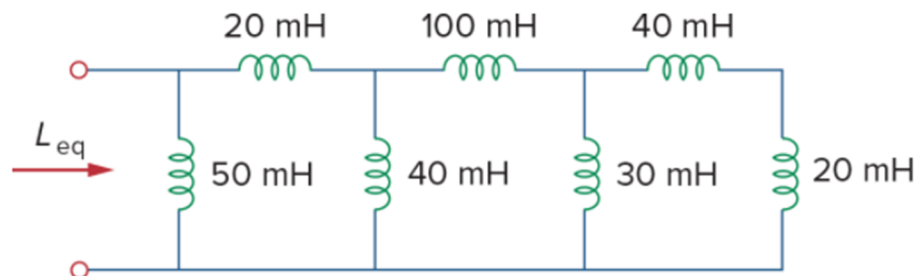


Figure 6.32

For [Practice Prob. 6.11](#).

**Answer:** 25 mH.

## Practice Problem 6.12

In the circuit of [Fig. 6.34](#),  $i_1(t) = 600e^{-2t}$  mA. If  $i(0) = 1.4$  A, find: (a)  $i_2(0)$ ; (b)  $i_2(t)$  and  $i(t)$ ; (c)  $v_1(t)$ ,  $v_2(t)$ , and  $v(t)$ .

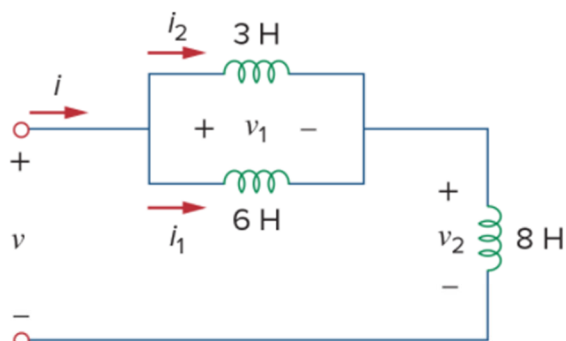


Figure 6.34

For [Practice Prob. 6.12](#).

**Answer:** (a) 800 mA, (b)  $(-0.4 + 1.2e^{-2t})$  A,  $(-0.4 + 1.8e^{-2t})$  A, (c)  $-36e^{-2t}$  V,  $-7.2e^{-2t}$  V,  $-28.8e^{-2t}$  V.