

EE2000 Logic Circuit Design

Chapter 3 – Combinational Logic Circuit Design

Outline



- 3.1 Design Procedure
- 3.2 Examples
 - Bi-switch lighting controller
 - Code converter
 - 7-segment display
- 3.3 Timing Hazard

3.1 Design Procedure

- 1. State the problem / specification for the design.
- 2. Determine the number of input variables and output variables.
- 3. Formulate truth tables / Boolean functions between inputs and outputs.
- 4. Simplification / minimization for the logic functions.
- 5. Design and draw the logic circuit diagram.

3.2 Examples

- Bi-switch lighting controller

  


State the case

Design a circuit to control the bulb

- The light turns on when both buttons are turned UP / DOWN.
- The light turns off when both buttons swap in different positions.
- ON / OFF light is a binary decision output.
- Button positions are the inputs (variables)

Formulation

 

Assume that two variables **A** and **B** are the button positions. And **F** is binary decision output of **A** and **B**.

0 is the button turns UP.

1 is the button turns DOWN.

Inputs		Output
A	B	F
0	0	1
0	1	0
1	0	0
1	1	1



$F(A, B)$ is 1 if $(A = 0 \text{ AND } B = 0)$ OR $(A = 1 \text{ AND } B = 1)$




i.e. $F(A, B) = A'B' + AB = \sum m(0, 3)$

■ Optimization:

■ From the truth table,

■ $F(A, B) = AB + A'B' (= A \otimes B)$


logic circuit diagram

   

 3.2 Examples

- Code converter

■ Design a logic circuit that perform code conversion



- Input is BCD 8421 code
- Output is Excess-3 code

State the case

Design a circuit to convert the BCD to the Excess-3 code

- A, B, C, D are the input of BCD.
- W, X, Y, Z are the output of Excess-3 code.
- The output functions are:
 $W(A, B, C, D)$
 $X(A, B, C, D)$
 $Y(A, B, C, D)$
 $Z(A, B, C, D)$

Formulation

Decimal digit	Input (8421 code)				Output (Excess-3 code)			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
Unused	X	X	X	X	X	X	X	X
Unused	X	X	X	X	X	X	X	X
Unused	X	X	X	X	X	X	X	X
Unused	X	X	X	X	X	X	X	X
Unused	X	X	X	X	X	X	X	X
Unused	X	X	X	X	X	X	X	X

Unused outputs can consider as DON'T CARE.

Formulation

- There are four variables (A, B, C, D) in the functions
- Each output variable depends on 4 variables
- So we need 4 four-variable K-maps
 - $W(A, B, C, D) = \Sigma m(5, 6, 7, 8, 9) + \Sigma d(10, 11, 12, 13, 14, 15)$
 - $X(A, B, C, D) = \Sigma m(1, 2, 3, 4, 9) + \Sigma d(10, 11, 12, 13, 14, 15)$
 - $Y(A, B, C, D) = \Sigma m(0, 3, 4, 7, 8) + \Sigma d(10, 11, 12, 13, 14, 15)$
 - $Z(A, B, C, D) = \Sigma m(0, 2, 4, 6, 8) + \Sigma d(10, 11, 12, 13, 14, 15)$

Minimization

K-map for W:

		AB			
		00	01	11	10
CD	00			x	1
	01		1	x	1
	11		1	x	x
	10		1	x	x

K-map for X:

		AB			
		00	01	11	10
CD	00		1	x	
	01	1		x	1
	11	1		x	x
	10	1		x	x





K-map for Y:

		AB			
		00	01	11	10
CD	00	1	1	x	1
	01			x	
	11	1	1	x	x
	10			x	x

K-map for Z:

		AB			
		00	01	11	10
CD	00	1	1	x	1
	01			x	
	11			x	x
	10	1	1	x	x

Minimization

    

Logic functions and circuit

- From the pervious K-maps,

- $W = A + BC + BD$

- $X = B'C + B'D + BC'D'$

- $Y = CD + C'D'$

- $Z = D'$


- We further optimize them (optional)

- $W = A + BC + BD = A + B(C+D)$

- $X = B'C + B'D + BC'D' = B'(C+D) + B(C+D)'$


- $Y = CD + C'D' = CD + (C+D)'$

DeMorgan's theorem

 

3.2 Examples

- 7-segment display

 

Formulation

Input BCD				Seven-Segment Display						
<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	x	x	x	x	x	x	x
1	0	1	1	x	x	x	x	x	x	x
1	1	0	0	x	x	x	x	x	x	x
1	1	0	1	x	x	x	x	x	x	x
1	1	1	0	x	x	x	x	x	x	x
1	1	1	1	x	x	x	x	x	x	x

Note: The corresponding outputs of those unused BCD code should be either 0 or don't care (depends on the specification)

Formulation

- Number of variables (input)?
- Number of functions (output)?
- Number of K-map?
- Example of functions:
- $$a(w, x, y, z) = \sum m(0, 2, 3, 5, 6, 7, 8, 9) + \sum d(10, 11, 12, 13, 14, 15)$$

K-maps of segment-*a*

	wx	00	01	11	10
yz	00	1		x	1
	01		1	x	1
	11	1	1	x	x
	10	1	1	x	x

	wx	00	01	11	10
yz	00	1		x	1
	01		1	x	1
	11	1	1	x	x
	10	1	1	x	x


$$a(w, x, y, z) = w + y + xz + x'z'$$

Exercise: find the simplified expression of *b*, *c*, *d*, *e*, *f* and *g*

3.3 Timing Hazard

- Logic devices (gates or other more complex circuits) are essentially made from semiconductor
- IC input impedance and PCB copper track inductance cause charging and discharging effect (similar to RC circuit response)
- The “real” input and output voltages are not a perfect step function
- Practical logic input and output waveforms exhibit “delay” nature

I/P and O/P waveform



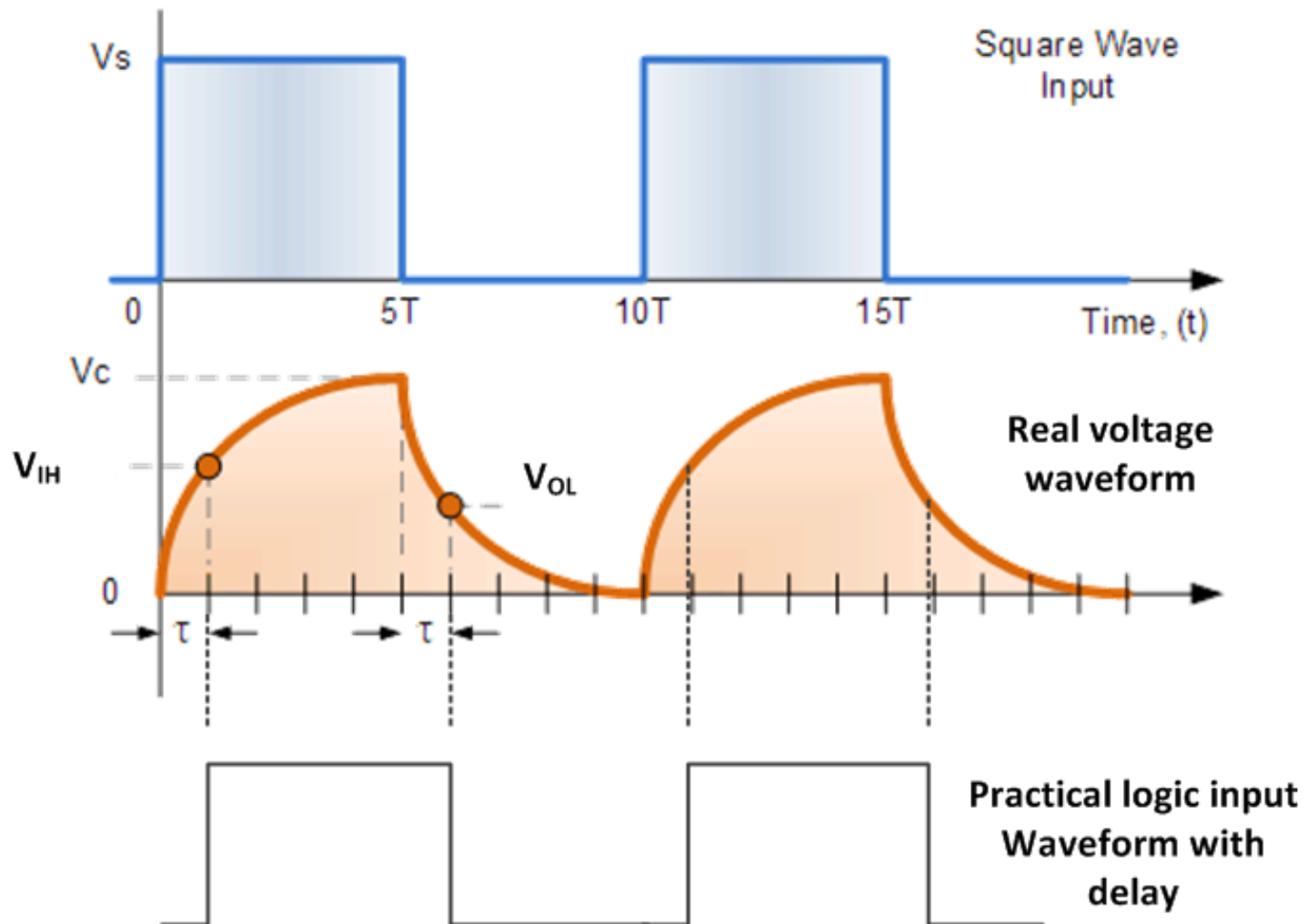


Timing Diagram

- The horizontal axis represents time
- The vertical axis shows a signal between 2 possible voltage levels



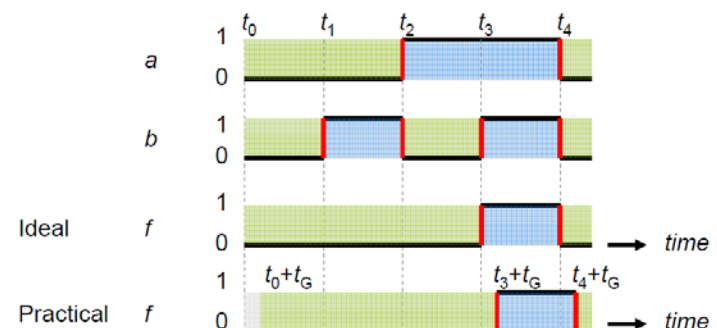  - When time is between t_0 to t_1 , a is 1
- At time t_1 , a is **changing** from 1 to 0
- When time is after t_1 , a becomes 0



Timing Hazards


- The circuit output may produce a short pulse (which should not be happened) at the transient time caused by delay in propagation of signals
- Two kinds of hazards: **static** and **dynamic**



Static-0 hazard: the output may momentarily go to 1 when it should *remain 0*



 Static-1 hazard: the output may momentarily go to 0 when it should *remain 1*




Dynamic hazard: The output changes three or more times when it should change from 1 to 0 or from 0 to 1 *only once*


Timing Hazard

Gate Delay

 - Output waveform is shifted t_G time units
- The length of time for an input change, to result in the corresponding output change



 - The propagation delay could cause undesirable events: **timing hazards**



Assuming that the delay of the gates are different as shown above.


With the initial input condition:


$$xyz = 111$$

Now, change z from "1" to "0".

Then the associated gate outputs will be change after their corresponding delays.

 An unwanted glitch will appear at the output – **static-1 hazard !!!**



 

Consider a different case


With the initial input condition:

$$xyz = 110$$


Now, change z from "0" to "1".

NO glitch !!!

 Hazard only occurs when input of xyz change from 111 to 110, NOT for the case of from 110 to 111.



Example

 


Now z changes from 1 to 0 at time t_0

But p changes from 0 to 1 after one t_{PD} time unit (r changes too)

Initial conditions:
(x, y, z) = (1, 1, 1)

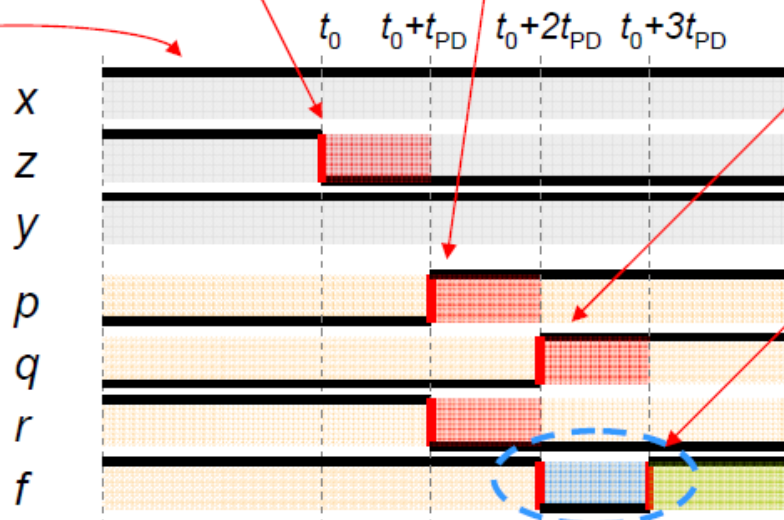Corresponding
output: (p, q, r, f)
= (0, 0, 1, 1)



Since p & r has changed, q & f change accordingly after another t_{PD} time unit


As q has changed, f changes again after another t_{PD} time unit. A static-1 hazard has formed

Timing hazard elimination

- The occurrence of the hazard can be detected by inspecting the K-map of the particular circuit.
- Eliminating a hazard is to enclose the two minterms in question with another product term that overlaps both groupings.
- The removal of hazards requires the addition of redundant gates to the circuit.


K-map for eliminating timing hazard

■ $f(x, y, z) = xz' + yz$

 

The optimal grouping

 Static-1 hazard occurs when
change from 111 to 110




Include an redundant product term

$$f = xz' + yz + xy$$

Now the hazard is removed!

Use K-map to Eliminate Hazards

 - To eliminating the hazard, group the two minterms that cause the hazards
- An additional redundant product term (gate) is introduced



Hazard-free realization

- General idea: to include all PIs
- Work for both K-map and QM-method

Please try to develop a hazard-free circuit for the function

$$f(a, b, c) = \sum m(0, 2, 4, 5)$$

Steps:

- a) Minimize the function f
- b) Realize f to a hazard-free circuit