

Phasor

Practice Problem 10.1

Using nodal analysis, find v_1 and v_2 in the circuit of Fig. 10.3.

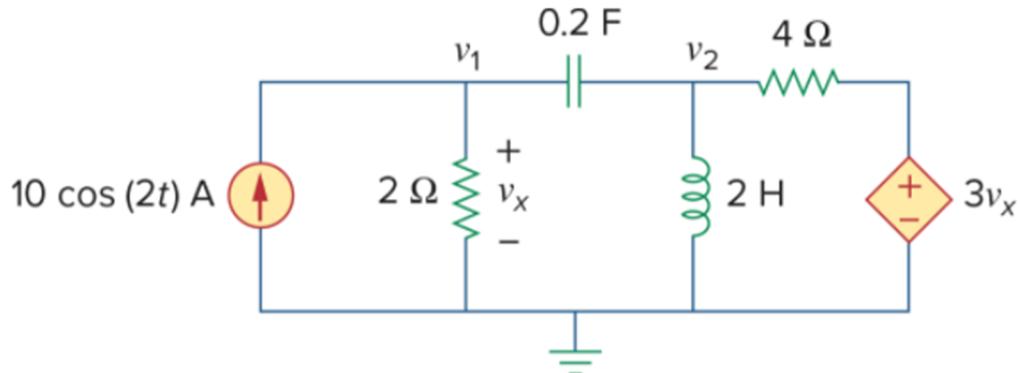


Figure 10.3

For Practice Prob. 10.1.

Answer: $v_1(t) = 11.325 \cos(2t + 60.01^\circ)$ V, $v_2(t) = 33.02 \cos(2t + 57.12^\circ)$ V.

Practice Problem 10.2

Calculate \mathbf{V}_1 and \mathbf{V}_2 in the circuit shown in Fig. 10.6.

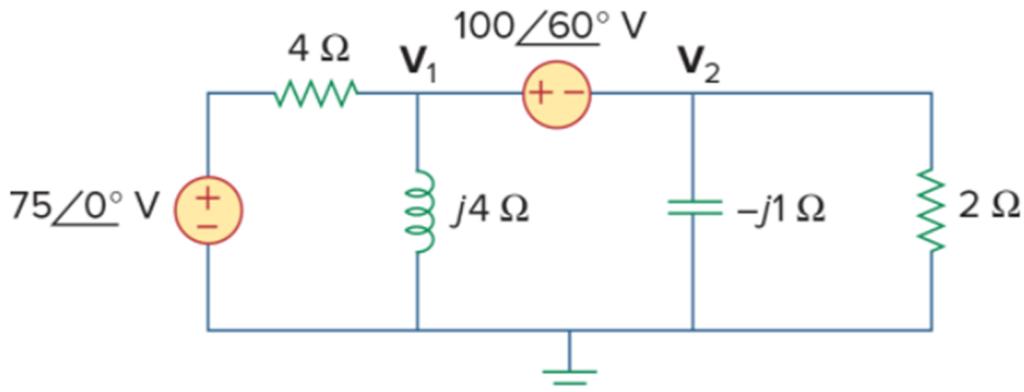


Figure 10.6

For Practice Prob. 10.2.

Answer: $\mathbf{V}_1 = 96.8 \angle 69.66^\circ$ V, $\mathbf{V}_2 = 16.88 \angle 165.72^\circ$ V.

Practice Problem 10.3

Find \mathbf{I}_o in Fig. 10.8 using mesh analysis.

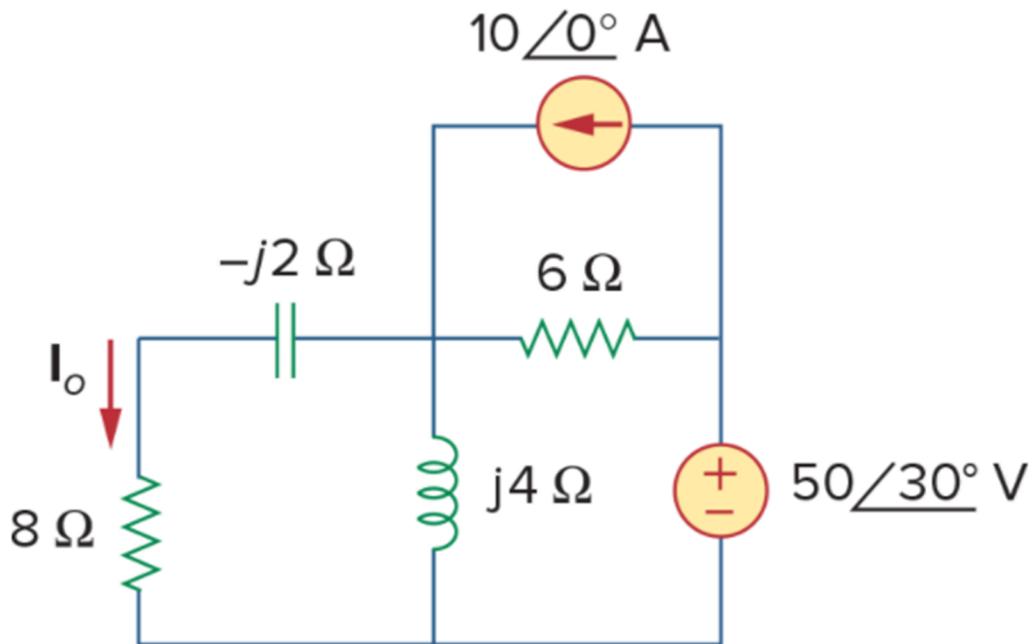


Figure 10.8
For Practice Prob. 10.3.

Answer: $5.969 \angle 65.45^\circ$ A.

Practice Problem 10.5

Find current \mathbf{I}_o in the circuit of Fig. 10.8 using the superposition theorem.

Answer: $5.97 \angle 65.45^\circ$ A.

Practice Problem 10.6

Calculate v_o in the circuit of Fig. 10.15 using the superposition theorem.

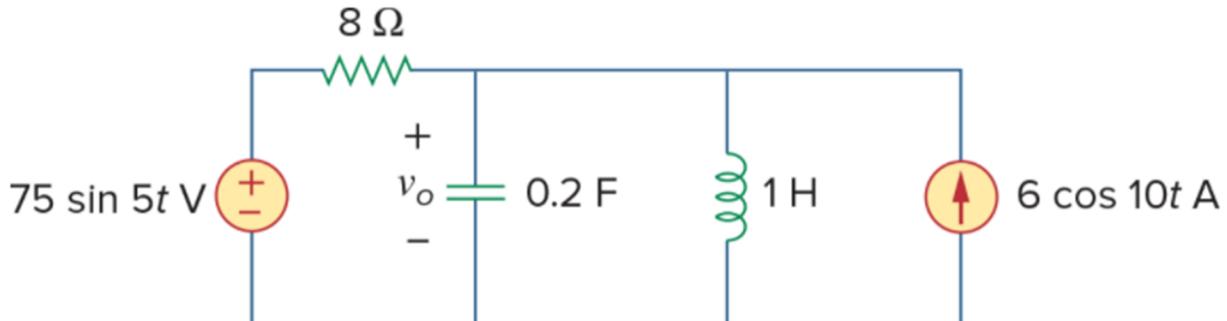


Figure 10.15

For Practice Prob. 10.6.

Answer: $11.577 \sin(5t - 81.12^\circ) + 3.154 \cos(10t - 86.24^\circ)$ V.

Practice Problem 10.7

Find I_o in the circuit of Fig. 10.19 using the concept of source transformation.

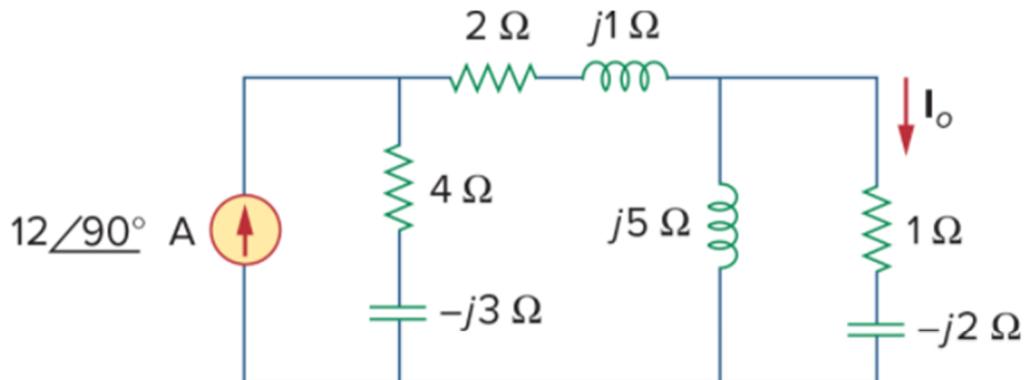


Figure 10.19

For Practice Prob. 10.7.

Answer: $9.863 \angle 99.46^\circ$ A.

Practice Problem 10.8

Find the Thevenin equivalent at terminals $a-b$ of the circuit in Fig. 10.24.

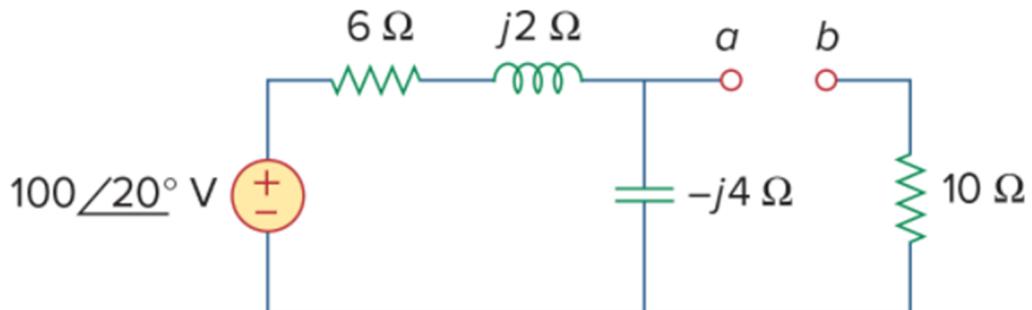


Figure 10.24

For Fig. Practice Prob. 10.8.

Answer: $Z_{Th} = 12.4 - j3.2 \Omega$, $V_{Th} = 63.24 \angle -51.57^\circ$ V.

Practice Problem 10.9

Determine the Thevenin equivalent of the circuit in Fig. 10.27 as seen from the terminals $a-b$.

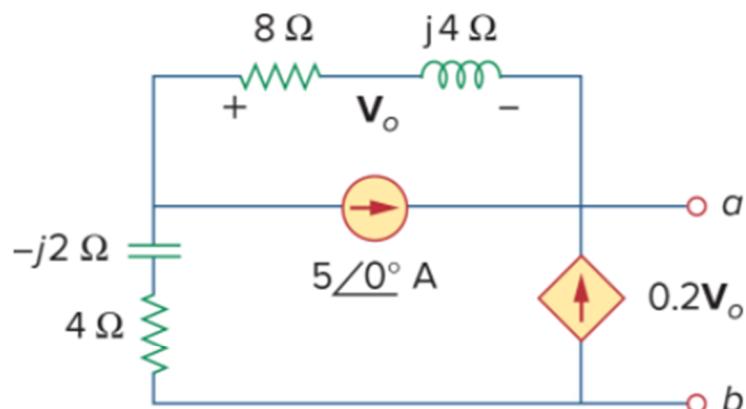


Figure 10.27

For Fig. Practice Prob. 10.9.

Answer: $Z_{Th} = 4.473 \angle -7.64^\circ \Omega$, $V_{Th} = 7.35 \angle 72.9^\circ$ volts.

Practice Problem 10.10

Determine the Norton equivalent of the circuit in Fig. 10.30 as seen from terminals *a*-*b*. Use the equivalent to find \mathbf{I}_o .

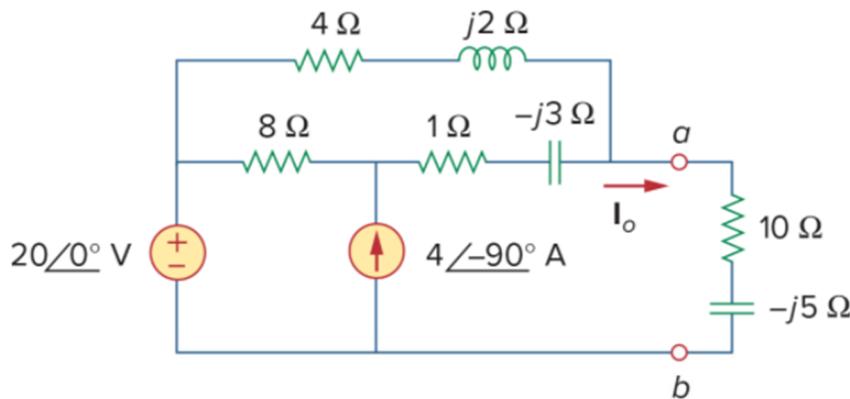


Figure 10.30

For Practice Prob. 10.10 and Prob. 10.35.

Answer: $\mathbf{Z}_N = 3.176 + j0.706 \Omega$, $\mathbf{I}_N = 8.396 \angle -32.68^\circ \text{ A}$, $\mathbf{I}_o = 1.9714 \angle -2.10^\circ \text{ A}$.

RMS

Practice Problem 11.7

Find the rms value of the current waveform of Fig. 11.15. If the current flows through a 9-Ω resistor, calculate the average power absorbed by the resistor.

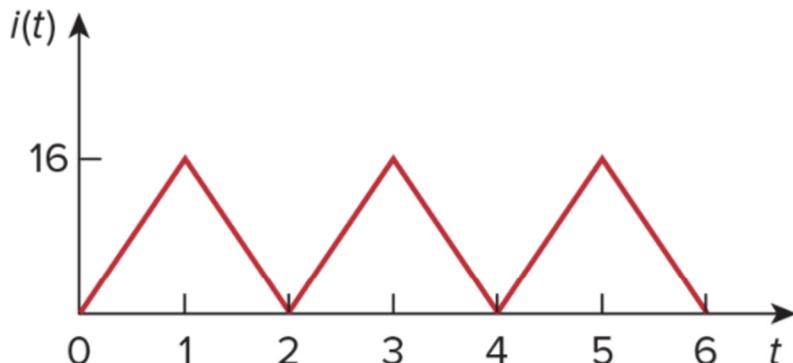


Figure 11.15

For Practice Prob. 11.7.

Answer: 9.238 A, 768 W.

Practice Problem 11.8

Find the rms value of the full-wave rectified sine wave in [Fig. 11.17](#). Calculate the average power dissipated in a $6\text{-}\Omega$ resistor.

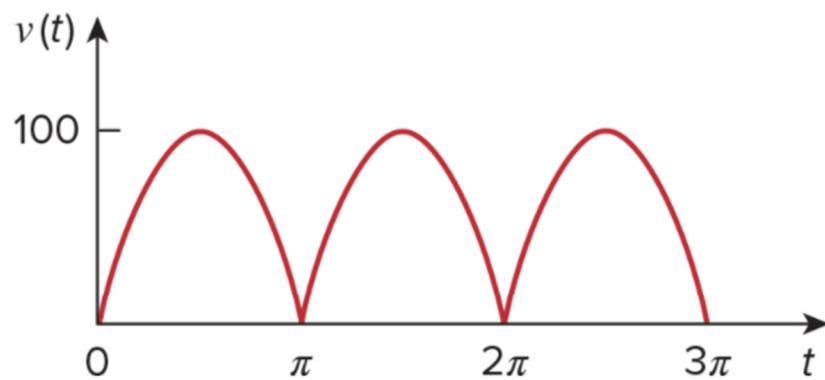


Figure 11.17

For [Practice Prob. 11.8](#).

Answer: 70.71 V, 833.3 W.