

**EE 2000 Logic Circuit  
Design Semester A 2021/22A**

Tutorial 1

1. Simplify the following expressions using boolean algebra

$$f(x, y, z) = \overline{x}z + y\overline{z} + \overline{x}y\overline{z} + xy$$

$$F(A, B, C) = A\overline{B}(\overline{B} + \overline{C})(A + C)$$

2. Simplify the following expressions using k-map.

(a)  $f = \overline{a}bc + \overline{b}\overline{c}\overline{d} + bcd + ac\overline{d} + \overline{a}\overline{b}c + \overline{a}bcd$

(b)  $f = wxy + yz + x\overline{y}z + \overline{x}y$

(c)  $f(a, b, c, d) = \Sigma m(4, 6, 7, 15)$

(d)  $f(a, b, c, d) = \Sigma m(3, 7, 11, 13, 14, 15)$

(e)  $f(a, b, c, d) = \Sigma m(0, 6, 8, 13, 14) + \Sigma d(2, 4, 10)$

(f)  $f(a, b, c, d) = \Sigma m(1, 3, 5, 7, 9, 15) + \Sigma d(4, 6, 12, 13)$

3. Map the following SOP expression on a K-map.


$$\overline{B}\overline{C} + \overline{A}\overline{B} + \overline{A}B\overline{C} + \overline{A}\overline{B}CD + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D$$

4. A simple locker system that has a output signal  $Z = 1$  when the hexadecimal keypad input is either 0, 1, 2, 3, 4, 5, 8, 9, or A; otherwise  $Z = 0$ . Assume that  $A_0 A_1 A_2 A_3$  represent a 4-digit binary number output from the keypad. Block A decodes these signals and outputs the signal  $Z$ .

(i) Write down the truth table of Block A.

(ii) Find the SOP and POS expression of Block A.

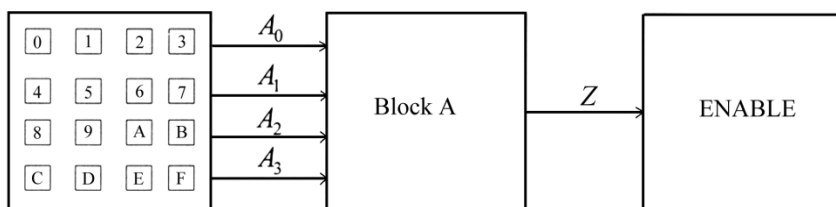(iii) Design the circuit of Block A using minimum number of AND, OR and NOT gates.




5. (a) Draw the logic circuit of the following Boolean function without simplification:

$$Y(A, B, C) = ABC + AB'(A'C)'$$

- (b) Simplify the logic function in (a) and, hence, re-draw the logic circuit.

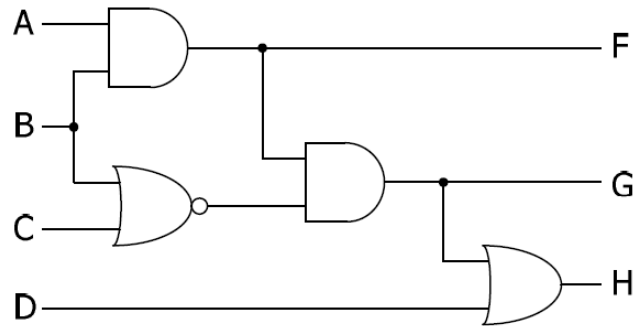6. (a) Derive Boolean functions to describe the operations of the logic circuit as follow:



- (b) Hence, simplify and draw a new logic circuit.

7. (a) Use a K-map to convert the following canonical SOP expression into a minimum POS expression.

$$f(a,b,c,d) = \sum m(0,1,2,5,7,8,10,13,14,15)$$

- (b) Use a K-map to convert the following canonical POS expression into a minimum SOP expression.

$$f(a,b,c,d) = \prod M(0,2,5,7,8,9,13)$$