

Block B Unit 3 Outline

1) First-order circuits

- Methodology [Section 7.1]
- RC and RL circuits [Section 7.2, 7.3]

Alexander & Sadiku,
“Fundamentals of Electric Circuits”
7th Edition Chapter 7

2) Step response

- RC circuit [Section 7.5]
- RL circuit [Section 7.6]

First-order Circuits

- 1) Apply Kirchhoff's laws to purely resistive circuits, resulting in algebraic equations
 - 2) Apply Kirchhoff's laws to RC and RL circuits, produces first order differential equations
- A first-order circuit is characterized by a first-order differential equation
 - Two ways to excite the circuits
 - 1) Source-free circuits, initial conditions of the storage elements
 - 2) By independent sources, i.e. dc sources

1.1 Source-Free RC Circuit


- A source-free RC circuit occurs when its dc source is suddenly disconnected.
- The energy that is initially stored in the capacitor is eventually dissipated in the resistor
- Capacitor is initially charged
- Initial value of energy stored

Initial voltage: $v(0) = V_0$

$$w(0) = \frac{1}{2} C V_0^2$$

- Apply KCL, $i_C + i_R = 0$
- By definition, $i_C = C dv/dt$, $i_R = v/R$
- Circuit response, the circuit reacts to


$v(t) = V_0 e^{-t/RC}$ an excitation.

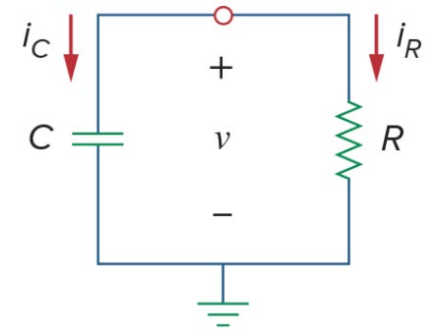

A source-free RC circuit

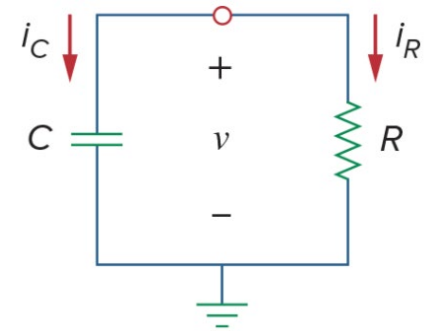1.1 Source-Free RC Circuit


- Derivation of RC circuit response: $v(t) = V_0 e^{-t/RC}$




A source-free RC circuit

Natural Response of RC Circuit

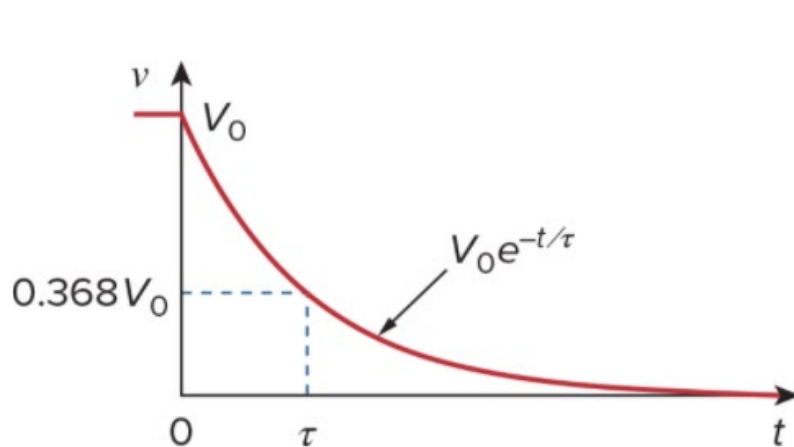- Voltage response of the RC circuit is an exponential decay of the initial voltage
- The voltage response is due to the initial energy stored, and not due to external voltage or current source
- Time constant ($\tau = RC$), is the same regardless of what the output is defined to be. $v(t) = V_0 e^{-t/\tau}$



Voltage response of RC circuit

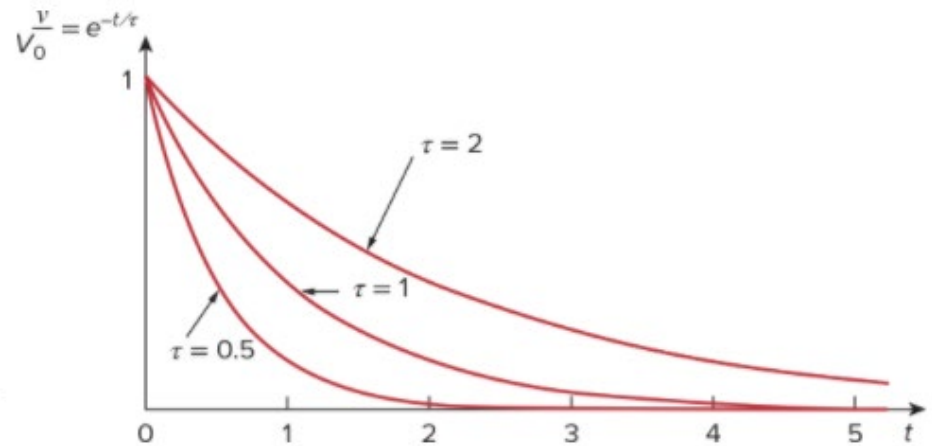

Small time constant gives a fast response


Thevenin's Theorem in RC Circuit

- Once $v(t)$ is obtained, i_C , v_R , and i_R can be determined.
- R , the Thevenin equivalent resistance at the terminals of the capacitor
- Take out the capacitor C , find $R = R_{th}$ at terminals
- Method:
 - Single capacitor, find Thevenin equivalent at the terminals of the capacitor
 - Several capacitors, combine to form a single equivalent capacitor, find Thevenin equivalent
 - Obtain capacitor voltage, v_C
 - Then determine v_x and i_x

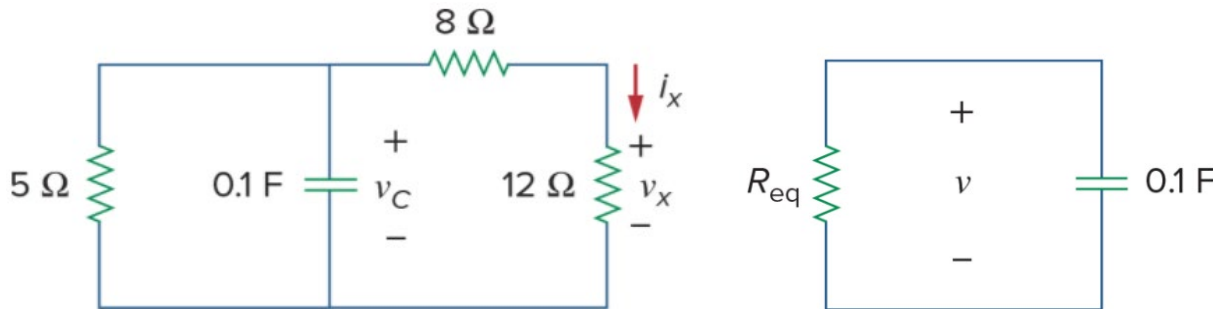Example 1.1.1

- Let $v_C(0) = 15 \text{ V}$. Find v_C , v_x and i_x for $t > 0$.

(Ans. $15e^{-2.5t} \text{ V}$, $9e^{-2.5t} \text{ V}$, $0.75e^{-2.5t} \text{ A}$)



General steps:

Step 1, find R_{eq}

Step 2 find τ

Step 3, find v_C

Step 4, find v_x and i_x

$$R_{eq} = \frac{20 \times 5}{20 + 5} = 4 \Omega$$




$$v_C = v = 15e^{-2.5t} \text{ V}$$

By voltage divider, $v_x =$

By ohm's law, $i_x =$

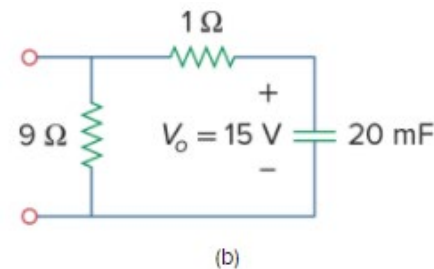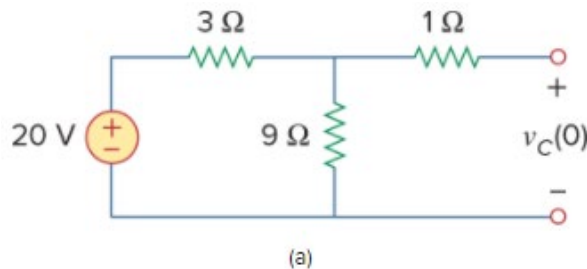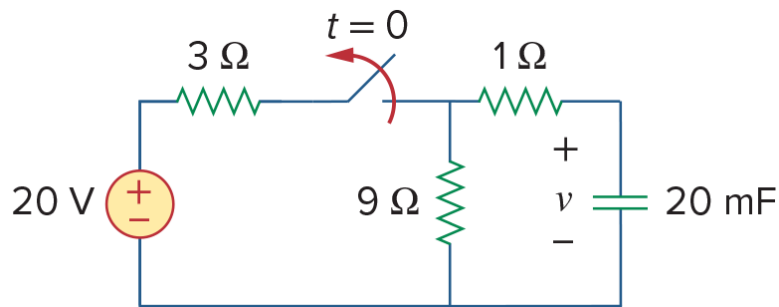Example 1.1.2

The switch has been closed for a long time, and it is opened at $t = 0$. Find $v(t)$, the voltage across the capacitor, for $t \geq 0$. ($15e^{-5t}$ V)



(a) $t < 0$, (b) $t > 0$.

- Fig. (a), for $t < 0$, switch is closed, capacitor is open (at DC)..

At $t < 0$, $v_C(t) =$

At $t = 0$, $v_C(0) = V_0 = 15V$

- Fig. (b), for $t > 0$, switch is open.

Step 1: $R_{eq} =$

Step 2: Time constant (τ) =

Step 3: At $t > 0$, voltage across the capacitor, $v_c(t) =$

1.2 Source-Free RL Circuit


- Circuit response, the current $i(t)$ through the inductor
- For inductor, current cannot change instantaneously
- Initial current: $i(0) = I_0$
- Initial value of energy stored

Apply KVL, $v_L + v_R = 0$

By definition, $v_L = L \, di/dt$

$$L \frac{di}{dt} + v_R = 0$$

$$w(0) = \frac{1}{2} L I_0^2$$

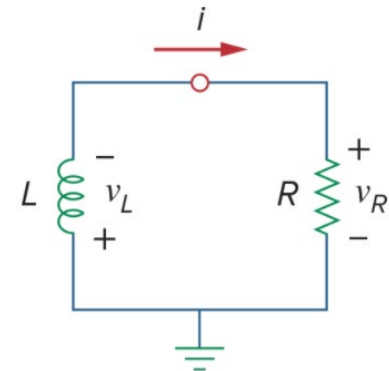


A source-free RL circuit

- Circuit response, $i(t) = I_0 e^{-Rt/L}$

Natural Response of RL Circuit

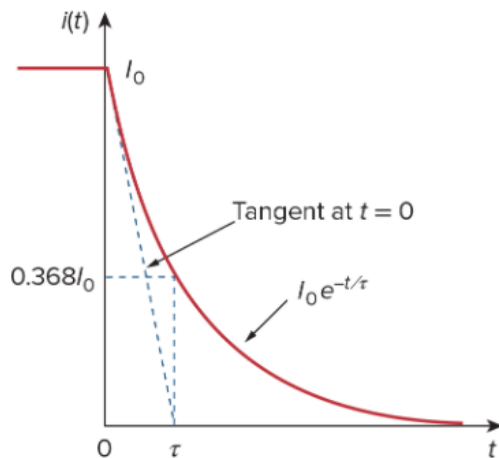- Natural response of the RL circuit is an exponential decay of the initial current
- Time constant, $\tau = \frac{L}{R}$. Current response, $i(t) = I_0 e^{-t/\tau}$
- Voltage across resistor, $v_R(t) = iR =$



- Similar to RC circuit, the smaller the τ of a circuit, the faster the rate of decay of the response.
- The larger the τ , the slower the rate of decay of the response.


Current response of RL circuit

Thevenin's Theorem in RL Circuit

- Once $i_L(t)$ is obtained, v_L , v_R , and i_R can be determined.
- R , the Thevenin equivalent resistance at the terminals of the inductor
- Take out the inductor L , find $R = R_{th}$ at terminals
- Method:
 - Single inductor, find Thevenin equivalent at the terminals of the inductor
 - Several inductors, combine to form a single equivalent inductor, find Thevenin equivalent
 - Obtain inductor voltage, v_L
 - Then determine v_x and i_x

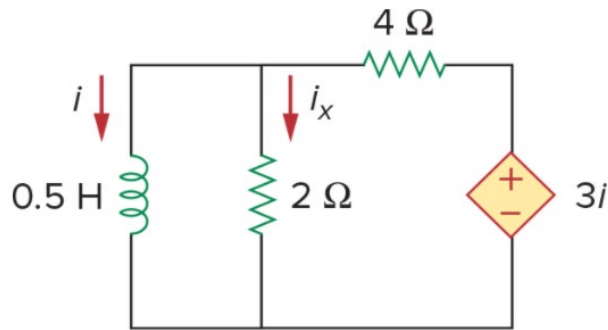Example 1.2.1


Assuming that $i(0) = 10\text{ A}$, calculate $i(t)$, and $i_x(t)$.



Two approach:

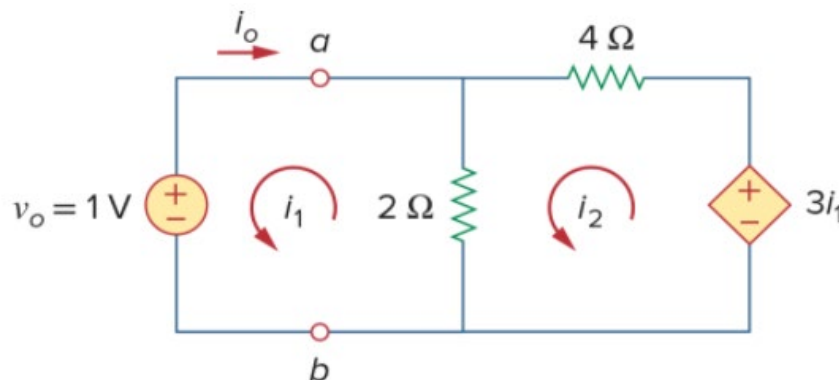1. Obtain equivalent resistance at the inductor terminals, apply current response
 2. Use KVL
- * First obtain the inductor current

- Method 1: Because of the dependent source, insert a voltage source with $v_0 = 1\text{ V}$ at the inductor terminals a-b




Apply KVL, using Mesh Analysis:

$$\text{Left loop: } 1 = 2(i_2 - i_1)$$

$$\text{Right loop: } 3i_1 = 4i_2 + 2(i_2 - i_1)$$



Example 1.2.1 (continued)

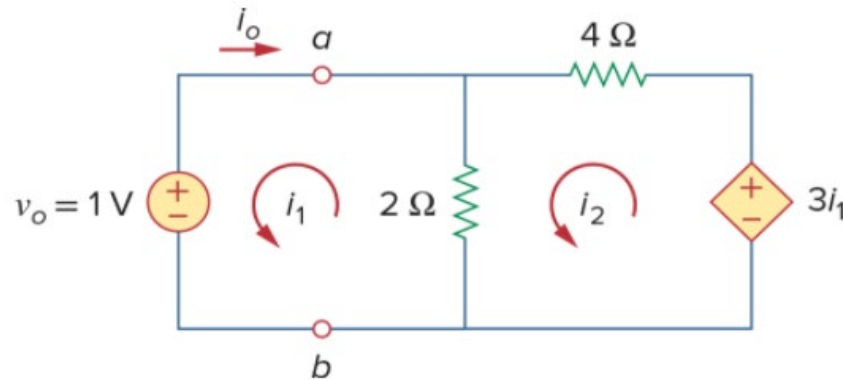

- $i_1 = -3A, i_2 = -2.5A$
- $i_0 = -i_1 = 3A$
- Therefore, R_{eq} (at the terminals of inductor) $= R_{Th} = \frac{v_o}{i_0} = \frac{1}{3} \Omega$
- Time constant $\tau = \frac{L}{R_{eq}} = 1.5 s$
- Circuit response, $i(t) = i(0)e^{-\frac{t}{\tau}} = 10e^{-\left(\frac{2}{3}\right)t} A, t > 0$

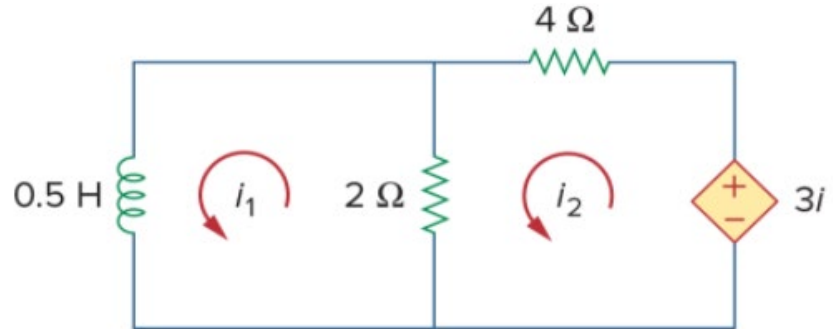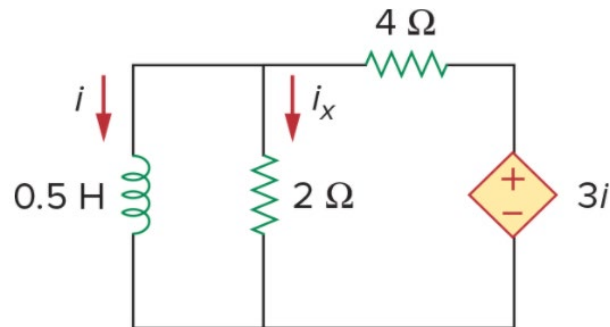Example 1.2.1 (continued)

Method 2: Direct apply KVL to the circuit





$$v_L(t) = L \frac{di}{dt}$$

$$\text{Left loop: } v_L(t) = 0.5 \frac{di_1}{dt} = 2(i_2 - i_1)$$

$$\text{Right loop: } 3i_1 = 4i_2 + 2(i_2 - i_1)$$

Example 1.2.1 (continued)

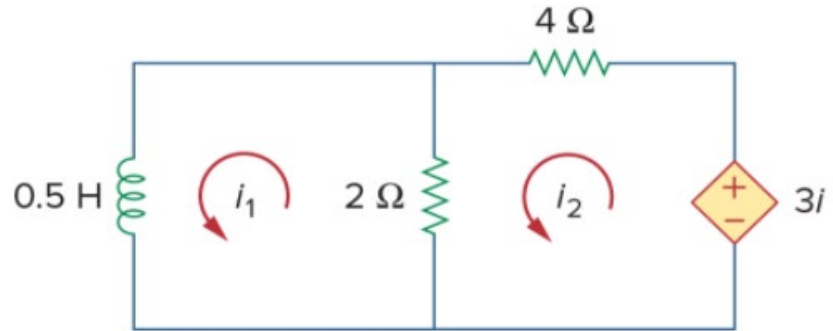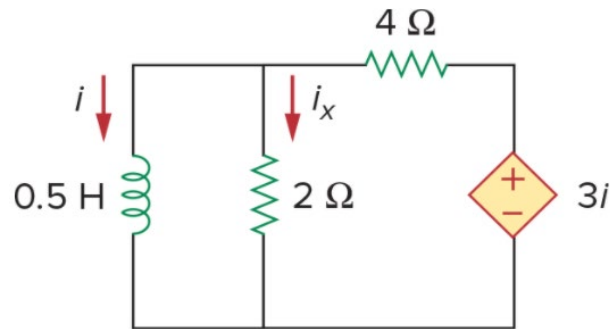


- Circuit response, $i(t) = i(0)e^{-\frac{t}{\tau}} = 10e^{-\left(\frac{2}{3}\right)t} A, t > 0$
- Voltage across the inductor, $v_L(t) = L \frac{di}{dt} = -\frac{10}{3}e^{-\left(\frac{2}{3}\right)t} V$
- Inductor and the 2- Ω resistor are in parallel,

$$i_x(t) = \frac{v_L}{2} = -\frac{5}{3}e^{-\left(\frac{2}{3}\right)t} A, t > 0$$

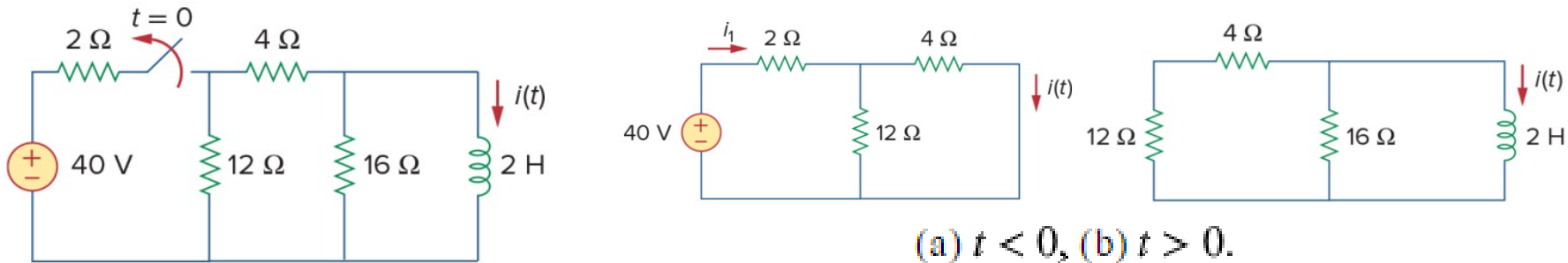Example 1.2.2

The switch in the circuit below has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ for $t > 0$. ($6e^{-4t}$ A)



- Fig. (a), for $t < 0$, switch is closed, inductor is shorted.

At $t < 0$, $i_1 = \frac{40}{2+3} = 8\text{A}$. By current division, $i(t) = \frac{12}{12+4} i_1 = 6\text{A}$

At $t=0$, $i(0) = 6\text{A}$

- Fig. (b), for $t > 0$, switch is open. $R_{eq} = (12 + 4) || 16 = 8\Omega$

Time constant (τ) = $i(t) = i(0)e^{-\frac{t}{\tau}} =$

Transient and Steady-State Response

Complete response = natural response + forced response
stored energy independent source

Complete response = transient response + steady-state response
temporary part permanent part


- **Transient response**, the circuit's temporary response that will die out with time
- **Steady-state response**, the behavior of the circuit a long time after an external excitation is applied
- The complete response is the sum of the transient response and the steady-state response

2.1 Step Response of RC Circuit

- Step response, the response of the circuit due to a sudden application of a dc voltage or current source
- Let the response be the sum of the transient response and the steady-state response

$$v = v_t + v_{SS}$$

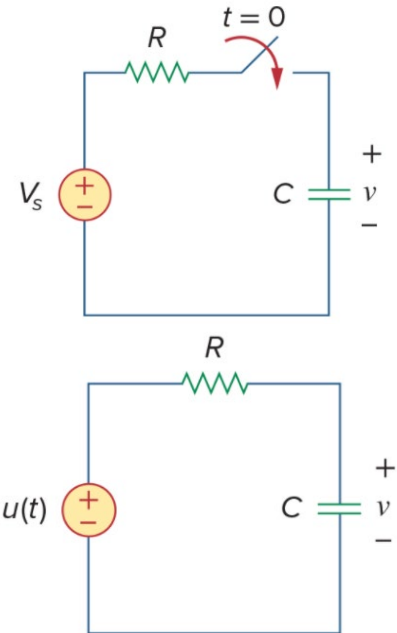- $v_t = Ae^{-t/\tau}$, a decaying exponential, $\tau = RC$, where A is a constant
- $v_{SS} = V_S$, after switch is closed for a long time, capacitor is opened
- $v = Ae^{-t/\tau} + V_S$



An RC circuit with voltage step input

Complete Response of RC Circuit

- Determine A from V_0 , the initial voltage across the capacitor
- At $t = 0$, $V_0 = A + V_S$
- Substitute A in the voltage response equation,

$$v(t) = (V_0 - V_S)e^{-t/\tau} + V_S$$

- Complete response:

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

- Summary to find step response of an RC circuit:
 - (1) Initial capacitor voltage, $v(0)$ at $t = 0$
 - (2) Final capacitor voltage, $v(\infty)$
 - (3) Time constant, $\tau = RC$


With and Without Initial Voltage

Complete response:

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

Capacitor is initially charged:
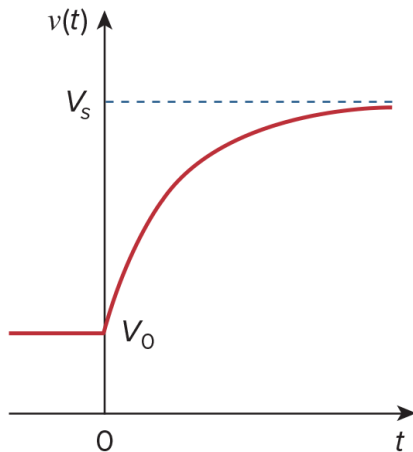
$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$




Response of an RC circuit with initially charged capacitor


Capacitor is uncharged initially ($V_0 = 0$):

$$v(t) = \begin{cases} 0, & t < 0 \\ V_s (1 - e^{-t/\tau}), & t > 0 \end{cases}$$
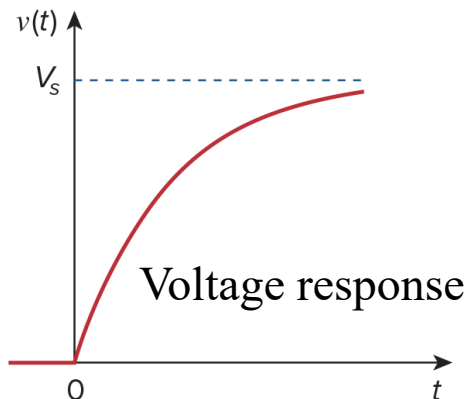
$$i(t) = C \frac{dv}{dt} = \frac{C}{\tau} V_s e^{-t/\tau}, \quad \tau = RC, \quad t > 0$$




Voltage response

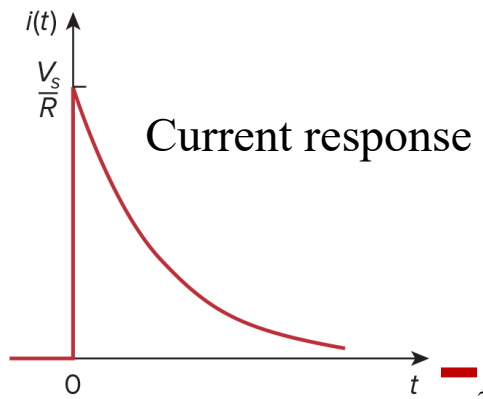

Current response

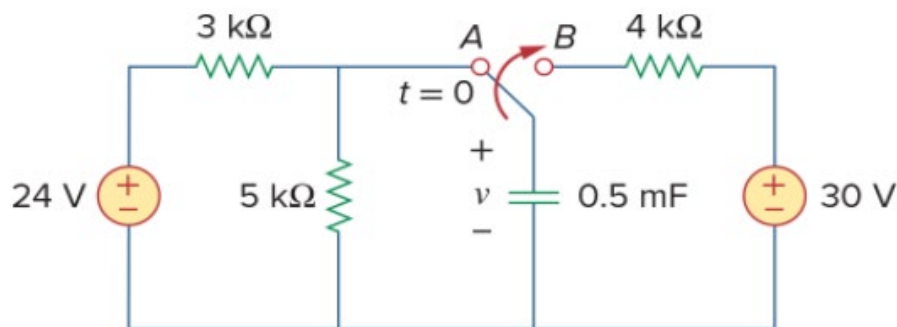Example 2.1.1

The switch in the circuit has been in position A for a long time. At $t = 0$, the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 1$ and 4 s. (Ans. $v(1)=20.9$ V, $v(4)=27.97$ V)



- For $t < 0$, capacitor acts like an open circuit.


By voltage division, $v(0) = 5/(5+3) * 24 = 15$ V

- For $t > 0$, R_{th} (terminals at capacitor) = 4 k Ω , $\tau = R_{Th}C = 2$ s

At dc steady state, $v(\infty) = 30$ V, $v(t) = v(\infty) + (V_0 - v(\infty))e^{-\frac{t}{\tau}}$

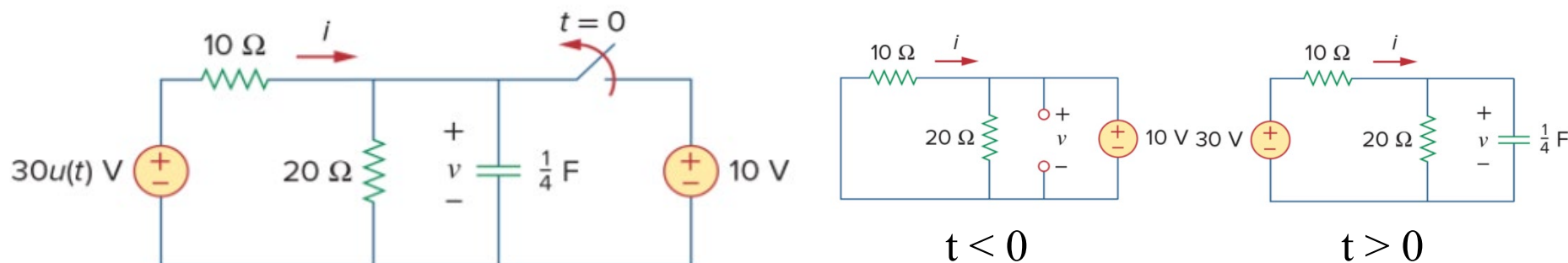Example 2.1.2

The switch has been closed for a long time and is opened at $t = 0$. Find i and v for all time.



- For $t < 0$, switch is closed, capacitor \rightarrow open, $30u(t) = 0$ V,
 $v = v(0) = 10$ V, $I = -v/10 = -1$ A




- For $t > 0$, switch is open, $R_{th} = 10 \parallel 20\ \Omega$, $\tau = R_{Th}C = \frac{5}{3}$ s

After long time, circuit reaches steady-state, capacitor \rightarrow open

$$v(\infty) = 20/(20+10) * 30 = 20$$
 V

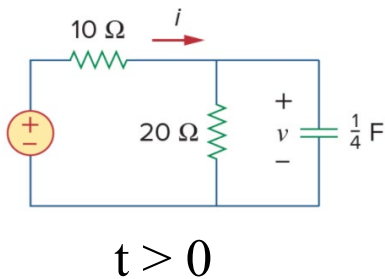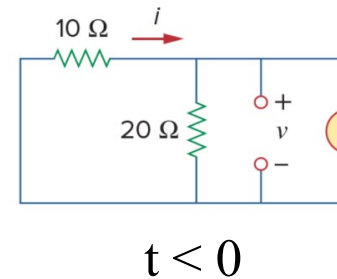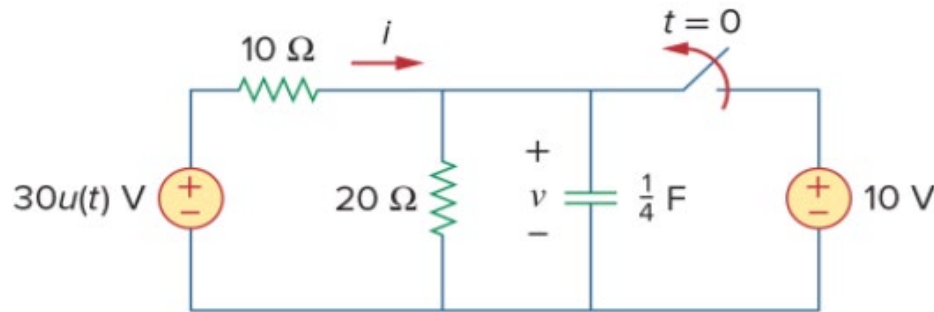Example 2.1.2 (continued)

- $$v(t) = v(\infty) + (V_0 - v(\infty))e^{-\frac{t}{\tau}} = (20 - 10e^{-0.6t})V$$



- To obtain i at $t > 0$, apply KCL,

$$i = \frac{v}{20} + C \frac{dv}{dt} = (1 + e^{-0.6t}) A$$

- Check, apply KVL, $v + 10i = 30$

$$v + 10i = (20 - 10e^{-0.6t}) + 10(1 + e^{-0.6t}) = 30$$


Therefore, the result is confirmed.

2.2 Step Response of RL Circuit


- To find the inductor current i as the circuit response
- Let the response be the sum of the transient response and the steady-state response

$$i = i_t + i_{SS}$$

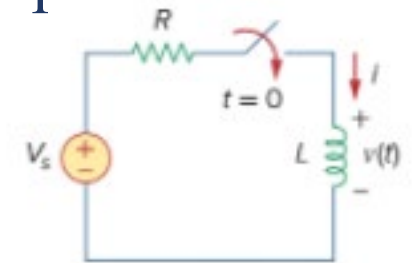- $i_t = Ae^{-t/\tau}$, a decaying exponential, $\tau = \frac{L}{R}$
 , where A is a constant
- $i_{SS} = \frac{V_S}{R}$, after switch is closed for a long time,
 inductor becomes shorted
- $i = Ae^{-t/\tau} + \frac{V_S}{R}$



(a)

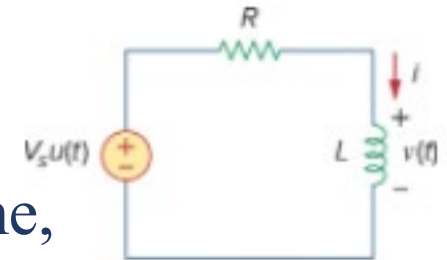

(b)

An RL circuit with voltage step input

Complete Response of RL Circuit

- Determine A from i_0 , the initial current through the inductor
- At $t = 0$, $I_0 = A + \frac{V_S}{R}$
- Substitute A in the circuit response equation,

$$i(t) = (I_0 - \frac{V_S}{R})e^{-t/\tau} + \frac{V_S}{R}$$

- Complete response:

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

- Summary to find step response of an RL circuit:
 - (1) Initial inductor current, $i(0)$ at $t = 0$
 - (2) Final inductor current, $i(\infty)$
 - (3) Time constant, $\tau = L/R$


With and Without Initial Current

Complete response:

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

With initial inductor current:
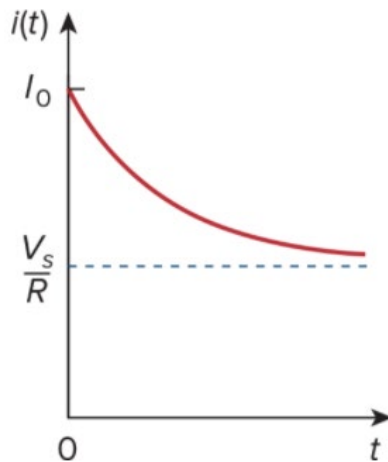
$$i(t) = \frac{V_S}{R} + (I_0 - \frac{V_S}{R})e^{-t/\tau}$$




Complete response of RL circuit
with initial inductor current I_0

Without initial inductor
current ($I_0 = 0$):


$$i(t) = \begin{cases} 0, & t < 0 \\ \frac{V_S}{R} (1 - e^{-t/\tau}), & t > 0 \end{cases}$$

$$v(t) = L \frac{di}{dt} = V_S \frac{L}{\tau R} e^{-t/\tau}, \quad \tau = \frac{L}{R}, \quad t > 0$$

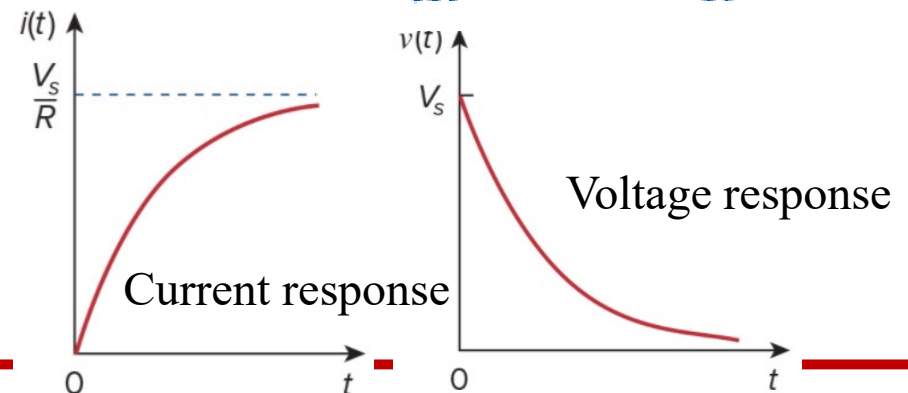

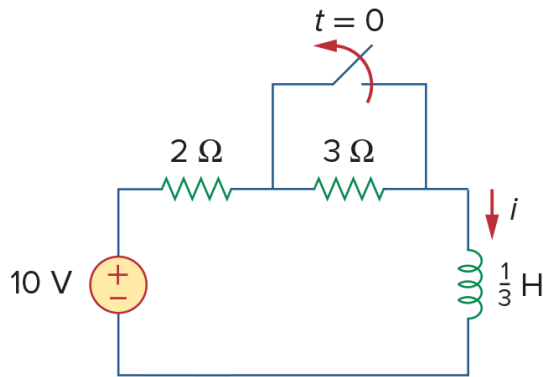Example 2.2.1

Find $i(t)$ in the circuit for $t > 0$. Assume that the switch has been closed for a long time



Solutions:

- When $t < 0$, 3-Ω is shorted, inductor acts like shorted
Current through inductor, $i(0) = 10/2 = 5 \text{ A}$


- When $t > 0$, switch is open, after a long time, inductor acts like shorted
Current through inductor, $i(\infty) = 10/(2+3) = 2 \text{ A}$

- Transient response: consider Thevenin resistance across inductor terminals

$$R_{Th} = 2+3 = 5 \Omega$$

- Time constant, $\tau = L/R_{Th} = 1/15 \text{ s}$

Example 2.2.1 (continued)

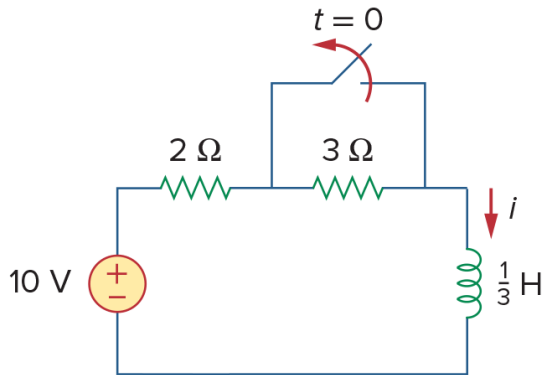

- Using the complete current response $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$

Therefore,

$$i(t) = 2 + 3e^{-t/\tau} A, t > 0$$

- Check:

For $t > 0$, KVL must be satisfied

$$10 = 5i + L \frac{di}{dt}$$

$$5i + L \frac{di}{dt} =$$

- This confirms the result.