
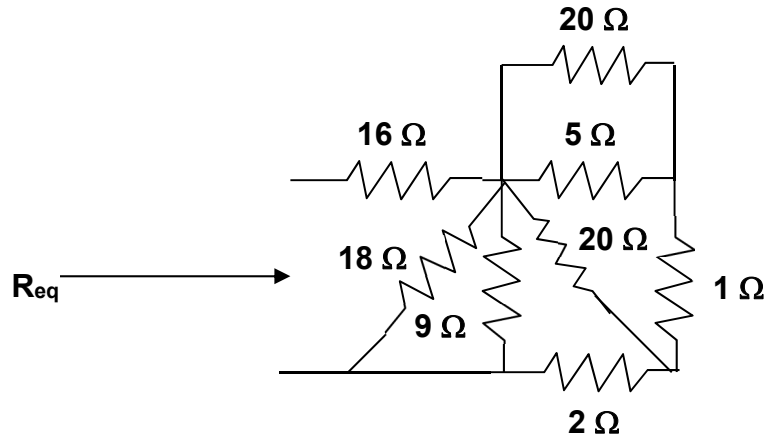


P.P.2.10

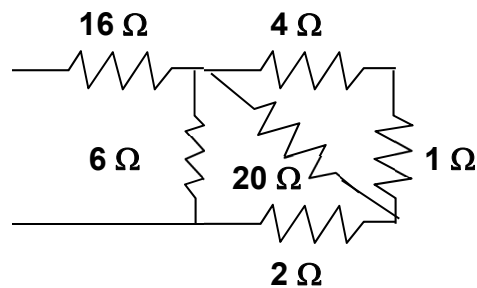


Combining the 9 ohm resistor and the 18 ohm resistor yields $[9 \times 18] / [9 + 18] = 6$ ohms.

Combining the 5 ohm and the 20 ohm resistors in parallel produces $[5 \times 20 / (5 + 20)] = 4$ ohms. We now have the following circuit:



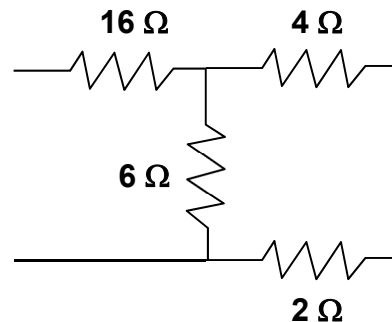
The 4 ohm and 1 ohm resistors can be combined into a 5 ohm resistor in parallel with a 20 ohm resistor. This will result in $[5 \times 20 / (5 + 20)] = 4$ ohms and the circuit shown below:



The 4 ohm and 2 ohm resistors are in series and can be replaced by a 6 ohm resistor. This gives a 6 ohm resistor in parallel with a 6 ohm resistor, $[6 \times 6 / (6 + 6)] = 3$ ohms. We now have a 3 ohm resistor in series with a 16 ohm resistor or $3 + 16 = 19$ ohms. Therefore:

$$R_{eq} = 19 \text{ ohms}$$


P.P. 2.11

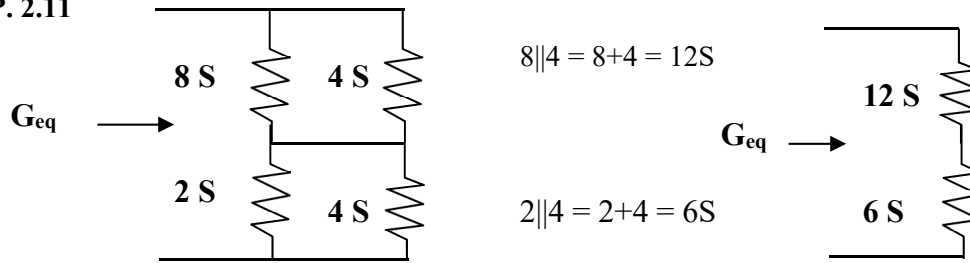

12 S in series with 6 S = $\{12 \times 6 / (12 + 6)\} = 4$ or:

$$G_{eq} = 4 \text{ S}$$

P.P.2.12

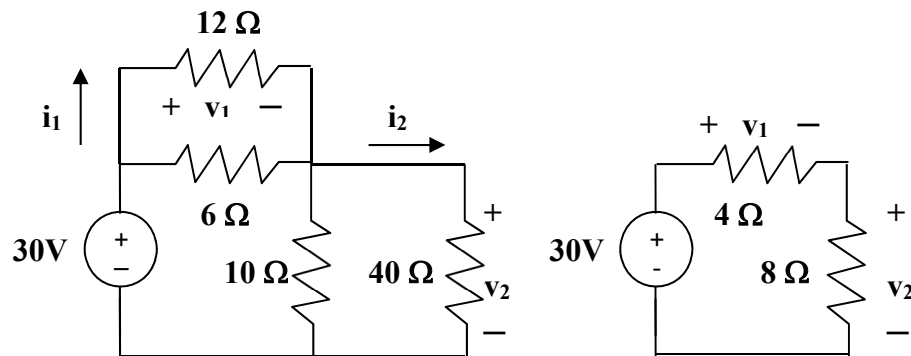

$6 \parallel 12 = [6 \times 12 / (6 + 12)] = 4 \text{ ohm}$ and $10 \parallel 40 = [10 \times 40 / (10 + 40)] = 8 \text{ ohm}$.


Using voltage division we get:

$$v_1 = [4 / (4 + 8)] (30) = \underline{10 \text{ volts}}, v_2 = [8 / 12] (30) = \underline{20 \text{ volts}}$$

$$i_1 = v_1 / 12 = 10 / 12 = \underline{833.3 \text{ mA}}, i_2 = v_2 / 40 = 20 / 40 = \underline{500 \text{ mA}}$$

$$P_1 = v_1 i_1 = 10 \times 10 / 12 = \underline{8.333 \text{ watts}}, P_2 = v_2 i_2 = 20 \times 0.5 = \underline{10 \text{ watts}}$$

P.P.3.3

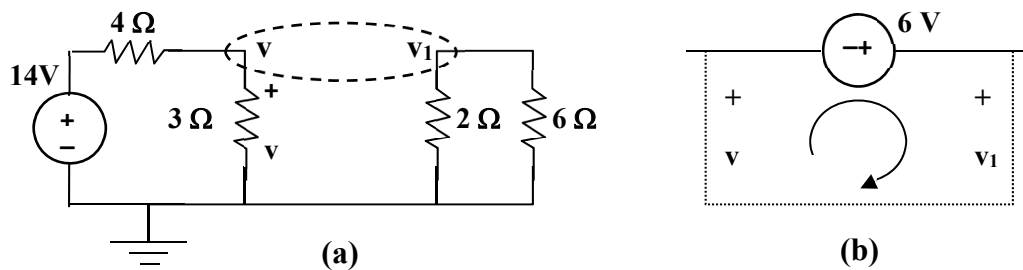

At the supernode in Fig. (a),

$$\frac{14 - v}{4} = \frac{v}{3} + \frac{v_1}{2} + \frac{v_1}{6}$$

$$\text{or } 42 = 7v + 8v_1 \quad (1)$$

Applying KVL to the loop in Fig. (b),

$$-v - 6 + v_1 = 0 \longrightarrow v_1 = v + 6 \quad (2)$$

Solving (1) and (2),

$$v = -400 \text{ mV}$$

$$v_1 = v + 6 = 5.6, i_1 = \frac{v_1}{2} = 2.8$$

$$i_1 = 2.8 \text{ A}$$

P.P.3.5 We apply KVL to the two loops and obtain

$$-45 + 2i_1 + 12(i_1 - i_2) + 4i_1 = 0 \text{ or}$$

$$-45 + 18i_1 - 12i_2 = 0 \text{ which leads to } 3i_1 - 2i_2 = 7.5 \quad (1)$$



$$12(i_2 - i_1) + 9i_2 + 30 + 3i_2 = 0 \text{ or}$$

$$30 + 24i_2 - 12i_1 = 0 \text{ which leads to } -3i_1 + 6i_2 = -7.5 \quad (2)$$

From (1) and (2) we get

$$i_1 = 2.5 \text{ A}, i_2 = 0 \text{ A}$$

P.P.3.7

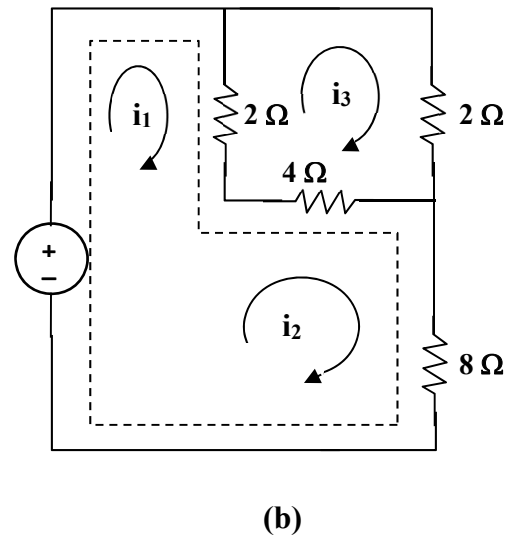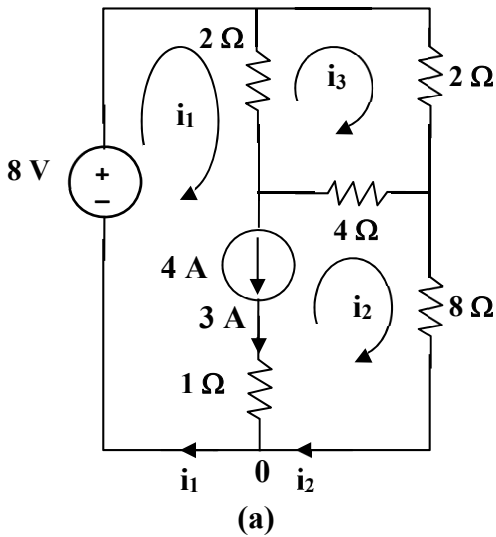

For the supermesh,

$$-8 + 2i_1 - 2i_3 + 12i_2 - 4i_3 = 0 \text{ or } i_1 + 6i_2 - 3i_3 = 4 \quad (1)$$

For mesh 3,

$$8i_3 - 2i_1 - 4i_2 = 0 \text{ or } -i_1 - 2i_2 + 4i_3 = 0 \quad (2)$$

At node 0 in Fig. (a),

$$i_1 = 4 + i_2 \longrightarrow i_1 - i_2 = 4$$

Solving (1) to (3) yields

$$i_1 = \mathbf{4.632 \text{ A}}, i_2 = \mathbf{631.6 \text{ mA}}, i_3 = \mathbf{1.4736 \text{ A}}$$

P.P.3.8 $G_{11} = 1/(1) + 1/(20) + 1/(5) = 1.25, G_{12} = -1/(5) = -0.2,$

$$G_{33} = 1/(4) + 1 = 1.25, G_{44} = 1/(1) + 1/(4) = 1.25,$$

$$G_{12} = -1/(5) = -0.2, G_{13} = -1, G_{14} = 0,$$

$$G_{21} = -0.2, G_{23} = 0 = G_{26},$$

$$G_{31} = -1, G_{32} = 0, G_{34} = -1/4 = -0.25,$$

$$G_{41} = 0, G_{42} = 0, G_{43} = 0.25,$$

$$i_1 = 0, i_2 = 3+2 = 5, i_3 = -3, i_4 = 2.$$

Hence,

$$\begin{bmatrix} \mathbf{1.25} & \mathbf{-0.2} & \mathbf{-1} & \mathbf{0} \\ \mathbf{-0.2} & \mathbf{0.2} & \mathbf{0} & \mathbf{0} \\ \mathbf{-1} & \mathbf{0} & \mathbf{1.25} & \mathbf{-0.25} \\ \mathbf{0} & \mathbf{0} & \mathbf{-0.25} & \mathbf{1.25} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{5} \\ \mathbf{-3} \\ \mathbf{2} \end{bmatrix}$$

P.P.3.9 $R_{11} = 50 + 20 + 80 = 150, R_{22} = 20 + 30 + 15 = 65,$

$$R_{33} = 30 + 20 = 50, R_{44} = 15 + 80 = 95,$$

$$R_{55} = 20 + 60 = 80, R_{12} = -20, R_{13} = 0, R_{14} = -80,$$

$$R_{15} = 0, R_{21} = -20, R_{23} = -30, R_{24} = -15, R_{25} = 0,$$

$$R_{31} = 0, R_{32} = -30, R_{34} = 0, R_{35} = -20,$$

$$R_{41} = -80, R_{42} = -15, R_{43} = 0, R_{45} = 0,$$


$$R_{51} = 0, R_{52} = 0, R_{53} = -20, R_{54} = 0,$$

$$v_1 = 30, v_2 = 0, v_3 = -12, v_4 = 20, v_5 = -20$$


Hence the mesh-current equations are

$$\begin{bmatrix} 150 & -20 & 0 & -80 & 0 \\ -20 & 65 & -30 & -15 & 0 \\ 0 & -30 & 50 & 0 & -20 \\ -80 & -15 & 0 & 95 & 0 \\ 0 & 0 & -20 & 0 & 80 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 30 \\ 0 \\ -12 \\ 20 \\ -20 \end{bmatrix}$$

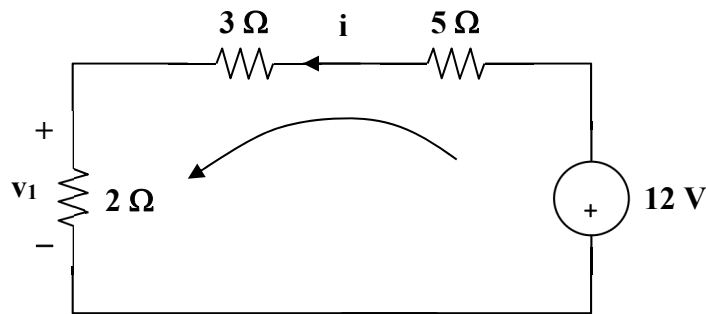P.P.4.3 Let $v_0 = v_1 + v_2$, where v_1 and v_2 are contributions to the 12-V and 5-A sources respectively.



(a)

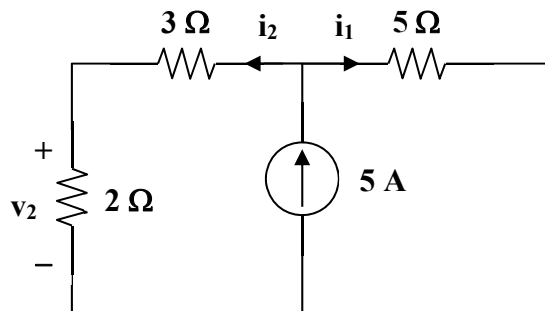

(b)

To get v_1 , consider the circuit in Fig. (a).

$$(2 + 3 + 5)i - 12 = 0 \text{ or } i = 12/(10) = 1.2 \text{ A}$$

$$v_1 = 2i = 2.4 \text{ V}$$

To get v_2 , consider the circuit in Fig. (b).


Since the resistors are equal ($5 = 2 + 3$) then the current divides equally and

$$i_1 = i_2 = 5/2 = 2.5 \text{ and } v_2 = 2i_2 = 5 \text{ V}$$

Thus, $v = v_1 + v_2 = 2.4 + 5 = \mathbf{7.4 \text{ V}}$

P.P.4.5 Let $i = i_1 + i_2 + i_3$

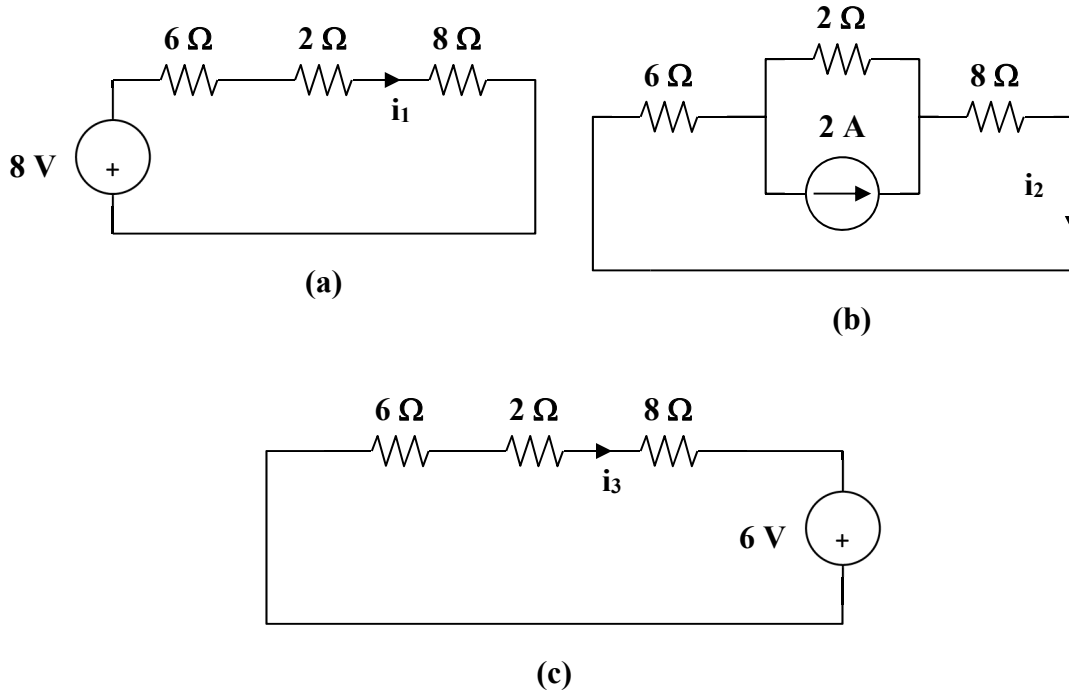where i_1 , i_2 , and i_3 are contributions due to the 8-V, 2-A, and 6-V sources respectively.




For i_1 , consider Fig. (a), $i_1 = \frac{8}{6+2+8} = 0.5 \text{ A}$

For i_2 , consider Fig. (b). By current division, $i_2 = \frac{2}{2+14}(2) = 0.25$


For i_3 , consider Fig. (c), $i_3 = \frac{-6}{16} = -0.375 \text{ A}$

Thus, $i = i_1 + i_2 + i_3 = 0.5 + 0.25 - 0.375 = \mathbf{375 \text{ mA}}$

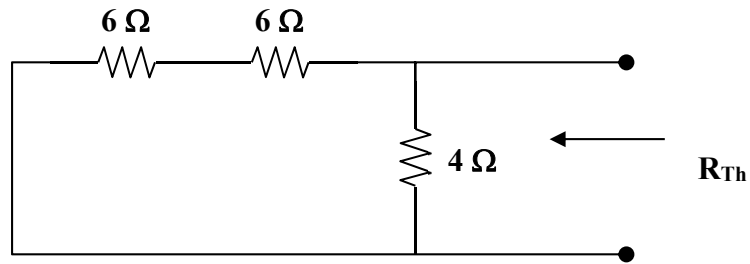.P.4.8 To find R_{Th} , consider the circuit in Fig. (a).




(a)

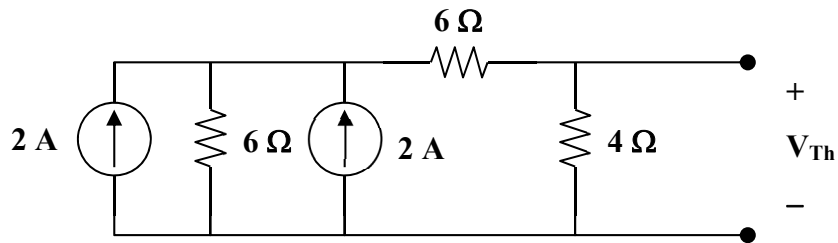

(b)

$$R_{Th} = (6 + 6) \parallel 4 = \frac{12 \times 4}{18} = 3 \Omega$$

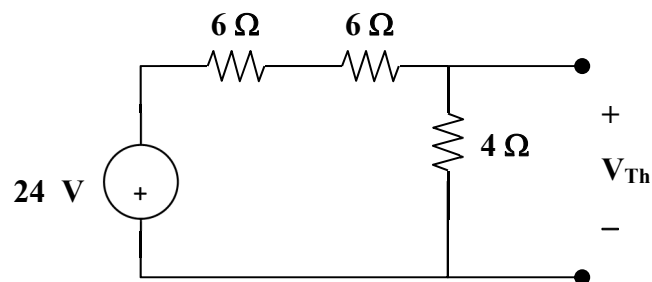To find V_{Th} , we use source transformations as shown in Fig. (b) and (c).




(c)

Using current division in Fig. (c),


$$V_{Th} = \frac{4}{4 + 12} (24) = 6 \text{ V}$$

$$i = \frac{V_{Th}}{R_{Th} + 1} = \frac{6}{3 + 1} = 1.5 \text{ A}$$

P.P.4.11

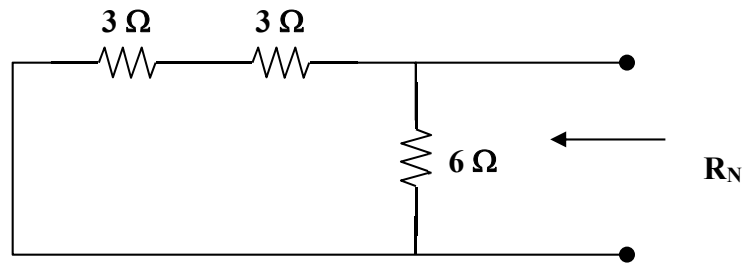


(a)

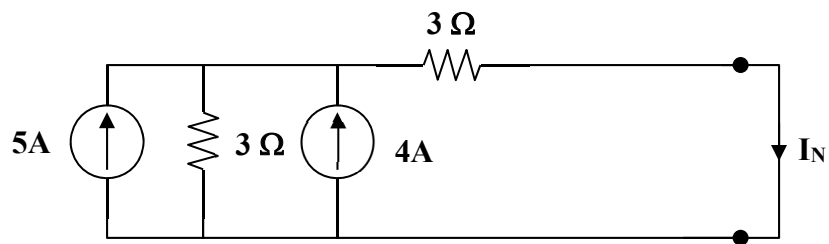


(b)

From Fig. (a), $R_N = (3 + 3) \parallel 6 = 3\ \Omega$

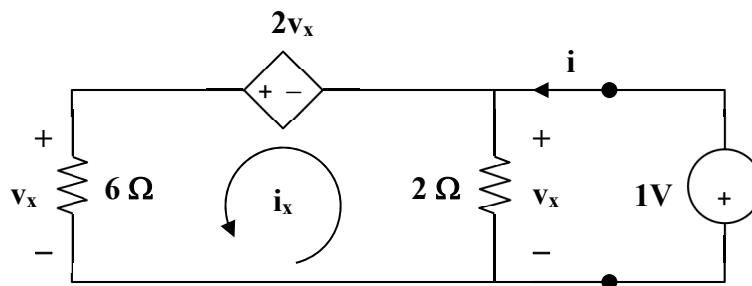From Fig. (b), $I_N = \frac{1}{2}(5 + 4) = 4.5\text{A}$




(a)

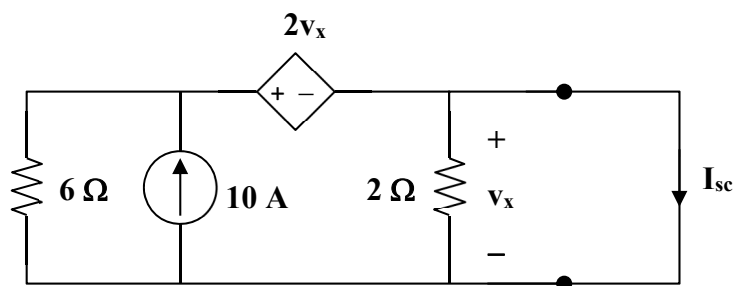

(b)

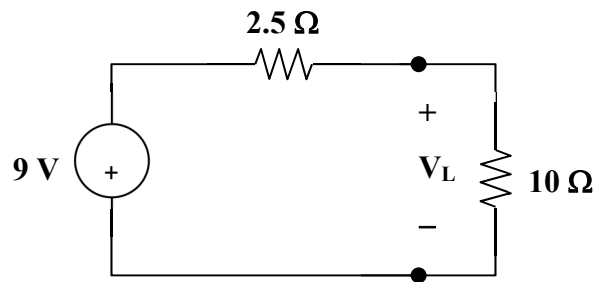P.P.4.16 $V_{Th} = 9V$, $R_{Th} = (v_{oc} - V_L) \frac{R_L}{V_L} = (9 - 1) \frac{20}{8} = 2.5\Omega$



$$V_L = \frac{10}{10 + 2.5}(9) = 7.2 \text{ V}$$