

EE2000 Logic Circuit Design

Chapter 7 – Latch and Flip-Flop Circuits

Outline

- 7.1 Latch
 - Active High
 - Active Low
- 7.2 Flip-Flop (FF)
 - SR-, D-, JK-, T- FFs
- 7.3 Master-Slave FF
- 7.4 Edge-Triggered FF
- 7.5 Synchronous and Asynchronous Inputs

Two classes of logic circuits

- Combinational logic circuit

Previous lectures have been discussed


- Sequential logic circuit

Output depends on present input + past history


Memory circuit (previous STATE information) is required

Sequential logic circuit


Examples

 

 Vending Machine
Food/ drink / MTR tickets



Digital counter / clock

 


Traffic light controller

7.1 Latch

- The output state of a *latch* is controlled by its excitation input signals
- *Latch* and *flip-flop* are memory devices and implemented using *bistable* circuit - its output will remain in either 0 or 1 state

■ The formal logic diagram and symbol

 

■ A binary storage device


- Q stores the **state** of the latch, or view as
- Storing the data (a binary value) in Q

Latch

- SR (reset-set) latch circuit

When S (set) is set to 1, the output Q will be set to 1. Likewise, when R (reset) is set to 1, the output Q will be set to 0. It is invalid to set both S and R to 1

- **Active High Latch**

 

NOR gate implementation


S	R	Next state of Q		State
		Q_{t+1}	Q'_{t+1}	
0	0	Q_t	Q'_t	Hold state
0	1	0	1	Reset state
1	0	1	0	Set state
1	1	0	0	Undefined state

Latch

- S'R' latch circuit

When S' (set) is set to 1, the output Q will be set to 0. Likewise, when R' (reset) is set to 1, the output Q will be set to 1. It is invalid to set both S' and R' to 1

- **Active Low Latch**

 


NAND gate implementation


S'	R'	Q_{t+1}	Q'_{t+1}	State
1	1	Q_t	Q'_t	Hold state
1	0	0	1	Reset state
0	1	1	0	Set state
0	0	1	1	Undefined state

Latch

 - Note that the input is active high for NOR gate implementation, whereas the input is active low for NAND gate implementation



Require a 1 signal to change its state

 

Require a 0 signal to change its state

Drawbacks

- If inputs S, R are unstable (or noise), output produces a unstable short pulse

Solution:

- Prevention of input noise
- Using “Gated Latch”
- The latches will enter undefined state for some inputs (e.g. $R = S = 1$)

Solution:

- Prevent R and S set to 1 simultaneously
- Using “D Latch”

7.2 Flip-Flop (FF)

- The state of flip-flop changes on the transition of the clock
- Four types of FF

SR FF

D-type FF


JK FF

T FF

Clocked SR FF

C can be presented by a clocked signal. Then the latch with the clocked signal is called Flip-flop

 - An additional control input C is introduced to act as an enable signal for the R , S inputs




C	S	R	State
0	x	x	Disable (Hold)
1	0	0	Hold state
1	0	1	Reset state
1	1	0	Set state
1	1	1	Undefined state

When $C = 0$, the two inputs to the SR latch are (0, 0), output Q will be unchanged (state change disabled)


When $C = 1$, the two inputs to the SR latch are (S , R), output Q will follow that of the SR latch (state change enabled)

Another Version

 

C	S'	R'	State
0	x	x	Disable (Hold)
1	1	1	Hold state
1	1	0	Reset state
1	0	1	Set state
1	0	0	Undefined state

 - The control input is also known as **enable input, gate**
- So this kind of latches are called **gated latches**




Logic symbol of gated SR latch


D-type FF

C can be presented by a clocked signal.

 Inputs **R** and **S** are correlated with **D** but differentiate by a NOT-gate



Symbol of gated **D** latch

 


- $S = D, R = D'$
- When $D = 0$,
 - $S = 0, R = 1$ (reset state)
- When $D = 1$,
 - $S = 1, R = 0$ (set state)
- No undefined state!

C	D	Q	Next state of Q
0	x	Q	Hold state
1	0	0 (= D)	Reset state
1	1	1 (= D)	Set state

Remember in this way:
The value of **D** is transferred to the **Q** output

JK FF

 
- The *JK* FF is a refinement of the *SR* FF in that the undetermined state of the *SR* type is defined in the *JK* type. Inputs *J* and *K* behave like inputs *S* and *R* to set and reset (clear) the FF, respectively. The input marked *J* is for *set* and the input marked *K* is *reset*.



J	K	clk=0	clk=1
		Q_{n+1}	Q_{n+1}
0	0	Q_n	Q_n
0	1	Q_n	0
1	0	Q_n	1
1	1	Q_n	\bar{Q}_n


T-type FF

 - The toggle (T) FF has a clock input which causes the output state changed for each clock pulse if T is in its active state. It is useful in counter design




clk	T	Q_{n+1}
0	X	Q_n
1	0	Q_n
1	1	$\overline{Q_n}$

 
Logic symbols of various latch and flip-flops




SR latch

 


SR flip-flop

 

D flip-flop

 

JK flip-flop

 


T flip-flop


7.3 Master-Slave Flip-Flop

- Master-Slave SR Flip-Flop



- Connect two gated SR latches like this

 

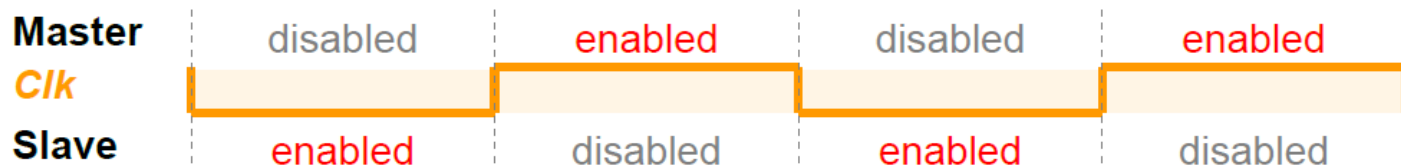
- The left clocked latch called **master**, the right is **slave**
- At any time, only one latch could be enabled



How Does It Work?

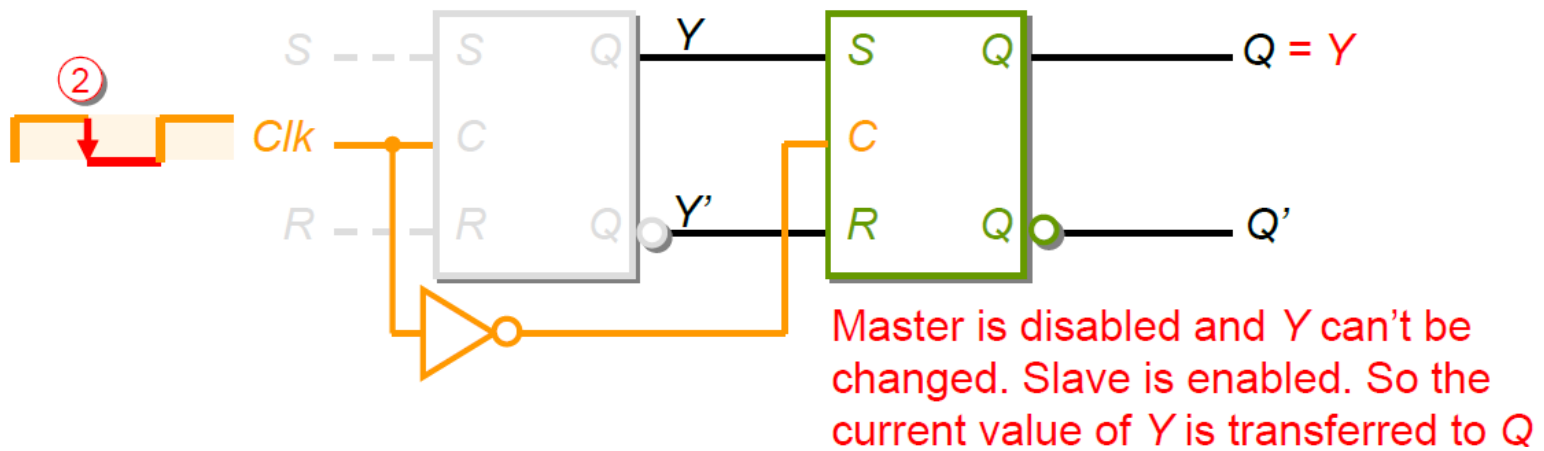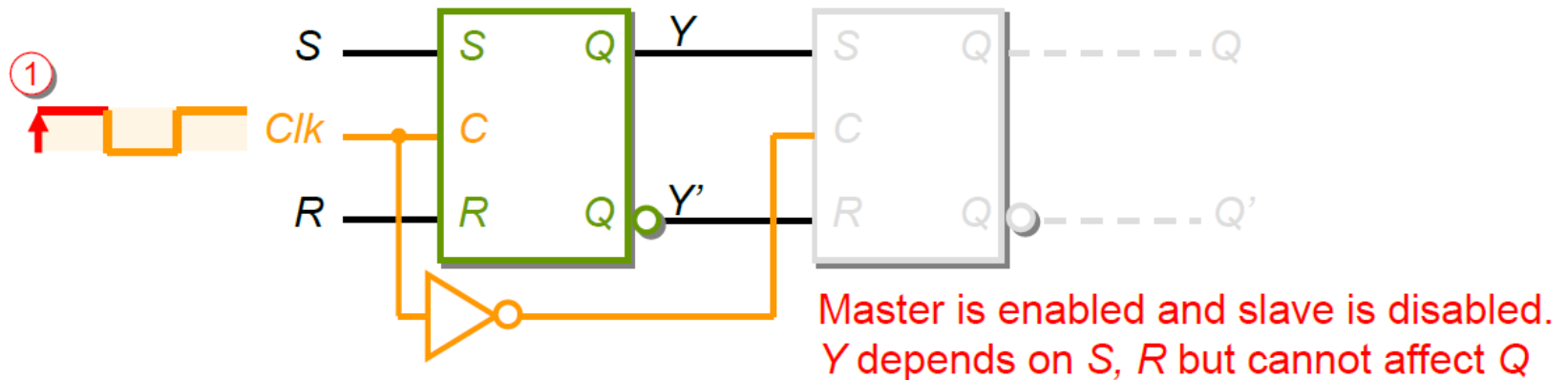

Timing Diagram of MS SR FF

 

1. Clk goes to 1, S affects the output of Y (master enabled)
2. Clk goes to 0, the output of Q is enabled (slave enabled)
3. Clk goes to 1 again
4. R goes to 1, Y is 0 (reset enabled)
5. The new Y is transferred to Q when Clk goes back to 0
6. Now Clk is 0 (master disabled), so any change in S , R can't affect Y
7. S goes to 1, and back to 0, Y set to 1 again
8. Q follows Y until Clk falls from 1 to 0

Pulse-Triggered FF

Its behavior depends on:





The rising and the period of the pulse remain at high (Y) and the falling edges (Q)

So referred to as **pulse-triggered flip-flops**

- When the clock pulse goes to 1
 - Master is enabled
 - Output Y is updated at this moment
- When the clock pulse remains at 1
 - Y will continue be changed if S and R change
- When the clock pulse goes to 0
 - Slave is enabled
 - Output Q is updated now
 - The state of the FF is changed (i.e. triggered)
- When the clock pulse remains at 0
 - Q remain unchanged as Y can't be changed


Behavior of the MS *SR* FF

The function table

<i>Inputs</i>			<i>Outputs</i>		
<i>S</i>	<i>R</i>	<i>Clk</i>	Next <i>Q</i>	Next <i>Q'</i>	Meaning
x	x	0	<i>Q</i>	<i>Q'</i>	Hold
0	0		<i>Q</i>	<i>Q'</i>	Hold
0	1		0	1	Reset
1	0		1	0	Set
1	1		?	?	Undefined

Master-Slave JK Flip-Flop

- Extension of master-slave SR flip-flop

 





- Want to eliminate the undefined state
 - $S = JQ'$, $R = KQ$

How to Operate?

- $S = JQ', R = KQ$
- 1) When $J = K = 0$
 - $S = 0, R = 0$ (Hold state)
- 2) When $J = 0, K = 1$
 - $S = 0, R = Q$
 - Hold state if Q is 0
 - Reset if Q is 1 (but Q will be 0 in next clock pulse)
 - Therefore, reset state
- 3) When $J = 1, K = 0$
 - $S = Q', R = 0$
 - Hold state if Q is 1
 - Set if Q is 0 (but Q will be 1 in next clock pulse)
 - Therefore, set state
- 4) When $J = 1, K = 1$
 - $S = Q', R = Q$
 - Reset if Q is 1 (next $Q = 0$)
 - Set if Q is 0 (next $Q = 1$)
 - Therefore, toggle the value of Q

Behavior of the MS *JK* FF

The function table



Inputs			Outputs		
<i>J</i>	<i>K</i>	<i>Clk</i>	Next <i>Q</i>	Next <i>Q'</i>	Meaning
x	x	0	<i>Q</i>	<i>Q'</i>	Hold
0	0		<i>Q</i>	<i>Q'</i>	Hold
0	1		0	1	Reset
1	0		1	0	Set
1	1		<i>Q'</i>	<i>Q</i>	Toggle

The same behaviors as
master-slave *SR* flip-flop

Eliminated the undefined state

Master-Slave *D* Flip-Flop

  - Extension of master-slave *SR* flip-flop





Symbol

- *D* stands for delay
 - $S = D, R = D'$ (Set *Q* if *D* is 1, reset *Q* if *D* is 0)
 - The output *Q* is just the input delayed *D* until the next active clock transition

Master-Slave T Flip-Flop

■ Extension of master-slave JK flip-flop

  


Symbol



■ $J = K = T$

- When $T = 0$, $J = K = 0$ (Hold)
- When $T = 1$, $J = K = 1$ (Toggle)

MS D FF & MS T FF

The function tables

Inputs		Outputs		
D	Clk	Next Q	Next Q'	Meaning
x	0	Q	Q'	Hold
x		D	D'	Set / Reset

Inputs		Outputs		
T	Clk	Next Q	Next Q'	Meaning
x	0	Q	Q'	Hold
0		Q	Q'	Hold
1		Q'	Q	Toggle

Problems

- For MSFF, master is enabled during the period of clock pulse is 1
- Undesired behavior produced when inputs values of S and R (or J , K , D , T) change at that period
- Better solution: **Edge-triggered flip-flops**

7.4 Edge-Triggered Flip-Flop

- Use one of the edges of the clock signal to read the input values
 - either positive or negative transition
 - **triggering edge**
- The response to the triggering edge at the output of the flip-flop is almost immediate
- The flip-flops remains unresponsive to the input change until the next triggering edge

Triggering Edge

- Triggered only during a signal transition from 0 to 1 (or from 1 to 0) on the **clock**

- Positive (rising, leading) edge-triggering: 0-to-1 transition





- Negative (falling, trailing) edge-triggering: 1-to-0 transition



- Additional circuit is included to ensure it will only response to the input at the transition edge of the clock pulse

Positive-Edge-Triggered D FF

 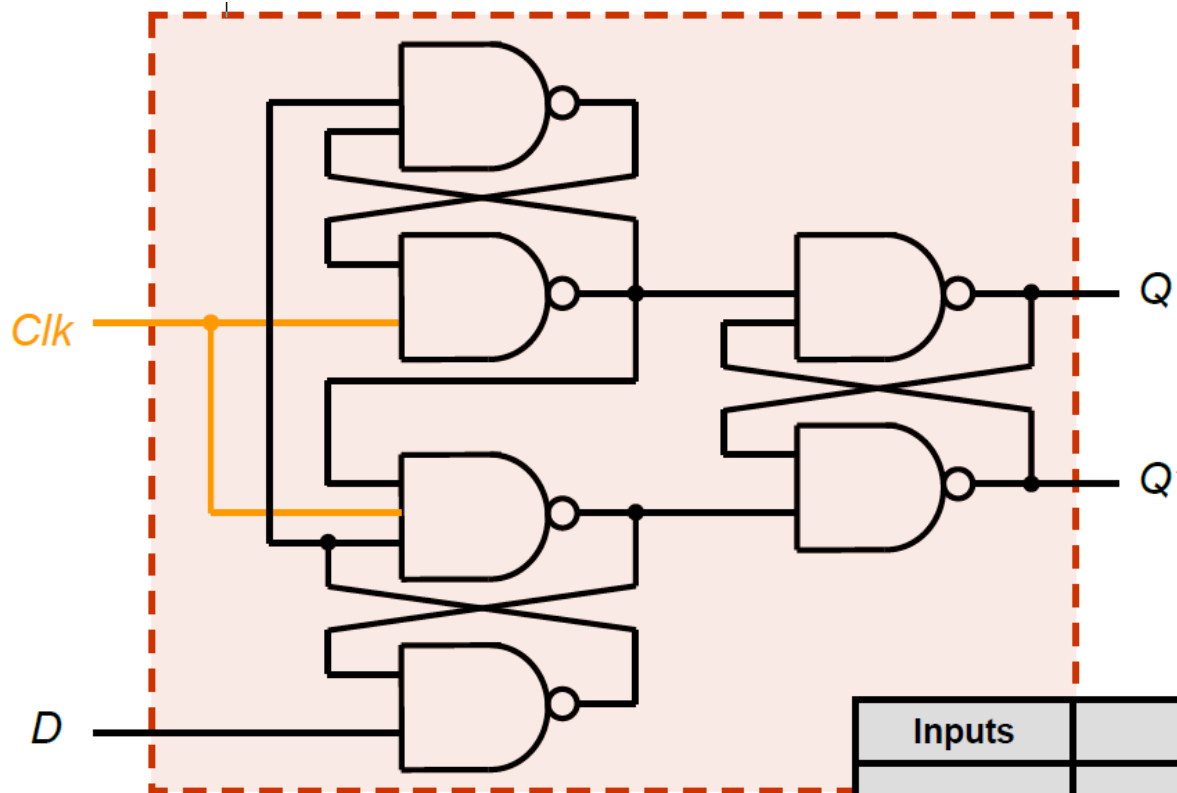


Remember the symbol instead of the configuration


Inputs		Outputs		
D	Clk	Next Q	Next Q'	State
x	$\downarrow, 0, 1$	Q	Q'	Hold
x	\uparrow	D	D'	Set / Reset

Timing Diagram


Timing Diagram of PET D FF

 

 Timing Diagram of PET D FF (if no output delay)




Negative-Edge-Triggered D FF

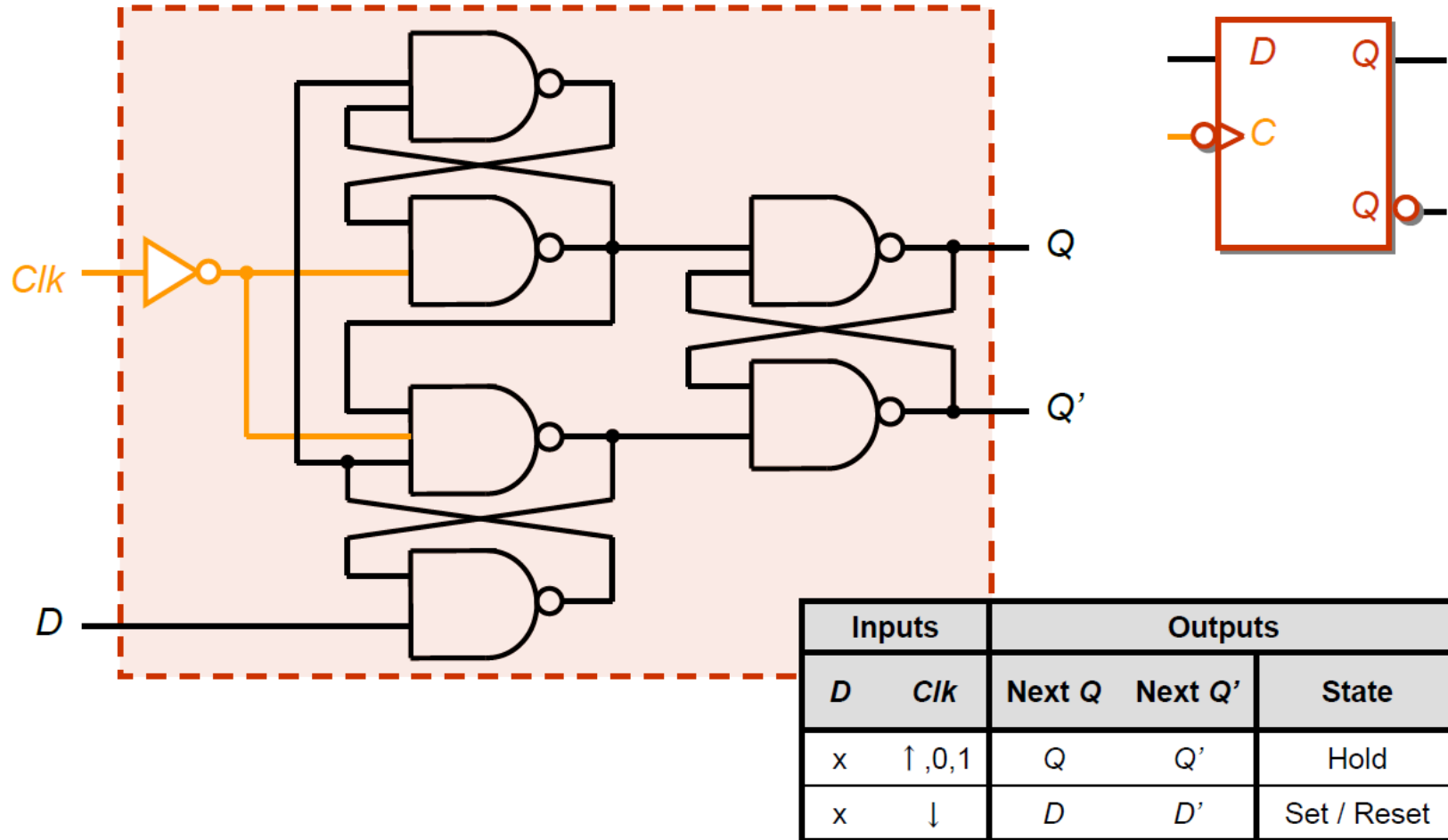


Timing Diagram



Timing Diagram of NET D FF

 

 Timing Diagram of NET D FF (if no output delay)



Edge-Triggered JK Flip-Flop

  


Inputs			Outputs		
J	K	Clk	Next Q	Next Q'	State
x	x	$\downarrow, 0, 1$	Q	Q'	Hold
0	0	\uparrow	Q	Q'	Hold
0	1	\uparrow	0	1	Reset
1	0	\uparrow	1	0	Set
1	1	\uparrow	Q'	Q	Toggle

Edge-Triggered T Flip- Flop

■ Assign $J = K = T$

 
- When $T = 0$ ($J = 0$ and $K = 0$), hold state
- When $T = 1$ ($J = 1$ and $K = 1$), toggle state
- Remove the reset and set state




Inputs		Outputs		
T	Clk	Next Q	Next Q'	State
x	$\downarrow, 0, 1$	Q	Q'	Hold
0	\uparrow	Q	Q'	Hold
1	\uparrow	Q'	Q	Toggle

Timing Diagram

 
Timing Diagram of PET JK FF (if no output delay)



 
Timing Diagram of PET T FF (if no output delay)



 
Logic symbols of various **edge-triggered** flip-flops




SR flip-flop

 

D flip-flop

 

JK flip-flop

 

T flip-flop

7.5 Synchronous and Asynchronous Inputs

- Inputs of flip-flops are categorized into two types
- **Synchronous** and **asynchronous**
- All inputs to FFs presented so far are synchronous inputs

Asynchronous Inputs

- The output will response to the sync. inputs only if all async. inputs are inactive
- Particularly useful for bringing a FF into a desired initial state prior to normal clocked operation
- The asynchronous (or direct) inputs usually called
 - **Preset** (denoted by *PRE*) and **clear** (denoted *CLR*)
 - Used to forcibly set and reset the state of flip-flop


Example

The corresponding function table

Inputs				Outputs		
PRE'	CLR'	Clk	D	Next Q	Next Q'	Meaning
0	1	x	x	1	0	Preset
1	0	x	x	0	1	Clear
0	0	x	x	1*	1*	Undefined
1	1	\uparrow	x	D	D'	Set / Reset
1	1	$\downarrow, 0, 1$	x	Q	Q'	Hold

*Unpredictable behavior will result if both PRE' and CLR' set to 1 simultaneously

} The same behaviors as D flip-flops

 


The logic symbol

Example

The function table of an negative-edge-triggered *JK* flip-flop with asynchronous preset and clear inputs

Inputs					Outputs		
<i>PRE'</i>	<i>CLR'</i>	<i>Clk</i>	<i>J</i>	<i>K</i>	Next <i>Q</i>	Next <i>Q'</i>	Meaning
L	H	x	x	x	H	L	Preset
H	L	x	x	x	L	H	Clear
L	L	x	x	x	H*	H*	Undefined
H	H	↓	L	L	<i>Q</i>	<i>Q'</i>	Hold
H	H	↓	H	L	H	L	Set
H	H	↓	L	H	L	H	Reset
H	H	↓	H	H	<i>Q'</i>	<i>Q</i>	Toggle
H	H	↑,0,1	x	x	<i>Q</i>	<i>Q'</i>	Hold


The logic symbol

 

The same behaviors as *JK* flip-flops

Timing Diagram

 Timing Diagram of PET T FF with asynchronous preset and clear inputs
(if no output delay)



Summary

- Flip-flops as memory elements
 - To store the value in Q
 - One FF can store 1-bit data
- Different types of FFs
 - SR -type, D -type, JK -type, T -type
 - By controlling the inputs (S , R , D , J , K , T) to change, set, reset or hold the value of Q
- Different Triggering Methods
 - Pulse-triggered
 - Edge-triggered