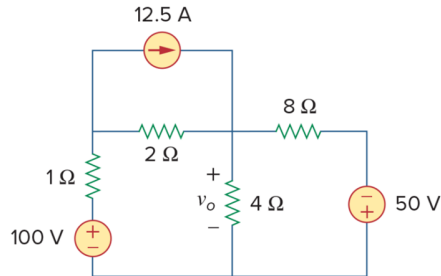



## EE1002      Tutorial 5

(Questions from the Textbook by Alexander & Sadiku, 7<sup>th</sup> edition Problems 3.14, 3.15, & 3.38)


1. Using nodal analysis, find  $v_o$  in the following circuit:



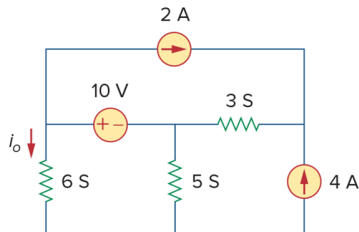2. Apply nodal analysis to find  $i_o$  and the power dissipated in each resistor in the circuit of the following figure (the unit of S is called Seimens, which is the reciprocal of the unit  $\Omega$ , e.g.,  $0.5\text{S} = 2\Omega$ ):



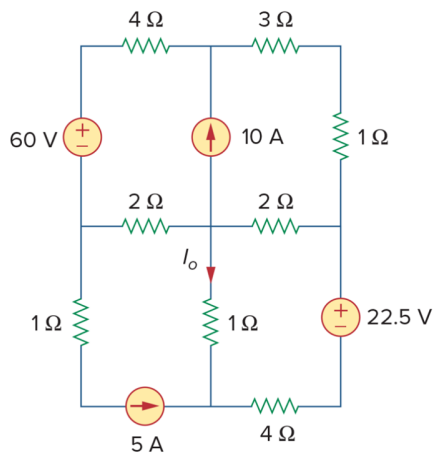3. Apply mesh analysis to the following circuit and obtain  $I_o$ .



Answers:

1.  $v_o = 50\text{ V}$ .
2.  $i_o = 29.45\text{ A}$ ;  $P_{6\text{S}} = 144.6\text{ W}$ ;  $P_{5\text{S}} = 129.6\text{ W}$ ; and  $P_{3\text{S}} = 12\text{ W}$ .
3.  $I_o = -6.375\text{ A}$ .