

Practice Problem 9.7

Find the voltage $v(t)$ in a circuit described by the integrodifferential equation

$$2 \frac{dv}{dt} + 5v + 10 \int v dt = 50 \cos(5t - 30^\circ)$$

using the phasor approach.

Answer: $v(t) = 5.3 \cos(5t - 88^\circ) \text{ V}$.

Practice Problem 9.8

If voltage $v = 10 \cos(100t + 30^\circ) \text{ V}$ is applied to a $50 \mu\text{F}$ capacitor, calculate the current through the capacitor.

Answer: $50 \cos(100t + 120^\circ) \text{ mA}$.

Practice Problem 9.9

Refer to Fig. 9.17. Determine $v(t)$ and $i(t)$.

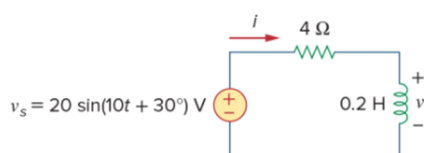


Figure 9.17

For Practice Prob. 9.9.

Answer: $8.944 \sin(10t + 93.43^\circ) \text{ V}$, $4.472 \sin(10t + 3.43^\circ) \text{ A}$.

Practice Problem 9.10

Determine the input impedance of the circuit in Fig. 9.24 at $\omega = 10 \text{ rad/s}$

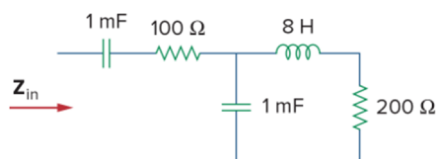


Figure 9.24

For Practice Prob. 9.10.

Answer: $(149.52 - j195) \Omega$.

Practice Problem 9.11

Calculate v_o in the circuit of Fig. 9.27.

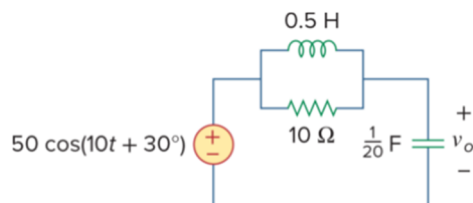


Figure 9.27


For Practice Prob. 9.11.

Answer: $v_o(t) = 35.36 \cos(10t - 105^\circ) \text{ V}$.

Note: Practice Problem 9.13 needs the knowledge of V_{rms} , which will be taught in Week 11.

Practice Problem 9.13

Design an RC circuit to provide a 90° lagging phase shift of the output voltage relative to the input voltage. If an ac voltage of 60 V rms is applied, what is the output voltage?

Answer:  Figure 9.34 shows a typical design; 20 V rms.

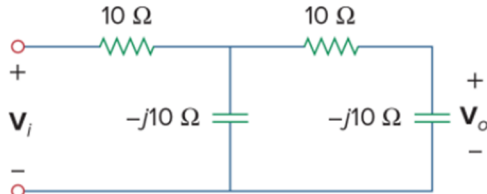



Figure 9.34

For  Practice Prob. 9.13.

Practice Problem 9.14

Refer to the RL circuit in  Fig. 9.36. If 10 V is applied to the input, find the magnitude and the phase shift produced at 5 kHz. Specify whether the phase shift is leading or lagging.

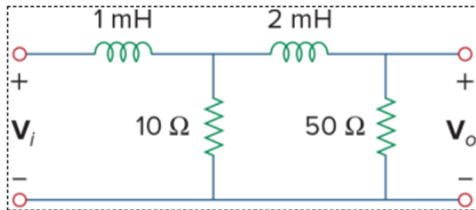


Figure 9.36

For  Practice Prob. 9.14.

Answer: 1.7161 V, 120.39° , lagging.