

EE1002 Principles of Electronic Engineering Test 1

Part I: Multiple choice (15 questions, 3 points per question, total 45 minutes)

1. If $z = \frac{a+4j}{2-3j}$ is a real number, where $a \in \mathbb{R}$, find a .

Answer: $a = -8/3$

2. If $z = \left(\frac{1+j}{1-j}\right)^4$, find z .

Answer: 1

3. If $y = \sqrt{3 - \cos^2 x}$, then find the derivative of y .

Answer: $\frac{\cos x \sin x}{\sqrt{3 - \cos^2 x}}$

4. If $\sin(x) + \cos(x) = \frac{1}{5}$ $\left(-\frac{\pi}{4} \leq x < 0\right)$, find $z = \cos^2(x)$.

Answer: 16/25

5. If $\sin(\alpha) + \sin(\beta) = 1$, $\cos(\alpha) - \cos(\beta) = \frac{1}{2}$, find $\cos(\alpha + \beta)$

Answer: 3/8

6. Evaluate $\int (1 - \sin^2 \frac{x}{2}) dx$

Answer: $\frac{1}{2}(x + \sin x) + c$

7. Evaluate $\int \frac{x}{x^4 - 1} dx$



[Hint: $\frac{1}{y^2 - 1} = \frac{1}{2} \left(\frac{1}{y-1} - \frac{1}{y+1} \right)$]

Answer: $\frac{1}{4} \ln \left| \frac{x^2 - 1}{x^2 + 1} \right| + c$

8. Find the general solution of $\frac{d^2 y}{dx^2} + \frac{dy}{dx} - 12y = 0$


Answer: $y = Ae^{-4x} + Be^{3x}$

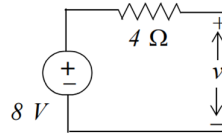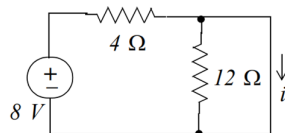9. For the following circuits, find the value of the current i and the value of the voltage v .




Answer: $i = 2 \text{ A}, v = 8 \text{ V}$.

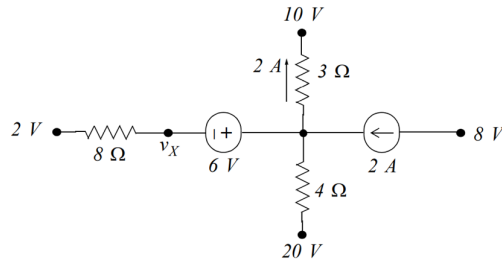10. Find the node voltage v_x of the following circuit.




Answer: 10 V

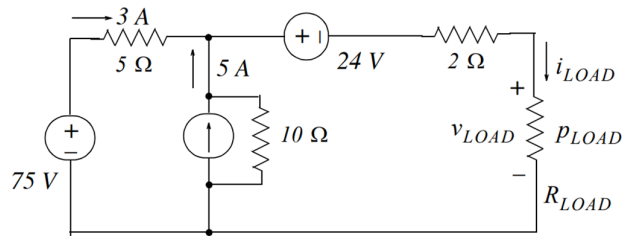11. In the following circuit, R_{LOAD} is the load. Find the current i_{LOAD} , voltage v_{LOAD} , and power p_{LOAD} of R_{LOAD} .




Answer: $i_{LOAD} = 8\text{ A}$, $v_{LOAD} = 20\text{ V}$, $p_{LOAD} = 160\text{ W}$.

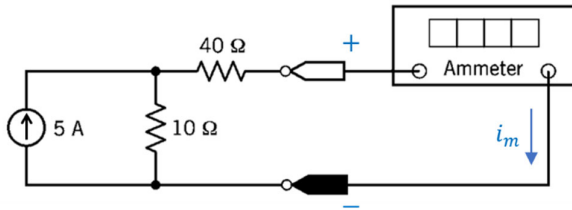12. Determine the current i_m measured by the actual ammeter (**Not ideal**) in the following circuit.




Answer: $i_m < 1\text{ A}$

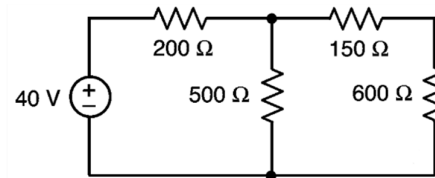13. Find the equivalent resistance seen by the source and the power supplied by the source.




Answer: $R_{eq} = 500\text{ }\Omega$, $P = 3.2\text{ W}$.

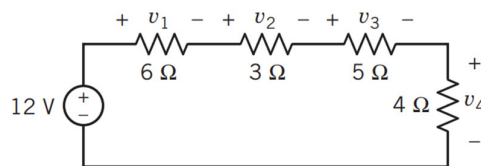14. Determine the voltages v_1 , v_2 , v_3 , and v_4 in the following circuit.



Answer: $v_1 = 4\text{ V}$, $v_2 = 2\text{ V}$, $v_3 = \frac{10}{3}\text{ V}$, $v_4 = \frac{8}{3}\text{ V}$.

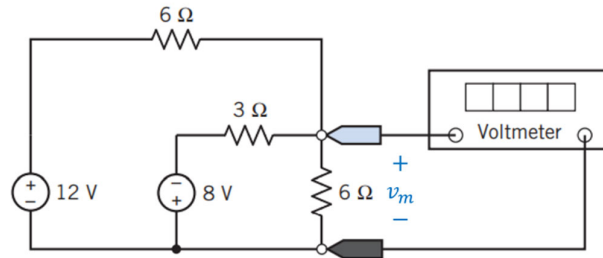15. Determine the value of the voltage measured by the ideal voltmeter v_m .



Answer: $v_m = -1\text{ V}$

Part II: Written Questions (2 questions, 25 points per question, total 40 minutes and 6 minutes per question)

Question 1

(a) Find the derivative of y .

$$y = \frac{1}{2} \ln(e^{\cos 4x} + 1)$$

(b) Evaluate the following integrals.

1) $\int \frac{\ln(\tan x)}{\cos x \sin x} dx$

2) $\int \frac{1+\ln x}{(x \ln x)^2} dx$

Answer:

a) $\frac{-2 \sin(4x) e^{\cos 4x}}{e^{\cos 4x} + 1}$

b)

1) $\frac{1}{2} (\ln \tan x)^2 + C$

$$\begin{aligned} \int \frac{\ln \tan x}{\cos x \sin x} dx &= \int \frac{\ln \tan x}{\cos^2 x \tan x} dx = \int \frac{\ln \tan x}{\tan x} \sec^2 x dx = \int \frac{\ln \tan x}{\tan x} d(\tan x) \\ &= \int \ln \tan x d(\ln \tan x) = \frac{1}{2} (\ln \tan x)^2 + C \end{aligned}$$

2) $-\frac{1}{x \ln x} + C$

$$\int \frac{1+\ln x}{(x \ln x)^2} dx = \int \frac{1}{(x \ln x)^2} d(x \ln x) = -\frac{1}{x \ln x} + C$$

(c) Find the general solution of the equation by using the integrating factor method:

$$x^2 \frac{dy}{dx} - y = \frac{x^2}{(1 - e^x) e^{\frac{1}{x}}}$$

Answer:

$$y = e^{-1/x} (-\ln|e^{-x} - 1| + C)$$

$$\therefore \frac{dy}{dx} - \frac{y}{x^2} = \frac{1}{(1 - e^x)e^{\frac{1}{x}}}$$

$$\therefore p(x) = -\frac{1}{x^2}, Q(x) = \frac{1}{(1 - e^x)e^{\frac{1}{x}}}$$

$$IF = e^{P(x)}, \text{ where } P(x) = \int p(x) dx = \int -\frac{1}{x^2} dx = \frac{1}{x}$$

$$\therefore IF = e^{\frac{1}{x}}$$

Multiplying both sides of the original equation by the integration factor gives:

$$e^{\frac{1}{x}} \frac{dy}{dx} - e^{\frac{1}{x}} \frac{y}{x^2} = e^{\frac{1}{x}} \cdot \frac{1}{(1 - e^x)e^{\frac{1}{x}}} = \frac{1}{1 - e^x}$$


$$\therefore ye^{\frac{1}{x}} = \int \frac{dx}{1 - e^x} = \int \frac{e^{-x} dx}{e^{-x} - 1} = - \int \frac{1}{e^{-x} - 1} d(e^{-x}) = - \int \frac{1}{e^{-x} - 1} d(e^{-x} - 1)$$

$$\therefore ye^{\frac{1}{x}} = -\ln|e^{-x} - 1| + C$$


$$\therefore y = e^{-1/x} (-\ln|e^{-x} - 1| + C)$$

Question 2

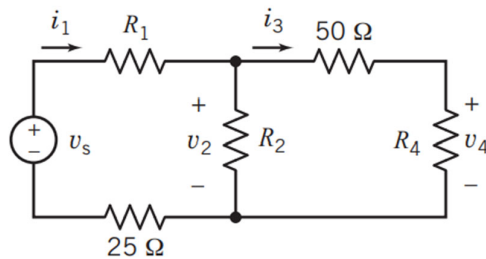- (a) Consider the following circuit. Given $v_2 = \frac{1}{3}v_s$, $i_3 = \frac{1}{5}i_1$, and $v_4 = \frac{3}{8}v_2$, determine the values of R_1 , R_2 , and R_4 .



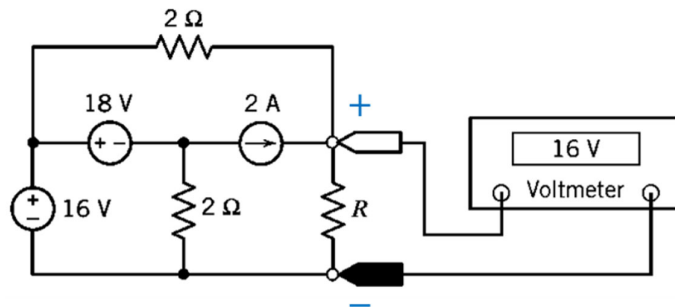- (b) Consider the circuit shown in the following figure (Ideal Voltmeter). Find the value of the resistance R .



Answer:

a) $R_1 = 7 \Omega, R_2 = 20 \Omega, R_4 = 30 \Omega$

Based on Voltage dividing method:

$$v_2 = \frac{1}{3} v_s \rightarrow (50 \Omega + R_4) \parallel R_2 = \frac{R_2 + 25 \Omega}{2}$$

$$v_4 = \frac{3}{8} v_2 \rightarrow \frac{R_4}{R_4 + 50 \Omega} = \frac{3}{8} \rightarrow R_4 = 30 \Omega$$


Based on the current dividing method:

$$i_3 = \frac{1}{5} i_1 \rightarrow \frac{R_2}{R_4 + 50 \Omega} = \frac{1}{4} \rightarrow R_2 = 20 \Omega$$

Then

$$R_1 = 7 \Omega$$

b) 8Ω

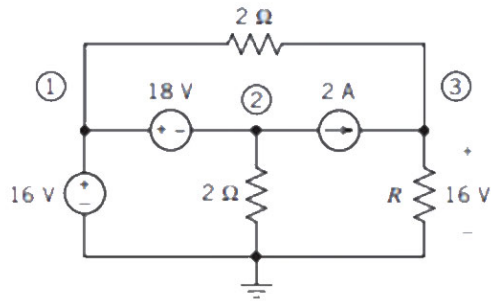

Apply KVL,

$$16 = v_1 - 0 \rightarrow v_1 = 16 V$$

$$18 = v_1 - v_2 \rightarrow 18 = 16 - v_2 \rightarrow v_2 = -2 V$$

$$v_3 = 16 V$$

Apply KCL at node 3

$$\frac{v_1 - v_3}{2} + 2 = \frac{v_3}{R}$$

Then

$$R = 8 \Omega$$