

# EE2000 Logic Circuit Design

---

## Chapter 2 – Minimization of Logic Functions

# Outline

- 2.1 Minimization using Boolean algebra
- 2.2 Karnaugh map
- 2.3 Minimization using Karnaugh map
- 2.4 Boolean functions with Don't'-care cases
- 2.5 Minimization using Quine-McCluskey method

# Advantages of minimization

- Obtain a simple (or simplest) logic circuit
- Reduce the cost of circuit

Cost in logic circuit

- **Gate** cost (number of gates in the implementation)
- **Gate-input** cost (number of inputs to the gates)
- Total cost = **Gate** cost + **Gate-input** cost

# Gate-input cost

- The number of gate-input is proportional to the number of transistors in the logic circuit
- The cost can be determined by checking logic diagram / schematic and the Boolean function

$$F_1 = abcd + a'b'c'd'$$

$$F_2 = (a' + b)(b' + c)(c' + d)(d' + a)$$

$F_1$  has 3 no. of gate and 10 no. of gate-input

Total cost = 13

$F_2$  has 5 no. of gate and 12 no. of gate-input

Total cost = 17

# Cost Reduce

The key of simplifying logic functions is to reduce the **no. of terms** and **no. of literals**

↓ no. of literals = ↓ no. of gate inputs  
↓ no. of terms = ↓ no. of gates

In addition, costs in space and power consumption can be reduced.

## 2.1 Minimization using Boolean algebra

- e.g. Given 4 equivalent Boolean functions  $f_1$  to  $f_4$  expressed in SOP form already (to be proved in next chapter).

- $f_1(a,b,c) = a'bc' + a'bc + ab'c' + ab'c + abc$  (5 product terms, 15 literals)
- $f_2(a,b,c) = a'b + ab' + abc$  (3 product terms, 7 literals)
- $f_3(a,b,c) = a'b + ab' + ac$  (3 product terms, 6 literals)
- $f_4(a,b,c) = a'b + ab' + bc$  (3 product terms, 6 literals)
- Both  $f_3$  &  $f_4$  are the minima

- How can you simplify  $f_1$  (the canonical sum form) to  $f_3$  (the MSP form)?

# Simplification

$$\blacksquare f_1(a,b,c) = a'bc' + a'bc + ab'c' + ab'c + abc$$

$$\blacksquare = (a'bc' + a'bc) + (ab'c' + ab'c) + abc$$

$$\blacksquare = a'b + ab' + abc = f_2$$

$$\blacksquare = a'b + a(b' + bc)$$


$$\blacksquare = a'b + a(b' + c)$$

$$\blacksquare = a'b + ab' + ac$$

$$\blacksquare = f_3$$

How to obtain  $f_4$  ?

# Simplification

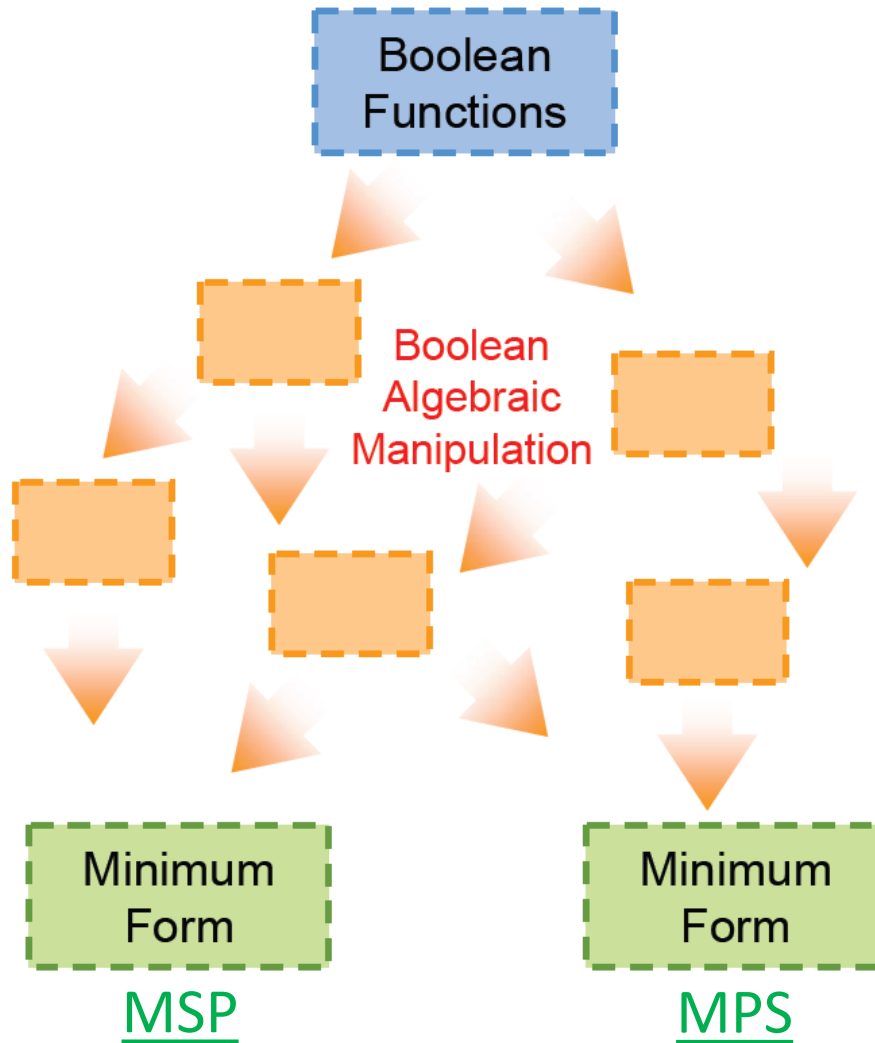

Properties of Boolean algebra:

Absorption  
Redundancy  
DeMorgan  
Consensus  
etc...



## 2.2 Karnaugh Map


- In 1953, Maurice Karnaugh introduced a map method known as **Karnaugh map (K-map)**
  - A straightforward procedure for minimizing Boolean functions in a table form
  - Graphical representation of a truth table
  - Minterm is used in the cell of the K-map
  - It is  $n$ -variable function (defined by  $2^n$ ):
    - Two-variable K-map has 4 cells
    - Three-variable K-map has 8 cells
    - Four-variable K-map has 16 cells

# Two-variable K-map

Variables are labeled on the upper left corner of the map



This column represents  $a = 1$

This row represents  $b = 1$

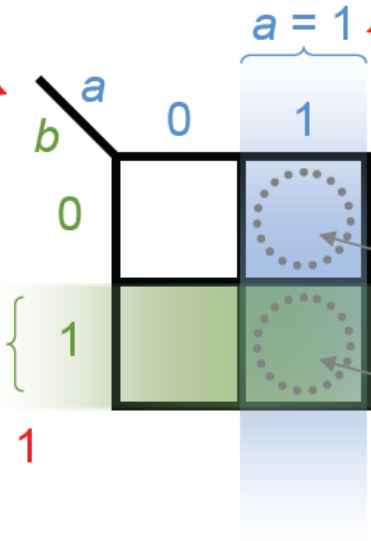

This cell means ( $a = 1$  AND  $b = 0$ )

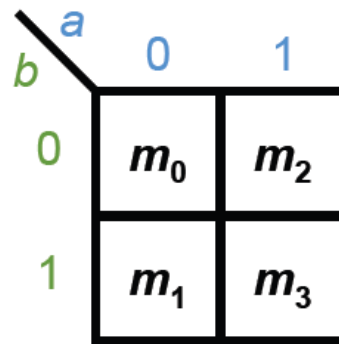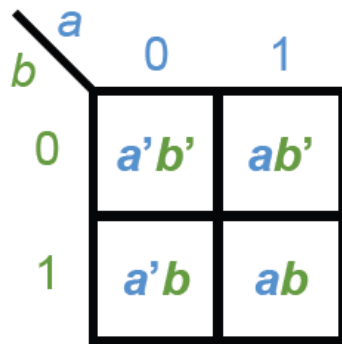This cell means ( $a = 1$  AND  $b = 1$ )



Minterm representations

# Plotting functions in K-map

$f(a, b) = \sum m(0, 3)$  Canonical form (contains Minterm)

$a \backslash b$	0	1
0		
1		

or

$a \backslash b$	0	1
0	1	
1		1

Put a 0 or leave blank for those minterms not included in the function

Put a 1 in the corresponding cells

$f(a, b) = a'b' + ab'$  Function must be formed by Minterm)


$a \backslash b$	0	1
0	1	1
1	0	0

or

$a \backslash b$	0	1
0	1	1
1		


Functions represented graphically with corresponding minterm cells labeled to value 1

# Three-variable K-map

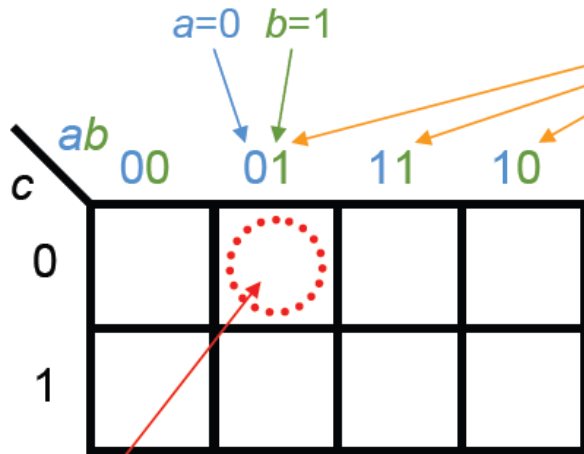

Note: the columns are not in numerical order, but Gray code order (why?)

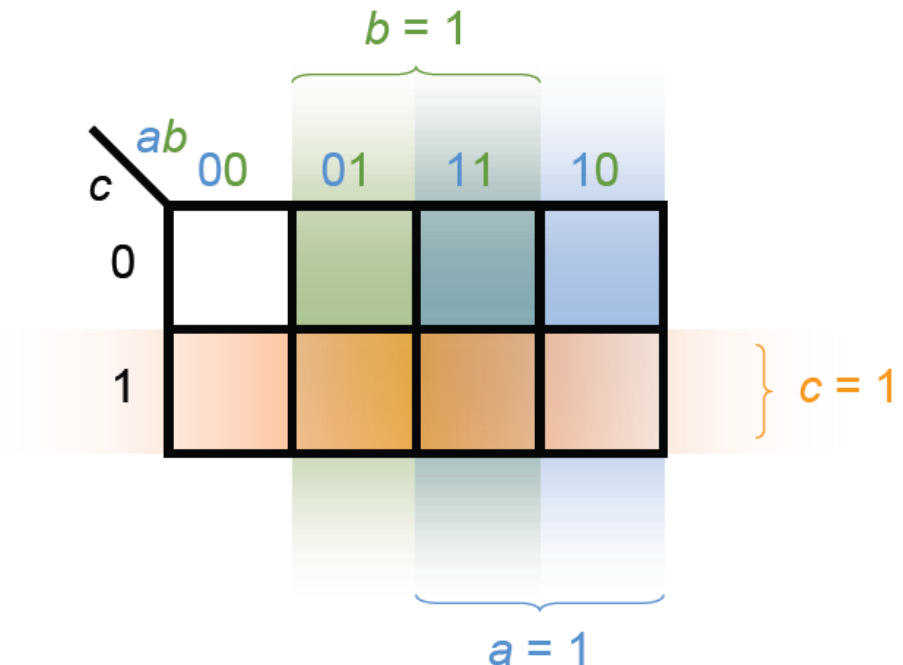This cell means:  
( $a = 0$  AND  $b = 1$  AND  $c = 0$ )



# Minterm representations

$c \backslash ab$		00	01	11	10
0	$a'b'c'$	$a'bc'$	$abc'$	$ab'c'$	
1	$a'b'c$	$a'bc$	$abc$	$ab'c$	

$c \backslash ab$		00	01	11	10
0	$m_0$	$m_2$	$m_6$	$m_4$	
1	$m_1$	$m_3$	$m_7$	$m_5$	

# Gray code in K-map

- Adjacent cells have 1-bit (1-variable) difference only
  - e.g. 00, 01, 10, 11 (two-variable)
  - $ab$  &  $ab'$  have 1-variable difference only!
- Any two adjacent cells sharing a common edge can form a pair of adjacent binary combinations
- This property can be used to simplify the product terms
- By this rule, we can group adjacent 1's on the map to form simplified product terms

# Simplification of Product Terms

Example: Simplify  $f(a, b, c) = \sum m(6, 7)$

c \ ab	00	01	11	10
	0	1	1	0
0			1	
1			1	

This group contains both 0 and 1 for  $c$  (i.e. no longer depends on  $c$ , depends on  $a$  and  $b$  only)

Using Boolean Algebra:


$$f(a, b, c) = abc' + abc$$

$$= ab \text{ (adjacency)}$$

Only one-variable difference

- Rule: whenever we group two adjacent cells, they can form a product term with one less variable

# Wrap-around Adjacency

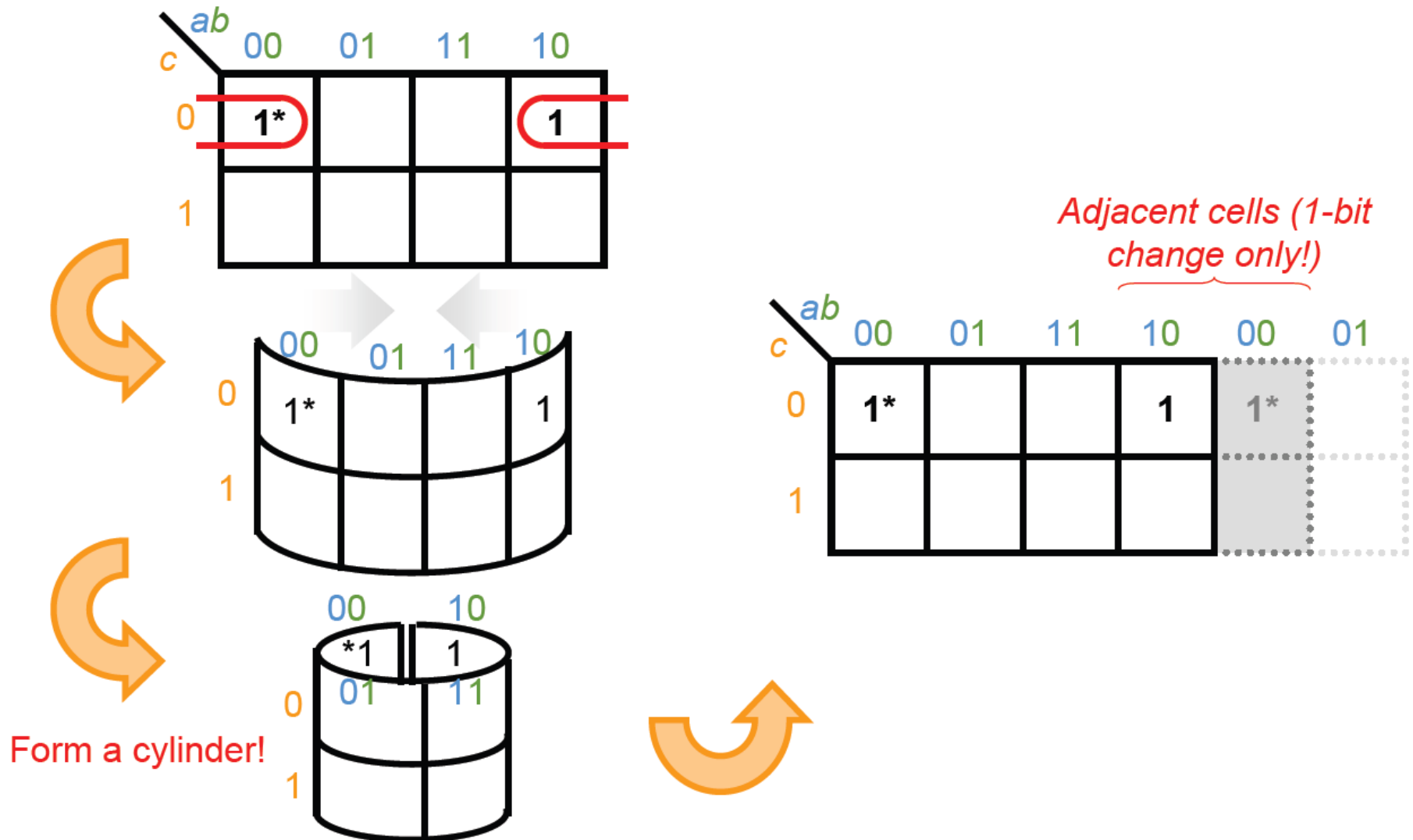



# More examples

$c \backslash ab$		00	01	11	10
0				1	1
1					

$$f(a, b, c) = abc' + ab'c'$$

$$= ac' \text{ (adjacency)}$$

We can even group adjacent 1's across the edges:

$c \backslash ab$		00	01	11	10
0	1				1
1					

$$f(a, b, c) = a'b'c' + ab'c'$$

$$= b'c' \text{ (adjacency)}$$

Also one-variable difference!

# If We Don't Use Gray Code...

We can group these two adjacent 1's:

		<i>ab</i>			
<i>c</i>		00	01	11	10
0			1	1	
1					

$$\begin{aligned} f(a, b, c) &= a'bc' + abc' \\ &= bc' \end{aligned}$$

But not these two: *Incorrect arrangement*

		<i>ab</i>			
<i>c</i>		00	01	10	11
0			1	1	
1					

$$\begin{aligned} f(a, b, c) &= a'bc' + ab'c' \\ &= c'(a'b + ab') \end{aligned}$$

two-variable difference!

Cannot be simplified into a single term!

# Format of three-variable

Label rows with first variable,  
columns with the others

<i>a</i>	<i>bc</i>			
	00	01	11	10
0	$m_0$	$m_1$	$m_3$	$m_2$
1	$m_4$	$m_5$	$m_7$	$m_6$

Vertical orientation of  
three-variable K-map

<i>bc</i>	<i>a</i>	
	0	1
00	$m_0$	$m_4$
01	$m_1$	$m_5$
11	$m_3$	$m_7$
10	$m_2$	$m_6$

Although there are different ways  
drawing the K-Maps, we use the same  
method to group the adjacent 1's!

# Four-variable K-map

Diagram illustrating the four-variable K-map with Gray code order and wrap-around adjacency highlighted.

Row labels (cd): 00, 01, 11, 10 (Gray code order).  
 Column labels (ab): 00, 01, 11, 10 (Gray code order).

Cells contain minterms (a, b, c, d):

00	01	11	10
$a'b'c'd'$	$a'bc'd'$	$abc'd'$	$ab'c'd'$
$a'b'cd$	$a'bcd$	$abcd$	$ab'cd$
$a'b'cd'$	$a'bcd'$	$abcd'$	$ab'cd'$

Annotations:

- $b = 1$  (Green bracket over columns 01 and 11)
- $a = 1$  (Blue bracket under columns 11 and 10)
- $c = 1$  (Orange bracket on the right side of rows 11 and 10)
- $d = 1$  (Pink bracket on the left side of rows 01 and 11)

Diagram illustrating the four-variable K-map with minterm indices.



00	01	11	10
$m_0$	$m_4$	$m_{12}$	$m_8$
$m_1$	$m_5$	$m_{13}$	$m_9$
$m_3$	$m_7$	$m_{15}$	$m_{11}$
$m_2$	$m_6$	$m_{14}$	$m_{10}$

## Wrap-around Adjacency


Note the Gray code order of the rows and columns

Diagram illustrating the four-variable K-map with minterm indices.

00	01	11	10
$m_0$	$m_4$	$m_{12}$	$m_8$
$m_1$	$m_5$	$m_{13}$	$m_9$
$m_3$	$m_7$	$m_{15}$	$m_{11}$
$m_2$	$m_6$	$m_{14}$	$m_{10}$

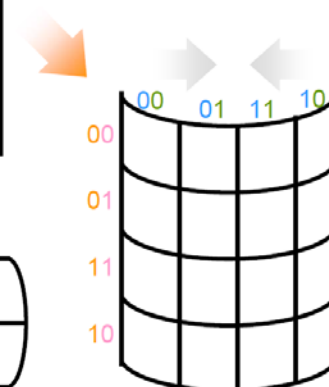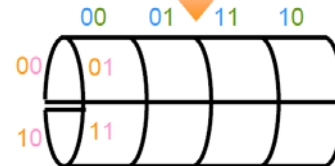

Adjacent cells

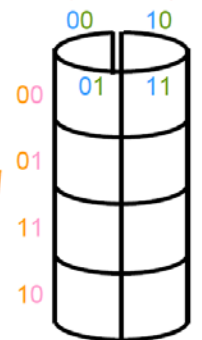


Form a cylinder!

# Imagine the Map as...


1-bit (1-variable) change only for every adjacent cells!

		$ab$							
		00	01	11	10	00	01	11	10
$cd$	00	$m_0$	$m_4$	$m_{12}$	$m_8$	$m_0$	$m_4$	...	
	01	$m_1$	$m_5$	$m_{13}$	$m_9$	$m_1$	$m_5$		
	11	$m_3$	$m_7$	$m_{15}$	$m_{11}$	$m_3$	$m_7$		
	10	$m_2$	$m_6$	$m_{14}$	$m_{10}$	$m_2$	$m_6$		
		$m_0$	$m_4$	$m_{12}$	$m_8$	$m_0$	$m_4$		
		$m_1$	$m_5$	$m_{13}$	$m_9$	$m_1$	$m_5$		
		...						...	


# Examples of 4-variable K-map

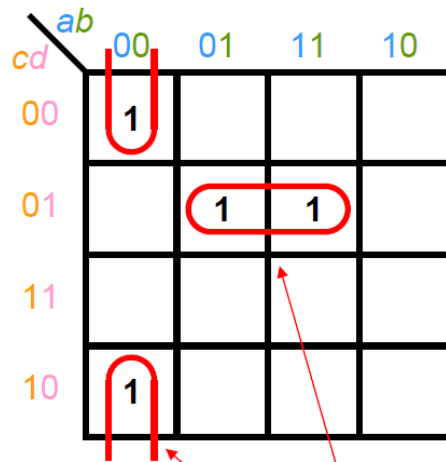

$$f(a, b, c, d) = a'b'd' + bc'd$$

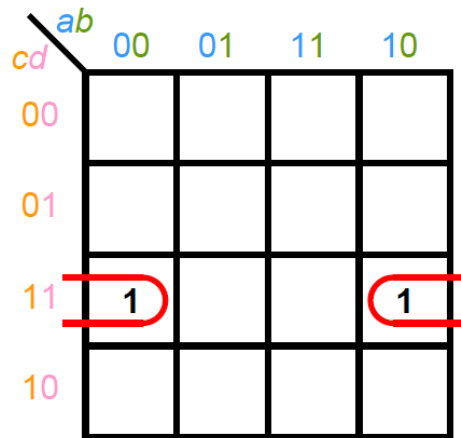


$$f(a, b, c, d) =$$

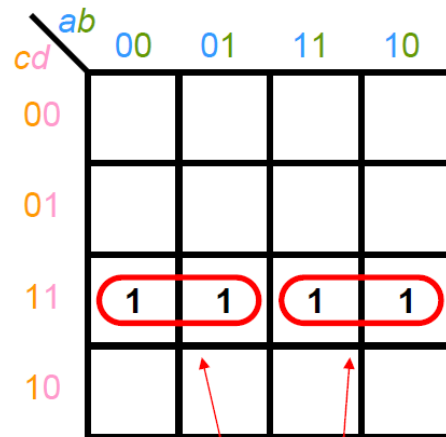


$$f(a, b, c, d) = a'cd + acd$$

$$= cd$$

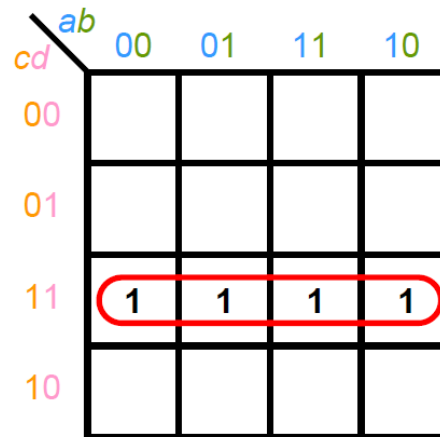


$$f(a, b, c, d) = cd$$

# Examples of 4-variable K-map

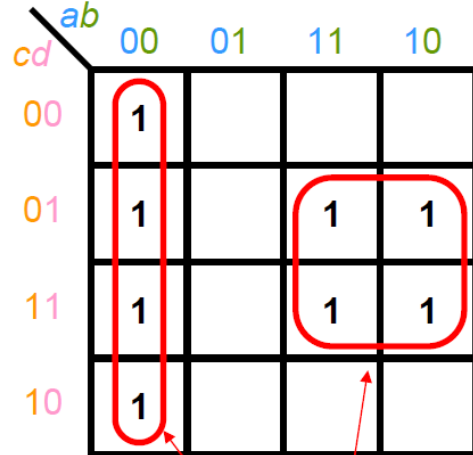


$$f(a, b, c, d) = a'b' + ad$$

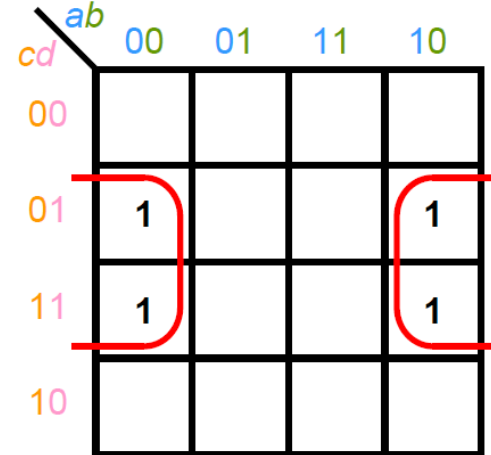


$$f(a, b, c, d) =$$

Across 4 corners:

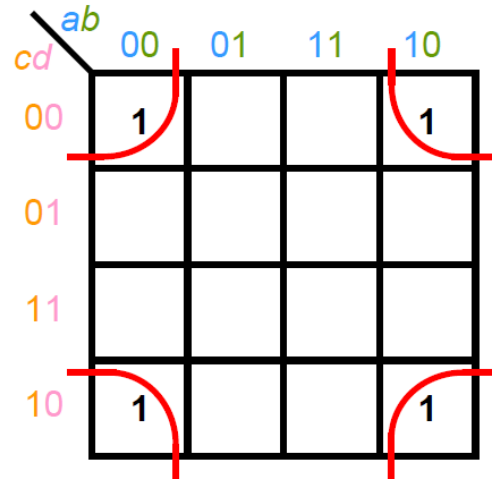


$$f(a, b, c, d) =$$

Group of eight:

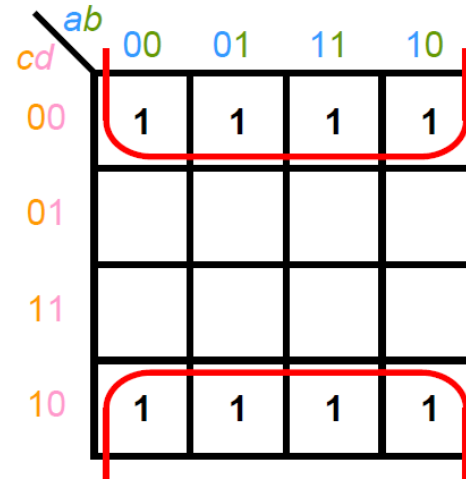


$$f(a, b, c, d) =$$

# Are They Adjacent Cells?

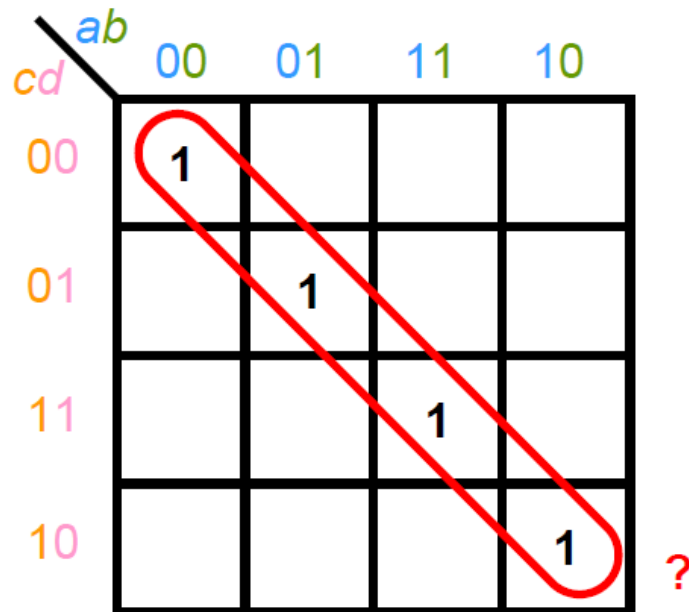


Diagonal?

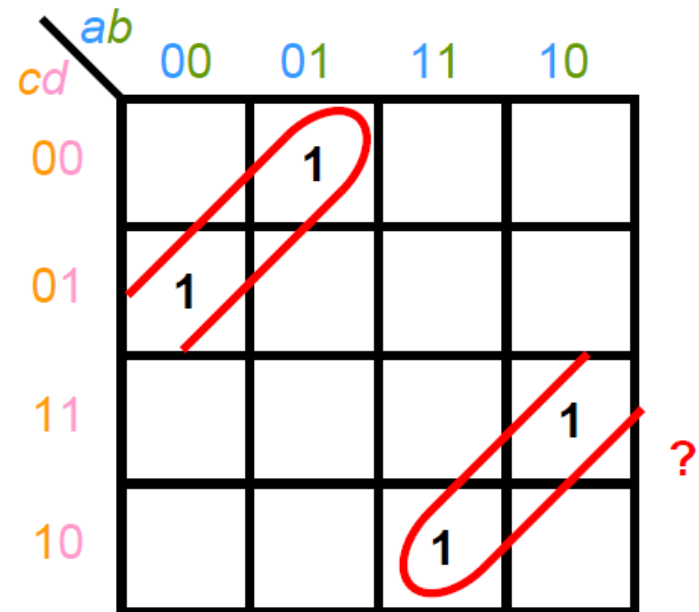


Magic square?



# Summary for K-map method

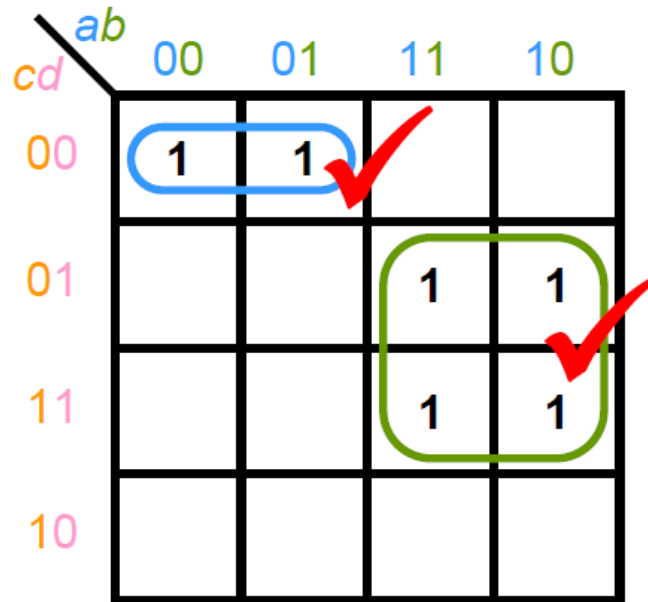

Group size is power of 2 (e.g. 2, 4, 8)

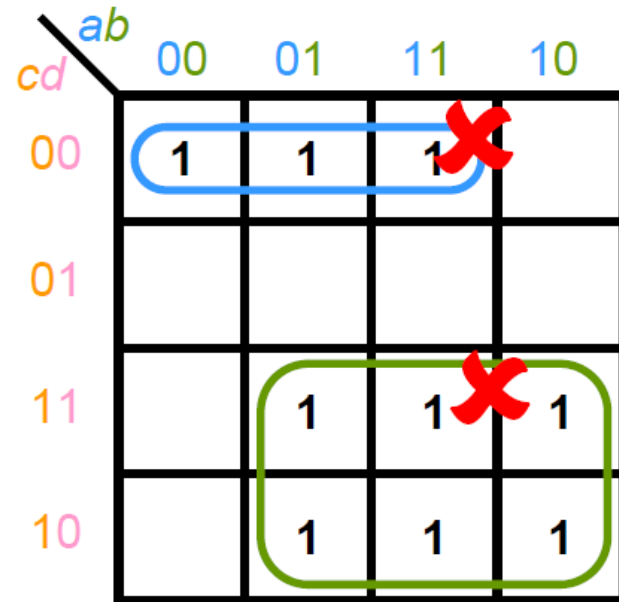

Other group size is illegal

## ■ Limitations

- The Boolean functions minimized by K-map are always in SOP or POS form
- Can handle minimization for two-level circuits, but not three or more levels





## 2.3 Minimization using Karnaugh map

- Group the adjacent cells (the number of cells must be a power of 2)
- Rules
  - (1) To find the fewest group that covers all cells with marked of 1s
  - (2) The groups should be as large as possible
- Goal
  - Reduce the number of products (terms) to minimum
  - Save the cost
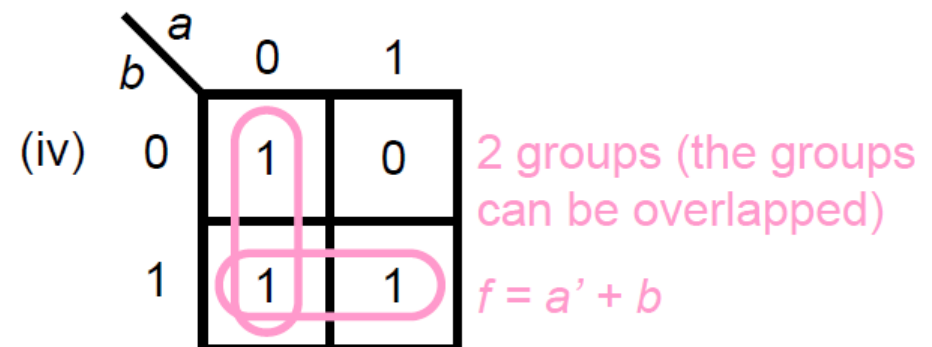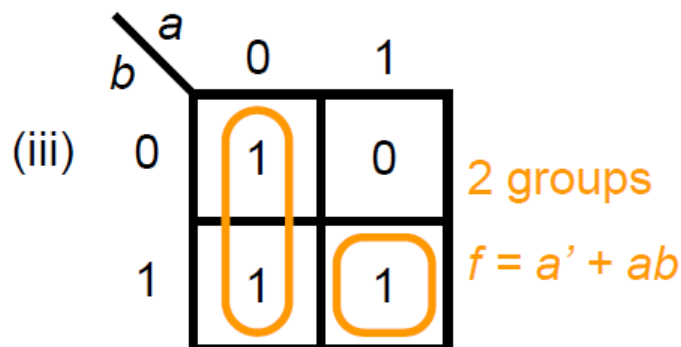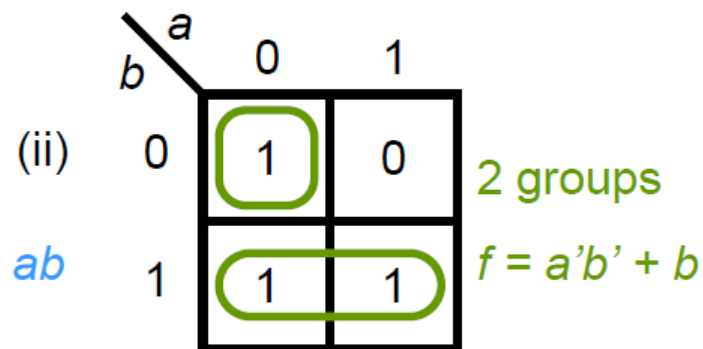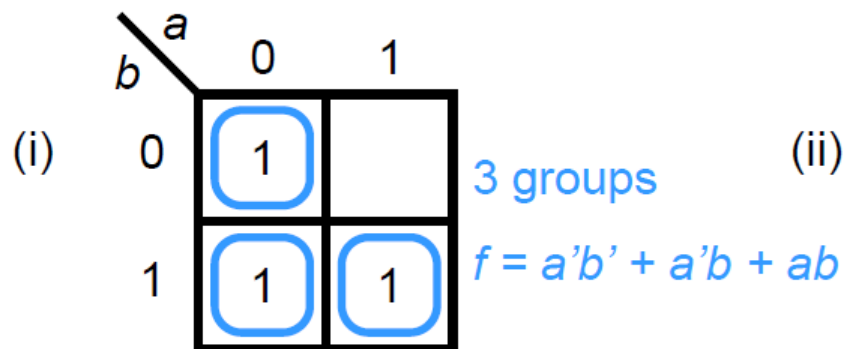
# Example: Two-variable K-map

Simplify  $f(a, b) = \Sigma m(0, 1, 3)$



*Many ways to group them. Which is the best solution?*



# Example: Three-variable K-map

Simplify  $f(a, b, c) = \sum m(0, 1, 2, 3, 4, 5)$

*Which solution is better?*

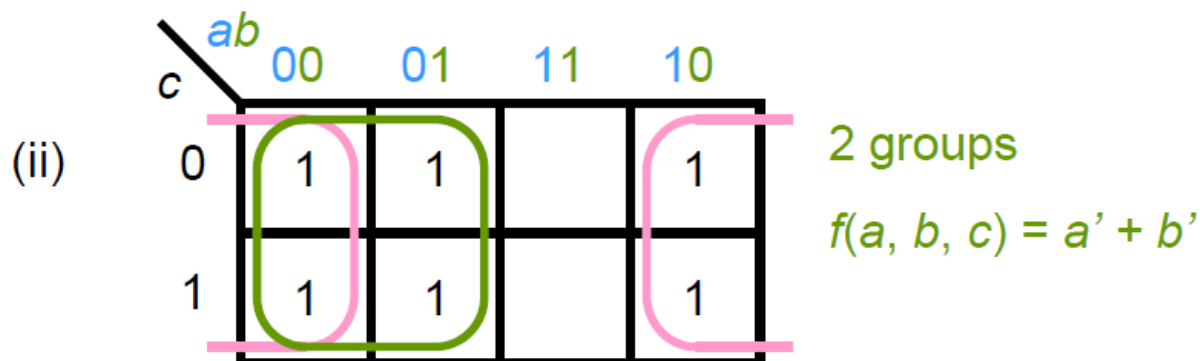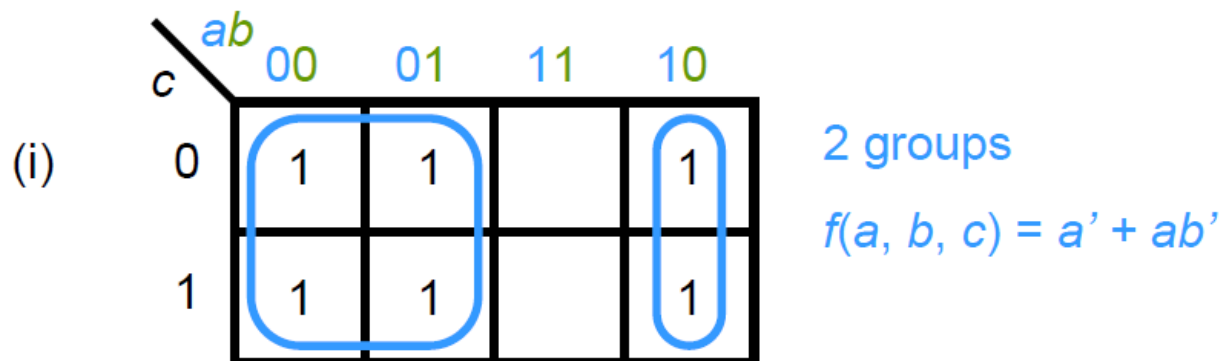


# Example: Four-variable K-map


Simplify  $f(a, b, c, d) = \sum m(0, 1, 2, 3, 4, 5, 7, 8, 10, 11, 15)$

$ab$		00	01	11	10
$cd$	00	1	1		1
	01	1	1		
	11	1	1	1	1
	10	1			1

# Grouping of K-map

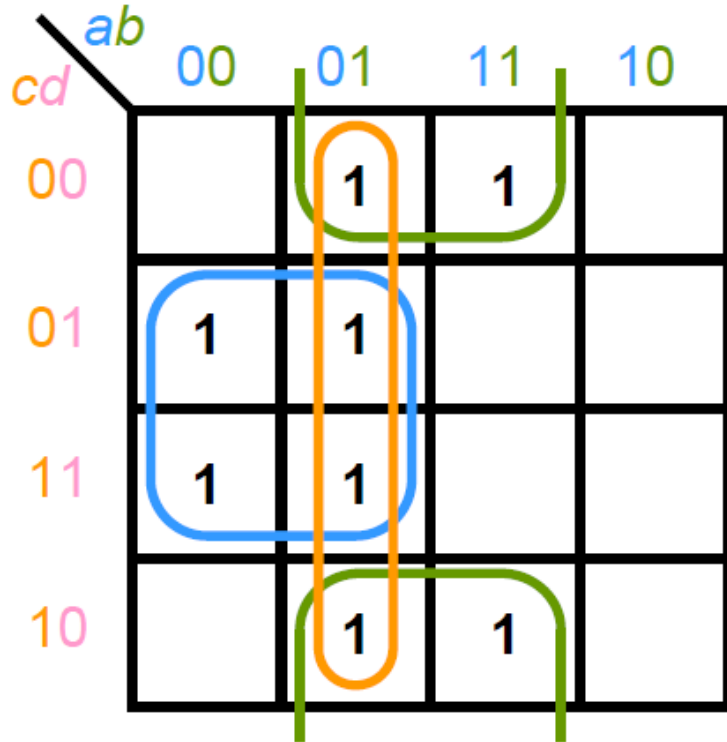


Three groups overlapped!

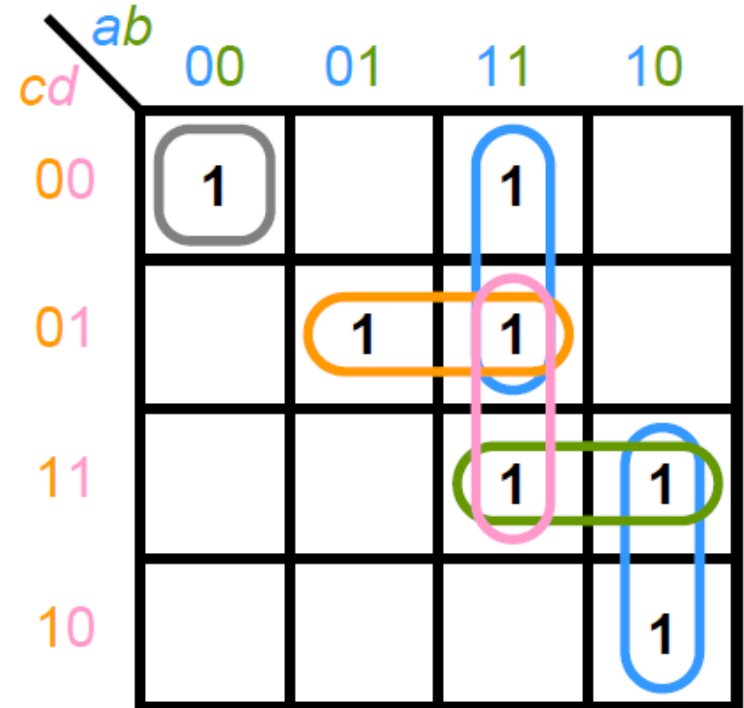

Too many overlaps!

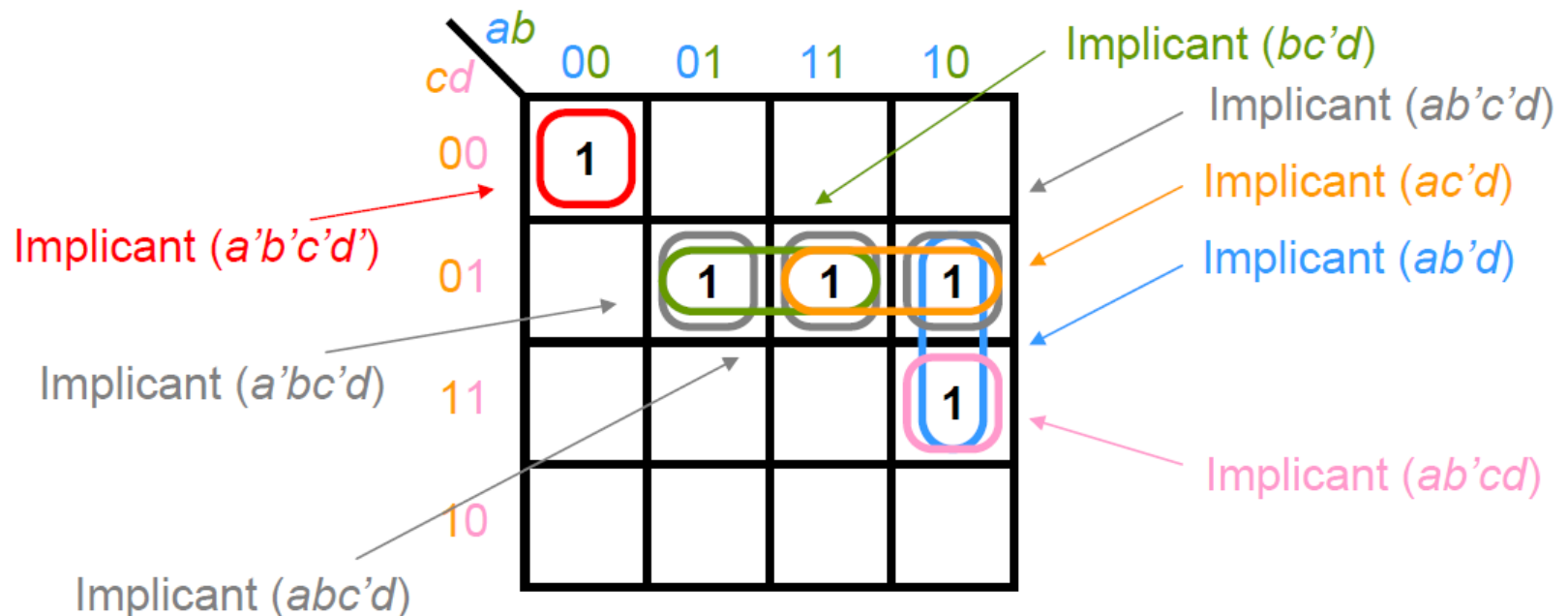
# Terminology: Implicant

- The product term is an **implicant** of a function if the function has the value 1 for all minterms of the product term


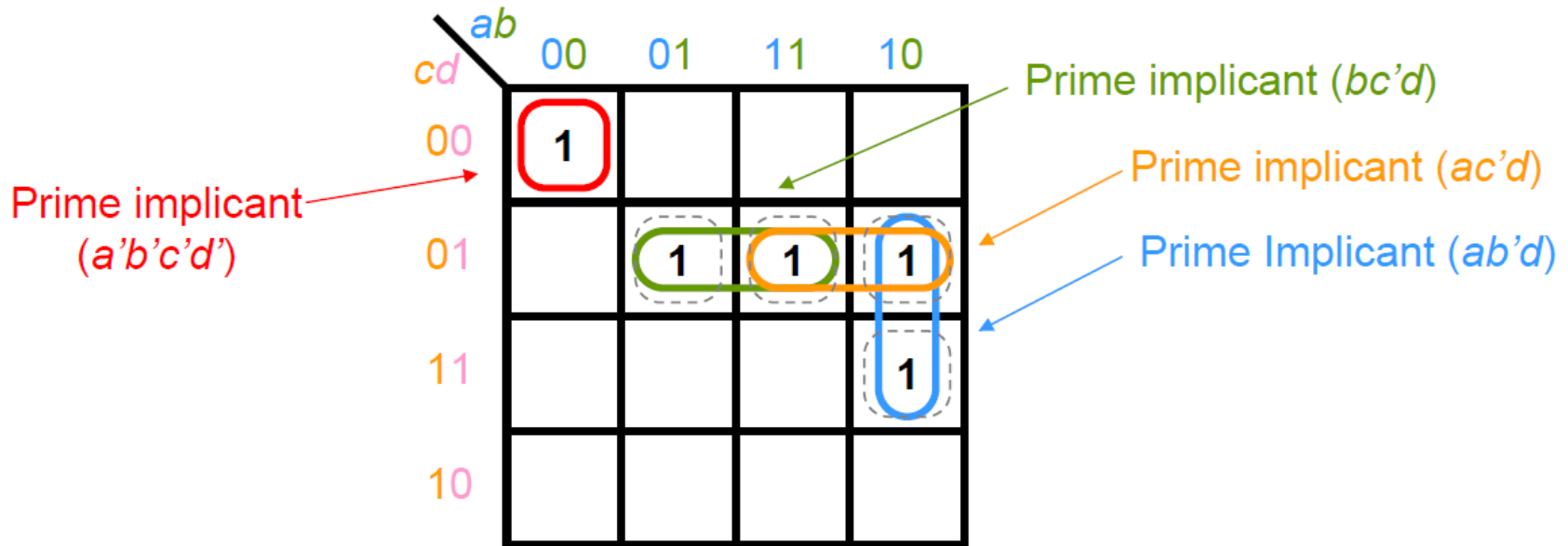
# Prime Implicant (PI)


- If the removal of any literal from an implicant  $P$  results in a product term that is not an implicant of the function,  $P$  is a **prime implicant**




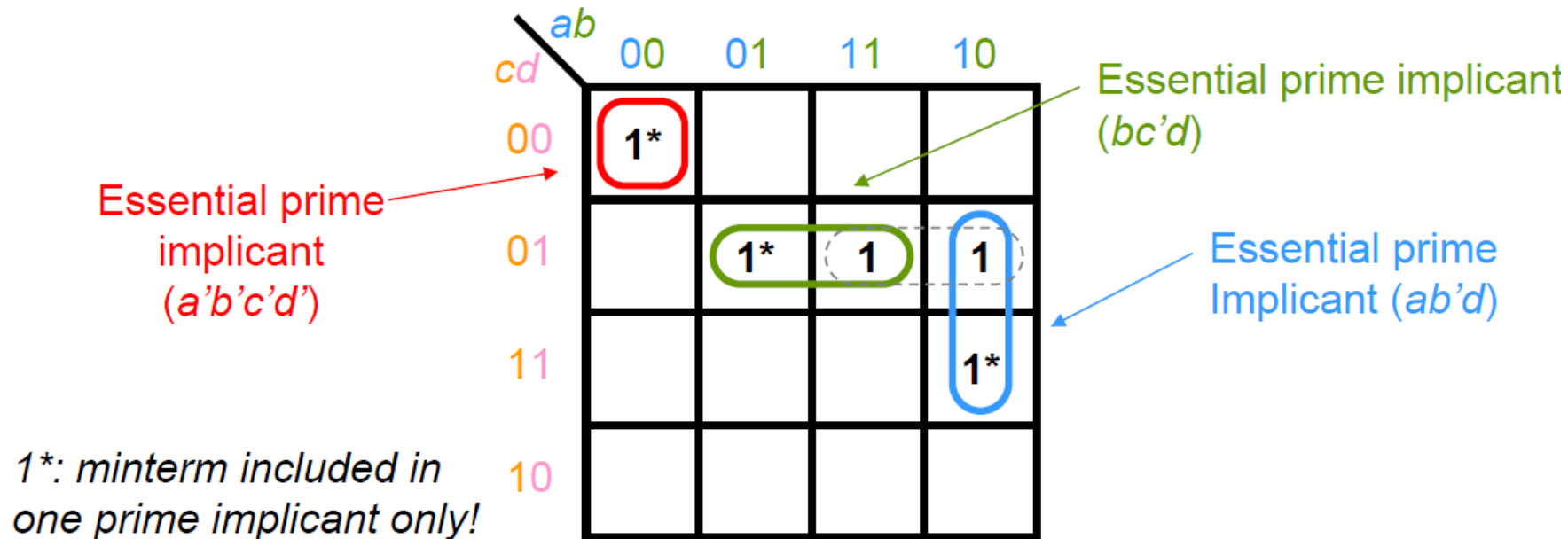
# Essential Prime Implicant


- If a minterm of a function is included in only one prime implicant, that prime implicant is **essential prime implicant**




# Systematic Procedure

- How to satisfy rule (1) and (2)?
- To find the minimized expression from the K-map
  - Step 1) First determine all Pls & EPIs
  - Step 2) Select the EPIs
  - Step 3) If there are remaining minterms, select the Pls that including them

# Back to the Previous Example

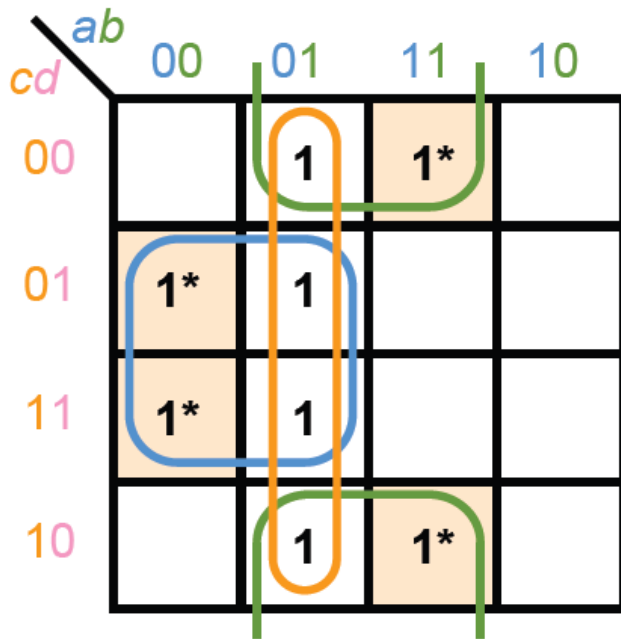


PIs:   
 EPI: 

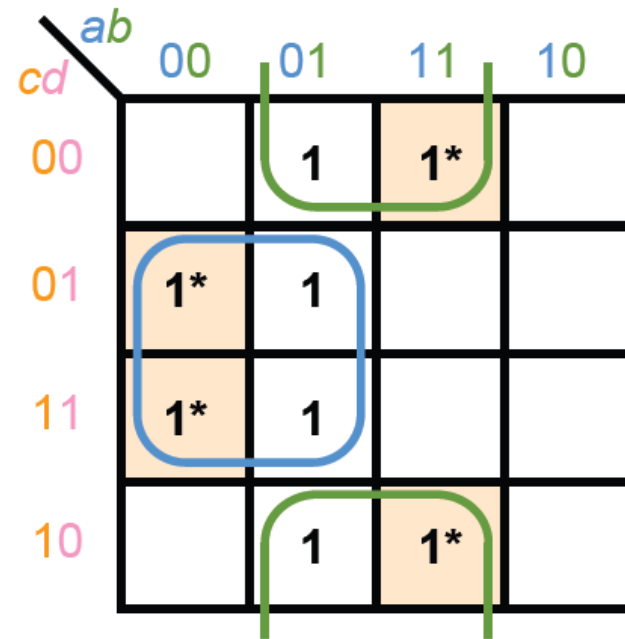

Select the essential prime implicants  
and no remaining minterms left!


$$f(a, b, c, d) = a'd + bd'$$

# Back to the Previous Example

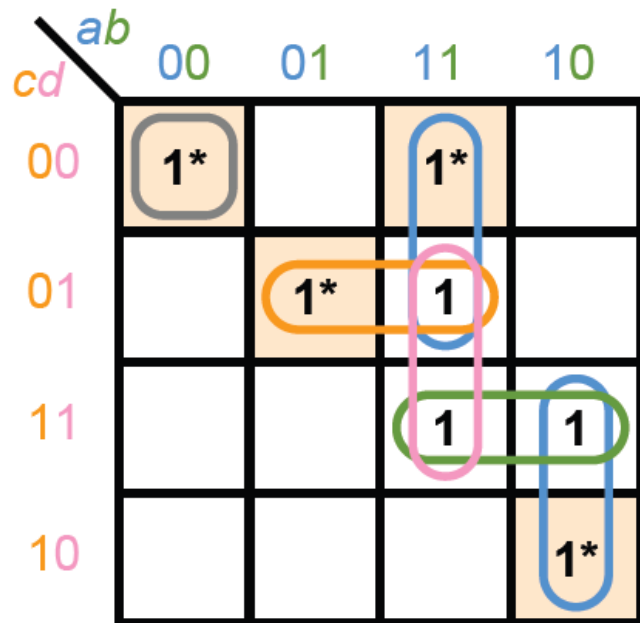

PIs:


EPIs:

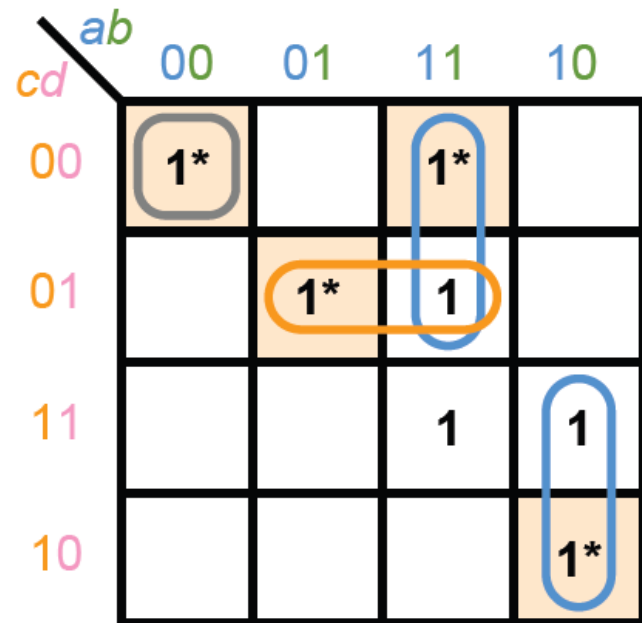

Select the essential prime implicants first


Still have a remaining minterm

# Two Solutions

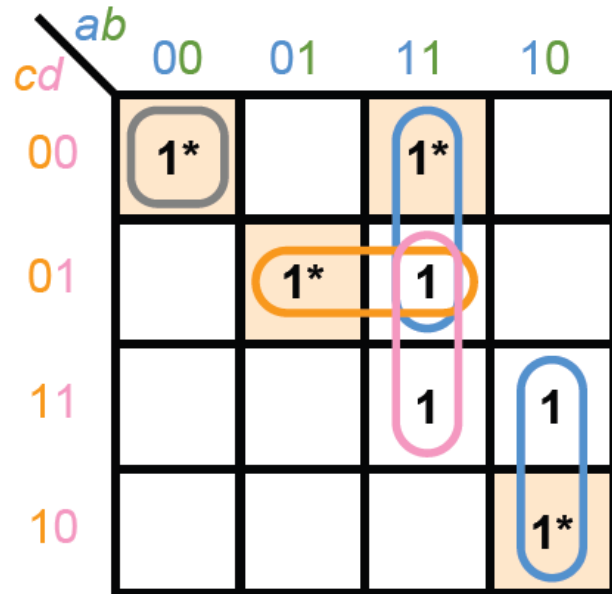

$$f(a, b, c, d) = a'b'c'd' + abc' + ab'c + bc'd + abd$$

or

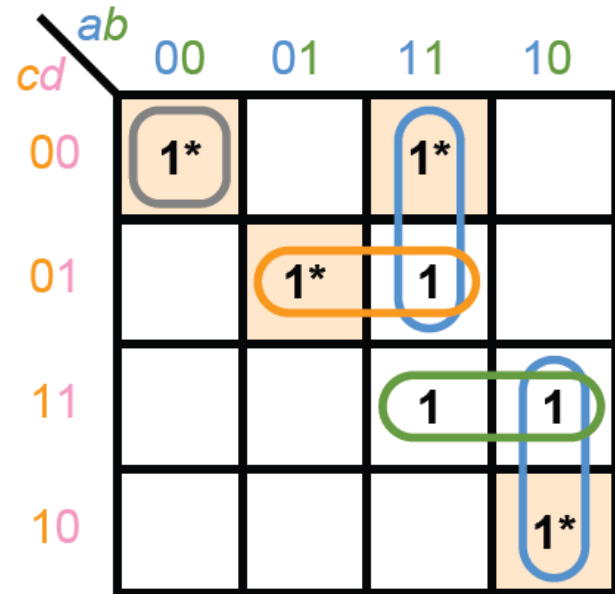

$$f(a, b, c, d) = a'b'c'd' + abc' + ab'c + bc'd + acd$$

We can choose either  or 

# Minimization using Karnaugh Map

- Previous examples only show the simplified Boolean functions in **SOP** form
- How to obtain functions in **POS** form
  - [Step 1] Group the 0s to obtain the complement of the  $f$  in **SOP** form
  - [Step2] Apply DeMorgan's Theorem to find  $f'$  in **POS** form

# Example: Find POS

Simplify  $f(a, b, c, d) = \Sigma m(0, 1, 2, 5, 8, 9, 10)$  in POS form

$cd \backslash ab$	00	01	11	10
00	1	0	0	1
01	1	1	0	1
11	0	0	0	0
10	1	0	0	1

Fill the 1s and 0s into the map

$cd \backslash ab$	00	01	11	10
00	1	0	0	1
01	1	1	0	1
11	0	0	0	0
10	1	0	0	1

Group the 0s using the same procedure as grouping the 1s

$$f'(a, b, c, d) = ab + cd + bd'$$

$$f(a, b, c, d) = (a' + b')(c' + d')(b' + d)$$

## 2.4 Boolean functions with Don't-care cases

The output of Boolean functions are **incompletely specified functions**,

- For some input conditions, the outputs are unspecified
- Input condition has no effects to the function
- Output values are defined as **don't-care**
- Don't-care term can be minterm / maxterms
- Don't-care term indicates by an  $\times$ ,  $d$ ,  $\phi$  or  $\varphi$



# Truth Table with Don't Care

$a$	$b$	$f$
0	0	0
0	1	1
1	0	1
1	1	X

*What the table says is:*

$f$  is 0 if  $(a = 0 \text{ AND } b = 0)$   
 $f$  is 1 if  $(a = 0 \text{ AND } b = 1)$ , or  
 $(a = 1 \text{ AND } b = 0)$   
 $f$  can be 0 or 1 if  $(a = 1 \text{ AND } b = 1)$

$$f(a, b) = \Sigma m(1, 2) + \Sigma d(3)$$

$a$	$b$	$f_1$	$f_2$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	1

Both  $f_1$  or  $f_2$  of table on the left are acceptable

# Don't-care in K-map

Which solution is better?

$b \backslash a$	0	1
0	0	1
1	1	X

$b \backslash a$	0	1
0	0	1
1	1	0

$f_1$  implementation

2 groups

$$f = a'b + ab'$$

$b \backslash a$	0	1
0	0	1
1	1	1

$f_2$  implementation

2 groups

$$f = a + b$$

# Procedure for K-map in don't-care cases

1. Must include all 1s in the map (but  $\times$  is optional)
2. Select the EPIs first, then remaining Pis
3. Choose the largest PI terms that may contains don't-care terms  $\times$

Simplify  $f(a, b, c, d) = \Sigma m(1, 3, 7, 11, 15) + \Sigma d(0, 2, 5)$

		$ab$			
		00	01	11	10
$cd$	00	$\times$	0	0	0
	01	1	$\times$	0	0
	11	1	1	1	1
	10	$\times$	0	0	0

		$ab$			
		00	01	11	10
$cd$	00	$\times$	0	0	0
	01	1	$\times$	0	0
	11	1	1	1	1
	10	$\times$	0	0	0

$$f(a, b, c, d) = a'b'd + cd$$

Is it a good solution?

# Other solutions

1. Must include all 1s in the map (but  $\times$  is optional)
2. Select the EPIs first, then remaining PIs
3. Choose the largest PI terms that may contains don't-care terms  $\times$

	$ab$			
	00	01	11	10
$cd$ 00	X	0	0	0
01	1	X	0	0
11	1	1	1	1
10	X	0	0	0

$$f(a, b, c, d) = a'b' + cd$$

	$ab$			
	00	01	11	10
$cd$ 00	X	0	0	0
01	1	X	0	0
11	1	1	1	1
10	X	0	0	0

$$f(a, b, c, d) = a'd + cd$$

Choose to include those Xs that give largest PIs

## 2.5 Minimization using Quine-McCluskey (QM) Method

- Developed by W. V. Quine and E. J. McCluskey in 1956
- Functionally identical to Karnaugh map
- More efficient in computer algorithms
- Ease to handle large number of variables

For number of variables is less than 4, we use K-map; otherwise, QM method will be more efficient.

# Procedure of QM-method

- Partitioning
- Combining
- Identifying Prime Implicants (PI)
- Generating PI chart
- Reducing chart
- Reporting result

# QM-method

- Partitioning

Simplify  $f(a, b, c, d) = \Sigma m(1, 4, 5, 6, 8, 9, 10, 12, 14)$

List all minterms of the function first

Minterms	<i>abcd</i>
$m_1$	0001
$m_4$	0100
$m_5$	0101
$m_6$	0110
$m_8$	1000
$m_9$	1001
$m_{10}$	1010
$m_{12}$	1100
$m_{14}$	1110



Partition them into groups

Minterms	<i>abcd</i>	
$m_1$	0001	} 1 1s
$m_4$	0100	
$m_8$	1000	
$m_5$	0101	} 2 1s
$m_6$	0110	
$m_9$	1001	
$m_{10}$	1010	
$m_{12}$	1100	} 3 1s
$m_{14}$	1110	

# QM-method

- Combing

Compare the partitioned terms that follows Gary code property

Combine adjacent group implicants into  $(n-1)$ -variable implicants

Mark the changed bit as “-” and give a ✓ to the combined implicants

Minterms	<i>abcd</i>
$m_1$	0001 ✓
$m_4$	0100 ✓
$m_8$	1000 ✓
$m_5$	0101 ✓
$m_6$	0110 ✓
$m_9$	1001 ✓
$m_{10}$	1010 ✓
$m_{12}$	1100 ✓
$m_{14}$	1110 ✓

implicants

Minterms	<i>abcd</i>
$m_1, m_5$	0-01
$m_1, m_9$	-001
$m_4, m_5$	010-
$m_4, m_6$	01-0
$m_4, m_{12}$	-100
$m_8, m_9$	100-
$m_8, m_{10}$	10-0
$m_8, m_{12}$	1-00
$m_6, m_{14}$	-110
$m_{10}, m_{14}$	1-10
$m_{12}, m_{14}$	11-0

implicants

0001  
0101



# QM-method

- Combing

Further compare the new partitioned terms that follows Gary

Further combine adjacent group implicants into  $(n-2)$ -variable implicants

Minterms	<i>abcd</i>
$m_1, m_5$	0-01
$m_1, m_9$	-001
$m_4, m_5$	010-
$m_4, m_6$	01-0 ✓
$m_4, m_{12}$	-100 ✓
$m_8, m_9$	100-
$m_8, m_{10}$	10-0 ✓
$m_8, m_{12}$	1-00 ✓
$m_6, m_{14}$	-110 ✓
$m_{10}, m_{14}$	1-10 ✓
$m_{12}, m_{14}$	11-0 ✓

Again, mark the changed bit as “-” and give a ✓ to the combined implicants

Minterms	<i>abcd</i>
$m_4, m_6, m_{12}, m_{14}$	-1-0
$m_8, m_{10}, m_{12}, m_{14}$	1--0

No more combination

$m_4, m_6: \underline{0}1-0$        $m_4, m_{12}: -1\underline{0}0$   
 $m_{12}, m_{14}: \underline{1}1-0$        $m_6, m_{14}: -1\underline{1}0$

# QM-method

- Identifying Prime Implicants (PI)

Minterms	<i>abcd</i>	Minterms	<i>abcd</i>	Minterms	<i>abcd</i>
$m_1$	0001 ✓	$m_1, m_5$	0-01 $PI_3$	$m_4, m_6, m_{12}, m_{14}$	-1-0 $PI_1$
$m_4$	0100 ✓	$m_1, m_9$	-001 $PI_4$	$m_8, m_{10}, m_{12}, m_{14}$	1--0 $PI_2$
$m_8$	1000 ✓	$m_4, m_5$	010- $PI_5$	<p>The remaining unmarked implicants are prime implicants. Label them as <math>PI_i</math> (label the rightmost column first)</p>	
$m_5$	0101 ✓	$m_4, m_6$	01-0 ✓		
$m_6$	0110 ✓	$m_4, m_{12}$	-100 ✓		
$m_9$	1001 ✓	$m_8, m_9$	100- $PI_6$		
$m_{10}$	1010 ✓	$m_8, m_{10}$	10-0 ✓		
$m_{12}$	1100 ✓	$m_8, m_{12}$	1-00 ✓		
$m_{14}$	1110 ✓	$m_6, m_{14}$	-110 ✓		
		$m_{10}, m_{14}$	1-10 ✓		
		$m_{12}, m_{14}$	11-0 ✓		

# QM-method

- Generating PI chart

Mark an X in the corresponding columns if this PI covers that minterms

e.g.  $PI_1$  involves  $m_4, m_6, m_{12}, m_{14}$

Essential  
prime  
implicants ✓  
✓

PI	Numeric	1	4	5	6	8	9	10	12	14
$PI_1$	-1-0		x		x				x	x
$PI_2$	1--0					x		x	x	x
$PI_3$	0-01	x		x						
$PI_4$	-001	x					x			
$PI_5$	010-		x	x						
$PI_6$	100-					x	x			

These two columns have one X only!

Minterms 6 & 10 are covered by only one prime implicant  
i.e.  $PI_1$  and  $PI_2$  are essential prime implicants

# QM-method

- Reducing chart

Reduce the chart by removing those rows of essential prime implicants and columns that covered by them

PI	Numeric	1	4	5	6	8	9	10	12	14
✓ $PI_1$	-1-0				⊗					
✓ $PI_2$	1--0					x		⊗	x	x
$PI_3$	0-01	x		x						
$PI_4$	-001	x					x			
$PI_5$	010-		x	x						
$PI_6$	100-					x	x			

# QM-method

- Reducing chart

The reduced PI chart may not have any essential prime implicants

PI	Numeric	1	5	9
$PI_3$	0-01	x	x	
$PI_4$	-001	x		x
$PI_5$	010-		x	
$PI_6$	100-			x

How to further reduce the chart?

# QM-method

- Reducing chart (covering rule)

Now go back to the reduced PI chart

PI	Numeric	1	5	9
$PI_3$	0-01	x	x	
$PI_4$	-001	x		x
$PI_5$	010-		x	
$PI_6$	100-			x



PI	Numeric	1	5	9
$PI_3$	0-01	x	x	
$PI_4$	-001	x		x

$PI_5$  is covered by  $PI_3$  (i.e.  $PI_5$  can be removed)

$PI_6$  is covered by  $PI_4$  (i.e.  $PI_6$  can be removed)

By choosing  $PI_3$  &  $PI_4$ , all minterms ( $m_1, m_5, m_9$ ) have been selected


So combining with previous result (all rows with ✓), the minimized function is

$$\begin{aligned}
 f(a, b, c, d) &= PI_1 + PI_2 + PI_3 + PI_4 \\
 &= -1-0 + 1--0 + 0-01 + -001 \\
 &= bd' + ad' + a'c'd + b'c'd
 \end{aligned}$$

**Result!!!**
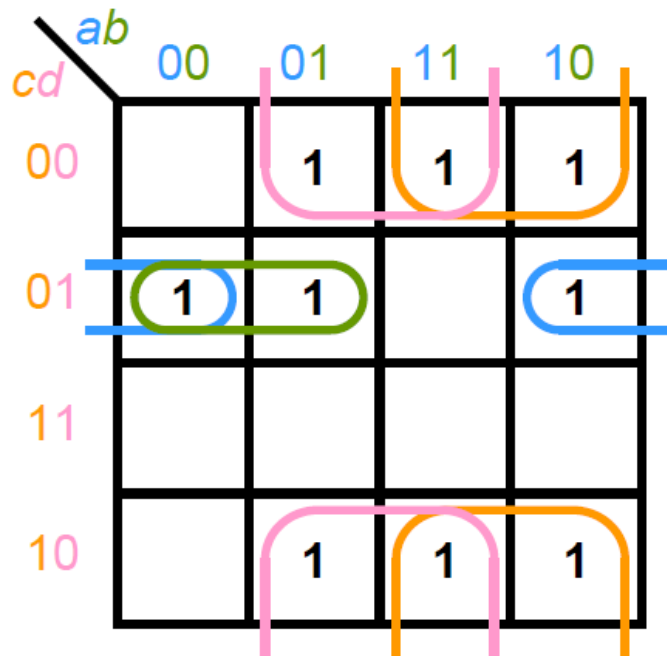
# Verify the Result by K-map

- Simplify  $f(a, b, c, d) = \sum m(1, 4, 5, 6, 8, 9, 10, 12, 14)$



$$f(a, b, c, d) = bd' + ad' + a'c'd + b'c'd$$

# Don't Care Conditions

- How to minimize incompletely specified functions using Q-M method?
  - The first three steps are the same (list, partition and combine)
  - But do **NOT** list the don't care minterms in the PI chart in step 4
- The reason is
  - We set don't care terms to minterms so as to find PIs
  - But omit them as the don't care terms are not essential to be covered



# Example: Don't Care

Simplify  $f(a, b, c, d) = \sum m(4, 8, 9, 10, 12, 15) + \sum d(2, 6, 13)$

The don't care terms are listed together      Partition the terms as usual

Minterms	<i>abcd</i>
$m_2$	0010
$m_4$	0100
$m_6$	0110
$m_8$	1000
$m_9$	1001
$m_{10}$	1010
$m_{12}$	1100
$m_{13}$	1101
$m_{15}$	1111



Minterms	<i>abcd</i>
$m_2$	0010
$m_4$	0100
$m_8$	1000
$m_6$	0110
$m_9$	1001
$m_{10}$	1010
$m_{12}$	1100
$m_{13}$	1101
$m_{15}$	1111

# Example: Don't Care

Combine them to form prime implicants

Minterms	<i>abcd</i>	Minterms	<i>abcd</i>	Minterms	<i>abcd</i>
$m_2$	0010 ✓	$m_2, m_6$	0-10 $PI_2$	$m_8, m_9, m_{12}, m_{13}$	1-0- $PI_1$
$m_4$	0100 ✓	$m_2, m_{10}$	-010 $PI_3$		
$m_8$	1000 ✓	$m_4, m_6$	01-0 $PI_4$		
$m_6$	0110 ✓	$m_4, m_{12}$	-100 $PI_5$		
$m_9$	1001 ✓	$m_8, m_9$	100- ✓		
$m_{10}$	1010 ✓	$m_8, m_{10}$	10-0 $PI_6$		
$m_{12}$	1100 ✓	$m_8, m_{12}$	1-00 ✓		
$m_{13}$	1101 ✓	$m_9, m_{13}$	1-01 ✓		
$m_{15}$	1111 ✓	$m_{12}, m_{13}$	110- ✓		
		$m_{13}, m_{15}$	11-1 $PI_7$		

# Example: Don't Care

Note that the don't care terms  $m_2, m_6, m_{13}$  are not listed in this chart!

Find the essential prime implicants and reduce the chart as usual

PI	Numeric	4	8	9	10	12	15
$PI_1$	1-0-		x	(x)		x	
$PI_2$	0-10						
$PI_3$	-010				x		
$PI_4$	01-0	x					
$PI_5$	-100	x				x	
$PI_6$	10-0		x		x		
$PI_7$	11-1						(x)



PI	Numeric	4	10
$PI_3$	-010		x
$PI_4$	01-0	x	
$PI_5$	-100	x	
$PI_6$	10-0		x



PI	Numeric	4	10
$PI_3$	-010		x
$PI_4$	01-0	x	



$$\begin{aligned}
 f(a, b, c, d) &= PI_1 + PI_3 + PI_4 + PI_7 \\
 &= 1-0- + -010 + 01-0 + 11-1 \\
 &= ac' + b'cd' + a'bd' + abd
 \end{aligned}$$

# Summary

