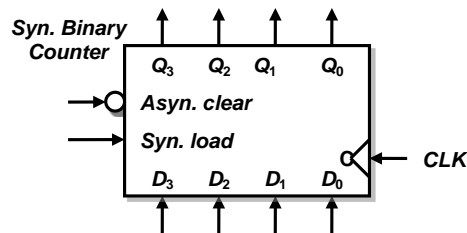


EE 2000 Logic Circuit Design
Semester A 2021A

Tutorial 10

1. Using JK FFs and with the minimum number of states to design a counter with counting sequence: 0,4,2,1,6 and repeat. State whether the circuit is a self started circuit.
2. Design a sequential circuit with two JK FFs, A & B , and two inputs, x & E . if $E=0$, the circuit remains in the same state regardless of the value of x . When $E = 1$ and $x = 1$, the circuit goes through the state transitions from 00 to 01 to 10 to 11 back to 00, and repeats. When $E = 1$ and $x = 0$, the circuit goes through the state transitions from 00 to 11 to 10 to 01 back to 00, and repeats.
3. Using a synchronous binary counters as shown in Figure 1, design and draw a counter to generate the following repeating sequences 2 to 9 repeatedly for a free running clock.



4. Write the VHDL code for a D-FF with (i) asynchronous Preset and Clear, and (ii) synchronous Preset and Clear.