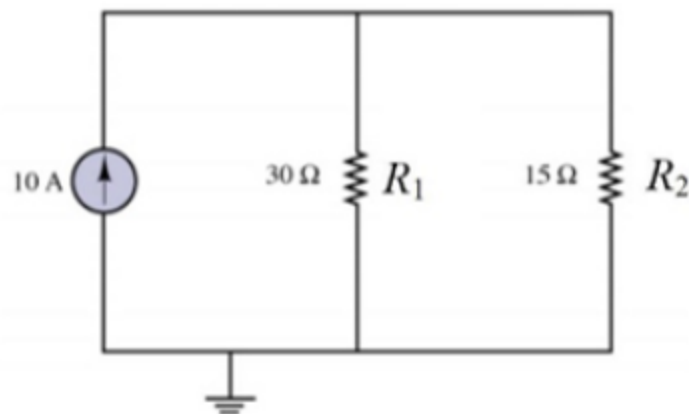


Question 1

3 pts

Find the power consumed by resistors R_1 and R_2 .


Find the power consumed by resistors R_1 and R_2 .



Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

For the four capacitors connected as shown on the following circuit, find the equivalent capacitance C_{ab} .

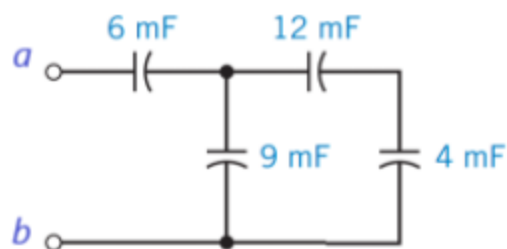For the four capacitors connected as shown on the following circuit, find the equivalent capacitance C_{ab} .



Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the image version first.



☐ 4 mF

4 mF

☐ 31 mF

31 mF

☐ $54/33\text{ mF}$

$\frac{54}{33}\text{ mF}$

☐ $78/7\text{ mF}$


$\frac{78}{7}\text{ mF}$

Question 3

3 pts

Under the dc condition, find i_L , v_C , and v_R in the following circuit.

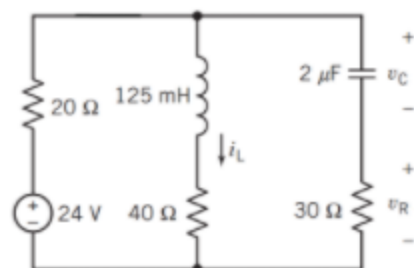Under the dc condition, find i_L , v_C , and v_R in the following circuit.



Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

- ☐ $i_L=0.4$ A, $v_C=0$ V, and $v_R=0$ V

$i_L = 0.4$ A, $v_C = 0$ V, and $v_R = 0$ V

- ☐ $i_L=0$ A, $v_C=0$ V, and $v_R=14.4$ V

$i_L = 0$ A, $v_C = 0$ V, and $v_R = 14.4$ V

- ☐ $i_L=0.4$ A, $v_C=16$ V, and $v_R=0$ V

$i_L = 0.4$ A, $v_C = 16$ V, and $v_R = 0$ V

- ☐ $i_L=0$ A, $v_C=0$ V, and $v_R=0$ V


$i_L = 0$ A, $v_C = 0$ V, and $v_R = 0$ V

Question 4

3 pts

Determine the equivalent impedance Z_{eq} of the following circuit at the frequency $\omega = 1000$ rad/s.

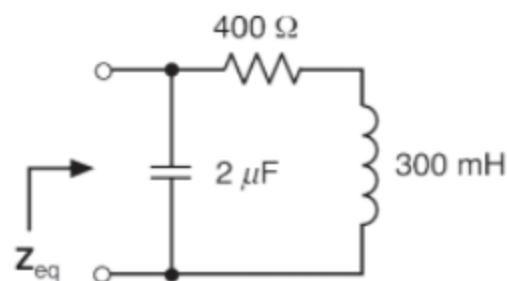Determine the equivalent impedance Z_{eq} of the following circuit at the frequency $\omega = 1000$ rad/s.



Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the **image version** first.

☐ $599\angle -26.5^\circ\ \Omega$

$599\angle -26.5^\circ\ \Omega$

☐ $0.0018\angle 26.5^\circ\ \Omega$

$0.0018\angle 26.5^\circ\ \Omega$

☐ $0.0018\angle -26.5^\circ\ \Omega$


$0.0018\angle -26.5^\circ\ \Omega$

☐ $599\angle 26.5^\circ\ \Omega$

$599\angle 26.5^\circ\ \Omega$

Find the Thevenin equivalent with respect to terminals a - b in the following circuit.

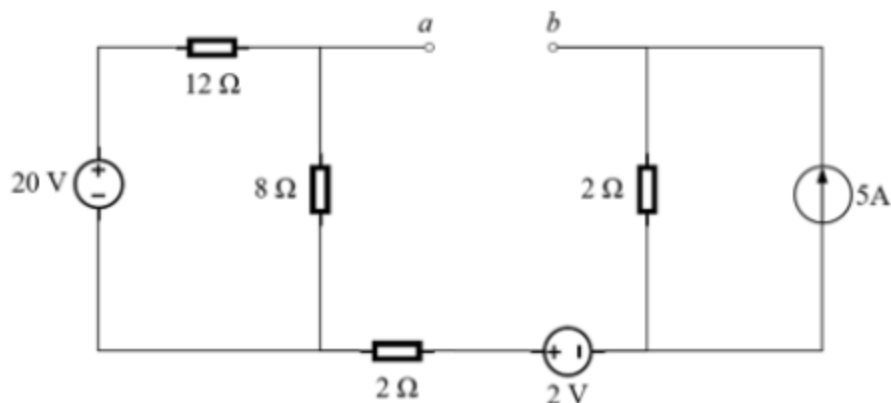Find the Thevenin equivalent with respect to terminals a - b in the following circuit.



Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

☐ $R_{th} = 4.8 \, \Omega, U_{ab} = 20 \, \text{V}$

$R_{th} = 4.8 \, \Omega, U_{ab} = 20 \, \text{V}$

☐ $R_{th} = 8.8 \, \Omega, U_{ab} = 20 \, \text{V}$

$R_{th} = 8.8 \, \Omega, U_{ab} = 20 \, \text{V}$

☐ $R_{th} = 4.8 \, \Omega, U_{ab} = 0 \, \text{V}$

$R_{th} = 4.8 \, \Omega, U_{ab} = 0 \, \text{V}$

☐ $R_{th} = 8.8 \, \Omega, U_{ab} = 0 \, \text{V}$

$R_{th} = 8.8 \, \Omega, U_{ab} = 0 \, \text{V}$

Question 6

3 pts

If $y = x^6 \sin(1/x)$, find the derivative of y .

If $y = x^6 \sin(1/x)$, find the derivative of y .

Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

☐ $x^5 \sin(1/x) - x^4 \cos(1/x)$

$x^5 \sin(1/x) - x^4 \cos(1/x)$

☐ $5x^5 \sin(1/x) + x^4 \cos(1/x)$

$5x^5 \sin(1/x) + x^4 \cos(1/x)$

☐ $6x^5 \sin(1/x) - x^4 \cos(1/x)$

$6x^5 \sin(1/x) - x^4 \cos(1/x)$

☐ $5x^5 \sin(1/x) - x^4 \cos(1/x)$

$5x^5 \sin(1/x) - x^4 \cos(1/x)$

If $\tan \alpha = 3/4$, find $\cos^2 \alpha + 2\sin 2\alpha$.

If $\tan \alpha = 3/4$, find $\cos^2 \alpha + 2\sin 2\alpha$.

Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

☐ 48/25

48/25

☐ 16/25

16/25

☐ 1


1

☐ 64/25

64/25

For the four inductors connected in the following circuit, find the equivalent inductance L_{ab} .

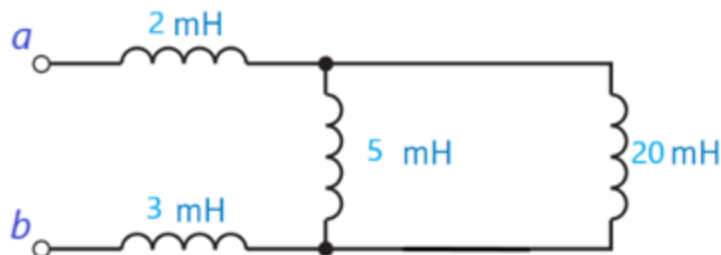For the four inductors connected in the following circuit, find the equivalent inductance L_{ab} .



Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

☐ 150/131 mH

150/131 mH

☐ 30 mH

30 mH

☐ 9 mH

9 mH

☐ 12/13 mH

12/13 mH


Question 9

3 pts

In the following circuit, the impedances are given by $Z_1 = 5\angle 51.3^\circ \Omega$ and $Z_2 = 8\sqrt{2}\angle -45^\circ \Omega$. Find the current $i(t)$.

In the following circuit, the impedances are given by $Z_1 = 5\angle 51.3^\circ \Omega$ and $Z_2 = 8\sqrt{2}\angle -45^\circ \Omega$.

Find the current $i(t)$.

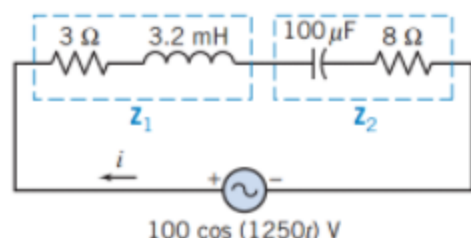

Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

☐ $i(t) = 8.55 \cos(1250t + 20^\circ)\text{ A}$

$i(t) = 8.55 \cos(1250t + 20^\circ)\text{ A}$

☐ $i(t) = 8.55 \cos(1250t - 20^\circ)\text{ A}$

$i(t) = 8.55 \cos(1250t - 20^\circ)\text{ A}$

☐ $i(t) = 8.55 \cos(1250t - 70^\circ)\text{ A}$

$i(t) = 8.55 \cos(1250t - 70^\circ)\text{ A}$

☐ $i(t) = 8.55 \cos(1250t - 110^\circ)\text{ A}$

$i(t) = 8.55 \cos(1250t - 110^\circ)\text{ A}$

If $(z - j)j = 2 + j$, find z .

If $(z - j)j = 2 + j$, find z .

Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

☐ $2 + j$

$2 + j$

☐ $1 + j$

$1 + j$

☐ $1 - j$


$1 - j$

☐ $2 - j$

$2 - j$

Express the voltage in the following figure in the general form $v(t) = A \cos(\omega t + \phi)$ V where $A \geq 0$ and $-180^\circ < \phi \leq 180^\circ$.

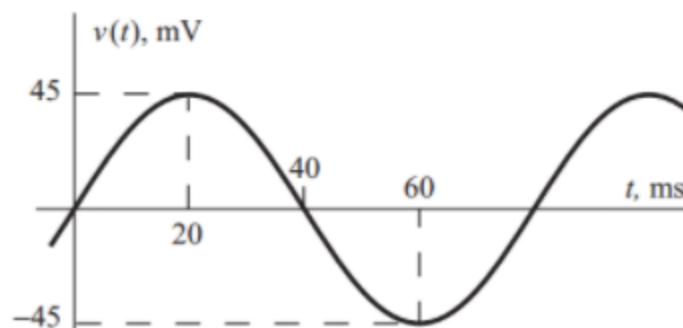Express the voltage in the following figure in the general form $v(t) = A \cos(\omega t + \phi)$ V where $A \geq 0$ and $-180^\circ < \phi \leq 180^\circ$.



Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

☐ $v(t) = 0.045 \cos(12.5t - 90^\circ)$ V

$v(t) = 0.045 \cos(12.5t - 90^\circ)$ V

☐ $v(t) = 0.045 \cos(25\pi t + 90^\circ)$ V

$v(t) = 0.045 \cos(25\pi t + 90^\circ)$ V

☐ $v(t) = 0.045 \cos(25\pi t - 90^\circ)$ V

$v(t) = 0.045 \cos(25\pi t - 90^\circ)$ V

☐ $v(t) = 0.045 \cos(12.5t + 90^\circ)$ V

$v(t) = 0.045 \cos(12.5t + 90^\circ)$ V

Question 12

3 pts

Determine the capacitance of a capacitor when the voltage across it is $v(t)=12\cos(500t-45^\circ)$ V and the current is $i(t)=3\cos(500t+45^\circ)$ mA.

Determine the capacitance of a capacitor when the voltage across it is $v(t) = 12 \cos(500t - 45^\circ)$ V and the current is $i(t) = 3 \cos(500t + 45^\circ)$ mA.

Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the image version first.

☐ C=0.5 mF

$$C = 0.5 \text{ mF}$$

☐ C=0.5 uF

$$C = 0.5 \text{ uF}$$

☐ C=8 mF

$$C = 8 \text{ mF}$$

☐ C=8 F

$$C = 8 \text{ F}$$

Evaluate $\int x e^{x^2} dx$

Evaluate $\int x e^{x^2} dx$

Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

☐ $x^2 e^x + c$

$x^2 e^x + c$

☐ $\frac{1}{2} e^{x^2} + c$

$\frac{1}{2} e^{x^2} + c$

☐ $e^{x^2} + c$


$e^{x^2} + c$

☐ $2e^{x^2} + c$

$2e^{x^2} + c$

Find the Norton equivalent with respect to terminals a - b in the following circuit.

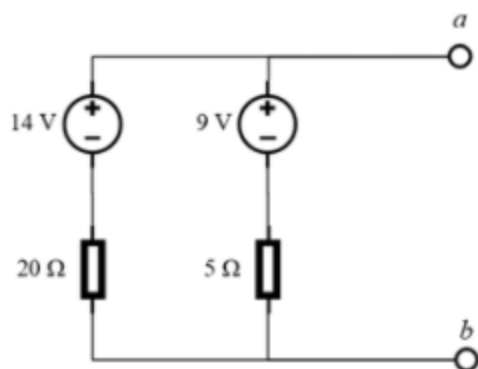Find the Norton equivalent with respect to terminals a - b in the following circuit.



Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

☐ $R_N = 0.25 \, \Omega, I_N = 1.06 \, \text{A}$

$R_N = 0.25 \, \Omega, I_N = 1.06 \, \text{A}$

☐ $R_N = 4 \, \Omega, I_N = 1.06 \, \text{A}$

$R_N = 4 \, \Omega, I_N = 1.06 \, \text{A}$

☐ $R_N = 4 \, \Omega, I_N = 2.5 \, \text{A}$


$R_N = 4 \, \Omega, I_N = 2.5 \, \text{A}$

☐ $R_N = 0.25 \, \Omega, I_N = 2.5 \, \text{A}$

$R_N = 0.25 \, \Omega, I_N = 2.5 \, \text{A}$

Under steady-state dc conditions, find i_L and v_c of the following circuit.

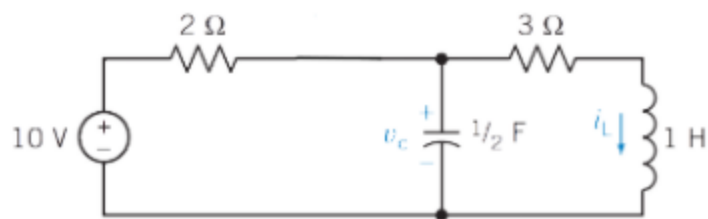Under steady-state dc conditions, find i_L and v_c of the following circuit.



Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the **image version** first.

☐ $i_L = 2 \text{ A}, v_c = 6 \text{ V}$

$i_L = 2 \text{ A}, v_c = 6 \text{ V}$

☐ $i_L = 3.33 \text{ A}, v_c = 4 \text{ V}$

$i_L = 3.33 \text{ A}, v_c = 4 \text{ V}$

☐ $i_L = 1.33 \text{ A}, v_c = 4 \text{ V}$

$i_L = 1.33 \text{ A}, v_c = 4 \text{ V}$

☐ $i_L = 1.33 \text{ A}, v_c = 6 \text{ V}$


$i_L = 1.33 \text{ A}, v_c = 6 \text{ V}$

Find i for the following circuit if $v = 5(1 - 2e^{-2t})$ V.

[Hint: You may use the KCL to solve the problem.]

Find i for the following circuit if $v = 5(1 - 2e^{-2t})$ V.

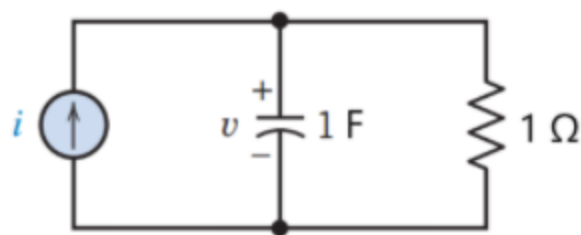[Hint: You may use the KCL to solve the problem.]



Note: Two versions will be given to avoid misunderstandings, the text version (black) and the image version (blue). If the two contents conflict, please refer to the [image version](#) first.

☐ $20e^{-2t}$ A

$20e^{-2t}$ A

☐ $5 - 10e^{-2t}$ A

$5 - 10e^{-2t}$ A

☐ $5 - 30e^{-2t}$ A

$5 - 30e^{-2t}$ A

☐ $5 + 10e^{-2t}$ A

$5 + 10e^{-2t}$ A