

# Block A Unit 2

---

- It is important to apply the 3 basic laws in circuit theory to analyze and design circuits
- This unit is organized into the following 2 sections

I. Nodal Voltage Analysis, Mesh Current Analysis, Superposition  
(Ch. 3, 4.3)

II. Thevenin Equivalent Circuit, Norton Equivalent Circuit,  
Source Transformation, (Ch. 4.4 - 4.6)  
Dependent Source (Ch. 1.6)

Alexander & Sadiku, “Fundamentals of Electric Circuits” , 7<sup>th</sup> Edition, McGraw Hill

# I. Nodal Voltage Analysis (NVA)

---


## KCL & Ohm's law in action

- The method of nodal voltage analysis is *an application of KCL and Ohm's law together*
- The unknown variables that you will solve for are **node voltages**
- We will apply KCL at a node and express the unknown currents as unknown node voltages

# Example on how to do NVA

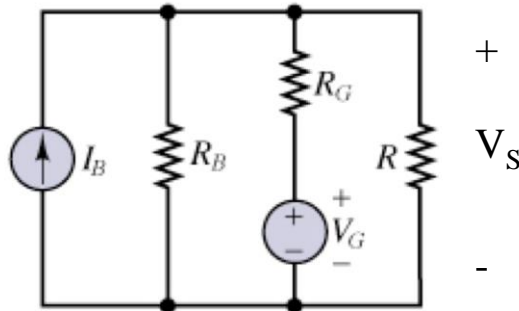**Find the voltage across the current source,  $V_S$ :**

Given:  $I_B = 12\text{A}$ ,  $V_G = 12\text{V}$ ,  $R_G = 0.3\Omega$ ,  $R_B = 1\Omega$ ,  $R = 0.23\Omega$



**Apply KCL at  $V_S$ :**

$$I_B = \frac{V_S}{R_B} + \frac{V_S - V_G}{R_G} + \frac{V_S}{R}$$

$$12 = \frac{V_S}{1} + \frac{V_S - 12}{0.3} + \frac{V_S}{0.23}$$


$$V_S = 5.99\text{V}$$

- Note that the negative terminal of  $V_G$  is used as a reference (0V) in the example
- The value of  $V_S$  is also referenced to this node
- The value of the reference node is not important since we are only interested in the voltage difference
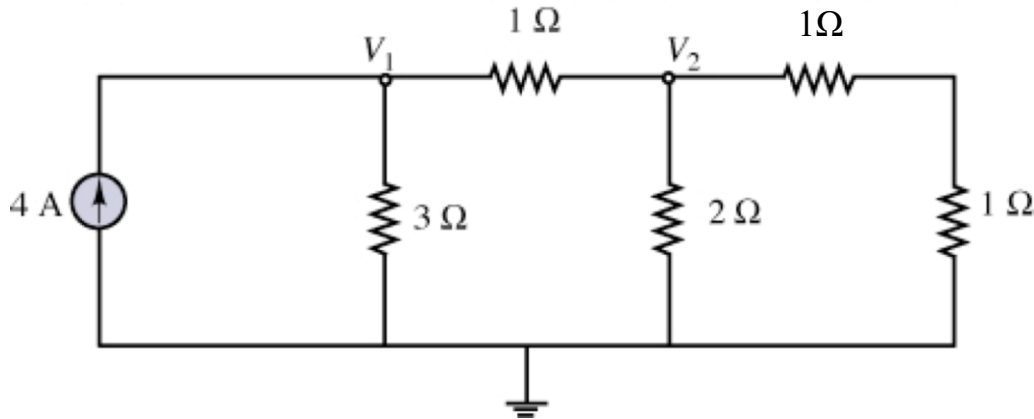
# Worked Example on NVA 1

Use nodal voltage analysis to find  $V_1$  and  $V_2$ . (Answer:  $V_1 = 4.8\text{V}$ ,  $V_2 = 2.4\text{V}$ )

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



**First method:**

- Apply KCL at  $V_1$  (1)
- Apply KCL at  $V_2$  (2)
- Solve equations (1) and (2)

**Alternate method:**

- Combine all the resistors to find  $V_1$  first
- Then combine the 3 resistors on the right followed by voltage divider rule to find  $V_2$

# Mesh Current Analysis (MCA)


---

## KVL & Ohm's law in action

- The method of mesh current analysis is *an application of KVL and Ohm's law together*
- The unknown variables that you will solve for are **mesh currents**
- From KVL, the sum of voltage drops and rise must equal zero
- The voltage differences are expressed as the current going through each branch in the mesh
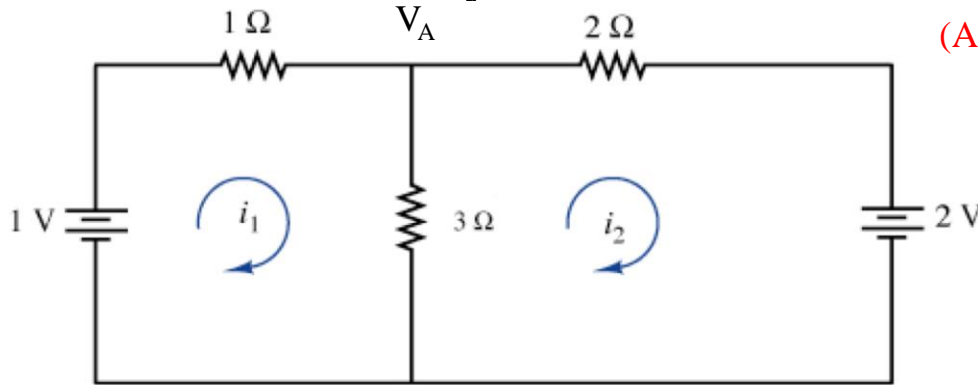
# Example on how to do MCA

Use mesh current analysis to find the current through the  $3\Omega$  resistor.



(Answer:  $i_{3\Omega} = 4/11\text{A}$ )

- There are 2 meshes and hence 2 mesh currents
- Apply KVL to each of these 2 meshes

**Apply KVL to mesh 1:**

$$1 = i_1(1 + 3) - 3i_2$$
$$4i_1 - 3i_2 = 1 \quad (1)$$

**Useful tip:**

- keep voltages of sources on one side of the equation, and keep voltages of resistors on the other side

**Apply KVL to mesh 2:**

Follow the defined direction of the mesh current


$$-2 = i_2(2 + 3) - 3i_1$$
$$5i_2 - 3i_1 = -2 \quad (2)$$

**Now, solve equation (1) and (2):**

$$i_{3\Omega} = i_1 - i_2$$
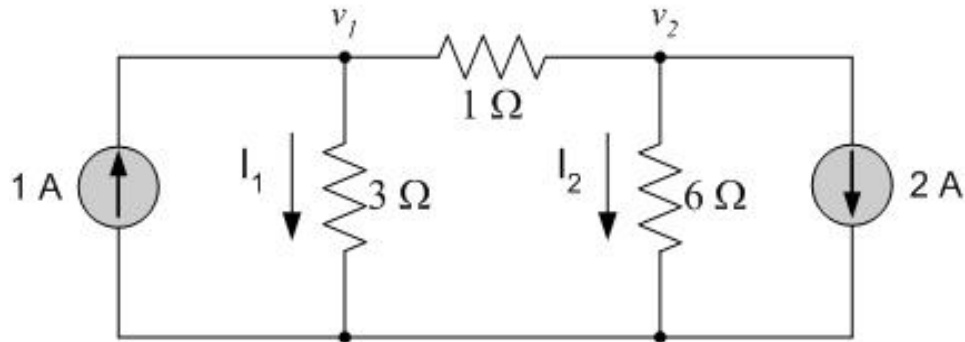
# Worked Example on MCA 1

Use mesh current analysis to find currents  $I_1$  and  $I_2$ . (Answer:  $I_1 = I_2 = -0.5\text{A}$ )



-You see 3 meshes, but only the middle mesh is unknown, the other 2 are defined by the current sources.


-For simplicity, defined the direction of known mesh currents in the same direction as the sources.

# Worked Example on MCA 2

Use mesh current analysis to find the voltage across the current source.

(Answer:  $V = 3.89 \text{ V}$ )

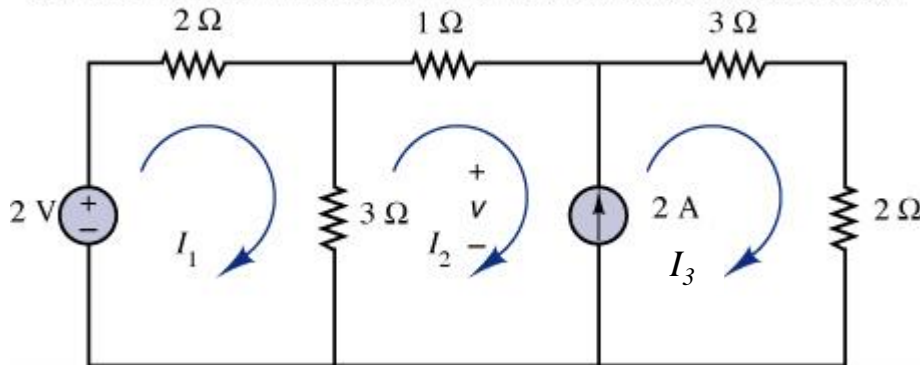Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



-In the process of deriving equations (2) and (3), a new variable  $V$  is introduced.

-Hence, we need one more equation, (4)

**Apply KVL at mesh 1:**

$$2 = I_1(2+3) - I_2(3)$$
$$\Rightarrow 5I_1 - 3I_2 = 2 \quad (1)$$

**Apply KVL at mesh 3:**

$$V = I_3(3+2)$$
$$\Rightarrow 5I_3 = V \quad (3)$$

**Apply KVL at mesh 2:**

$$-V = I_2(3+1) - I_1(3)$$
$$\Rightarrow 4I_2 - 3I_1 = -V \quad (2)$$

**One more equation:**

$$I_3 - I_2 = 2A \quad (4)$$

**Solve for  $V$ , verify by  $V = (I_3)(3+2)$**



# Quick note on choosing NVA and MCA

---


How do you choose between NVA and MCA?

- Your choice should not be due to level of familiarity between the methods.
- One consideration is whichever is simpler to use for a given circuit.
- How then do you decide what is simpler?
- For a start, having fewer equations certainly makes solving easier.

# Superposition
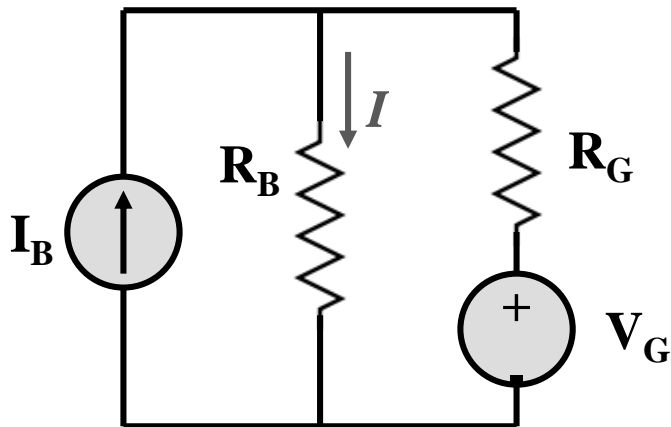
## The method

- This method applies only to circuits that have **multiple sources**
- In such case, it can come in handy (or not)
- In a circuit with multiple sources, superposition considers the current or voltage associated with a given branch for one of the sources, while turning the rest off



**Aim: Find the current through  $R_B$ .**

1. Find the current ( $I_1$ ) through  $R_B$  when only  $I_B$  is present ( $V_G$  is removed)
2. Find the current ( $I_2$ ) through  $R_B$  when only  $V_G$  is present ( $I_B$  is removed)
3. The net current  $I = I_1 + I_2$

Fig 1: Basic circuit with 2 sources

# How do we “remove” a current source or voltage source?

## Disabling sources

**Voltage source:** If the voltage source does not exist, the voltage across the terminals would be zero. It looks like a short circuit. (see Fig 14a)

**Current source:** If the current source does not exist, the current through it would be zero. It looks like an open circuit. (see Fig 14b)

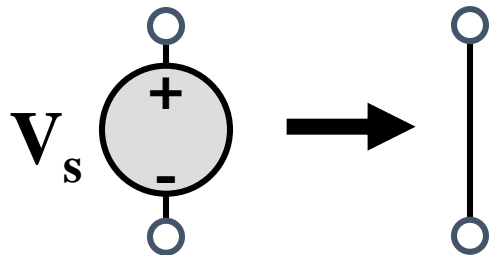


Fig 2a: Disable a voltage source by Replacing with a short circuit.

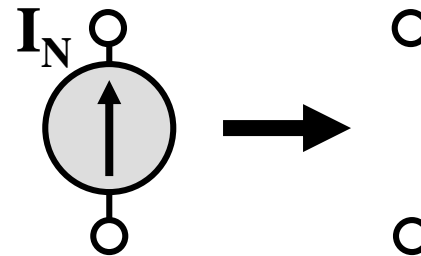


Fig 2b: Disable a current source by Replacing with an open circuit.

# Apply the tips to Fig 1



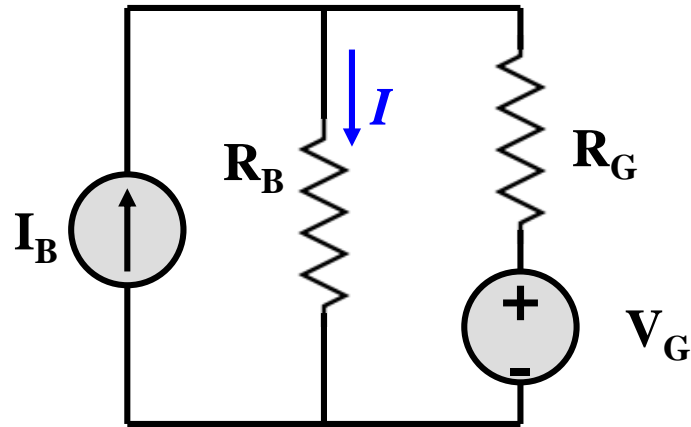


Fig 1: Basic circuit with 2 sources

**Disabling  $V_G$ ,  $V_G = 0$**

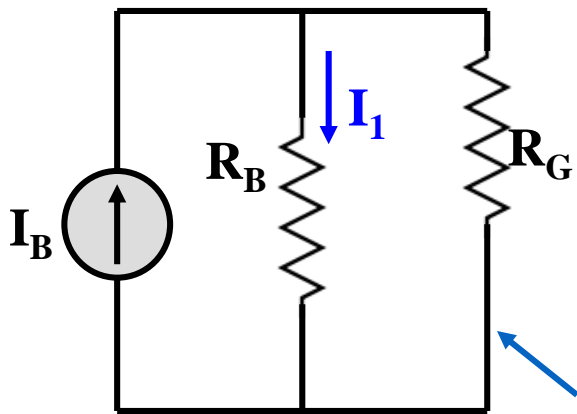

**Disabling  $I_B$ ,  $I_B = 0$**

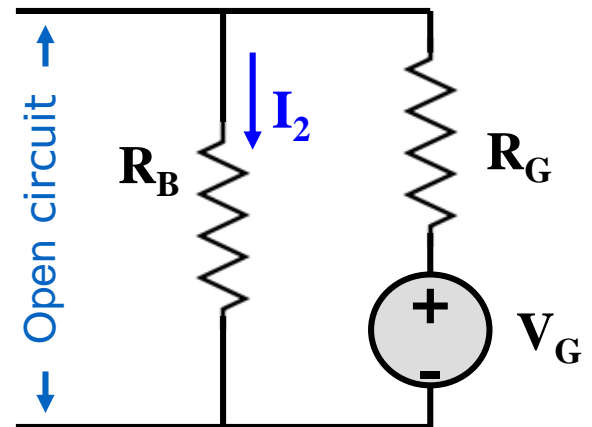

$$I = I_1 + I_2$$

Short circuit


Open circuit

# Worked Example on Superposition

Determine the current through  $R_1$  using superposition.

Given  $R_1 = 560\Omega$ ,  $R_2 = 3.5k\Omega$ ,  $R_3 = 810\Omega$ ,  $V_{S2} = V_{S1} = 90V$

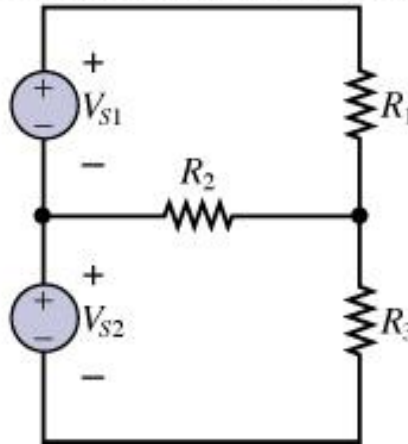Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



a. First, short  $V_{S1}$   
Voltage across  $R_1$ :

$$V_{R1a} = \frac{R_1 \parallel R_2}{(R_1 \parallel R_2) + R_3} V_{S2}$$

$$= \frac{560 \parallel 3500}{(560 \parallel 3500) + 810} 90$$

$$= 33.61V$$

Current through  $R_1$ :

$$I_{R1a} = V_{R1a} / R_{1a}$$

$$= 33.61 / 560$$

$$= 0.06A$$

# Worked Example on Superposition

---

b. Next, short  $V_{S2}$

Current through  $R_1$ :

$$I_{R1b} = \frac{V_{S1}}{R_1 + (R_2 \parallel R_3)} = \frac{90}{560 + (3500 \parallel 810)} \\ = 0.074A$$

**Take careful note of the directions defined for each of these currents.**

Finally,

$$I_{R1} = I_{R1a} + I_{R1b} = 0.134A$$

# One-Port Network

## Introduction

- A **one port network** is simply a **two terminal device** (See Fig below)

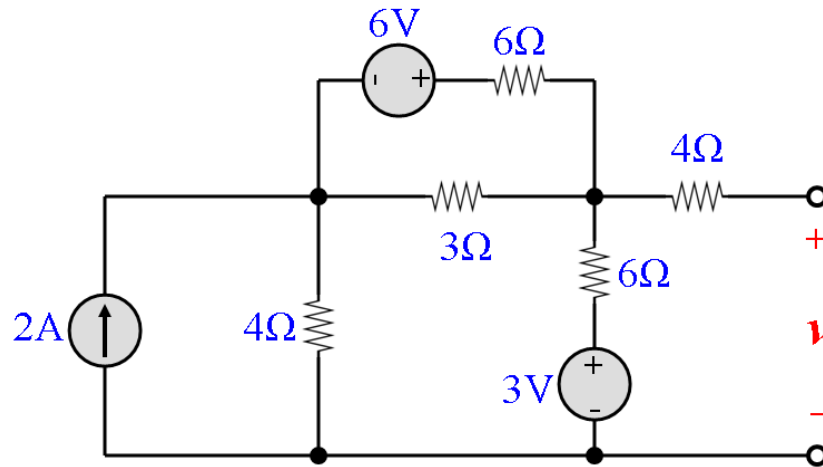



Fig 2: An example of a one port network

- Given a number of different resistor loads, if you were asked to find the current and voltage at the terminals for each resistor, you would have to recalculate the whole circuit
- A different load will give you different output current & voltage

# One-Port Network
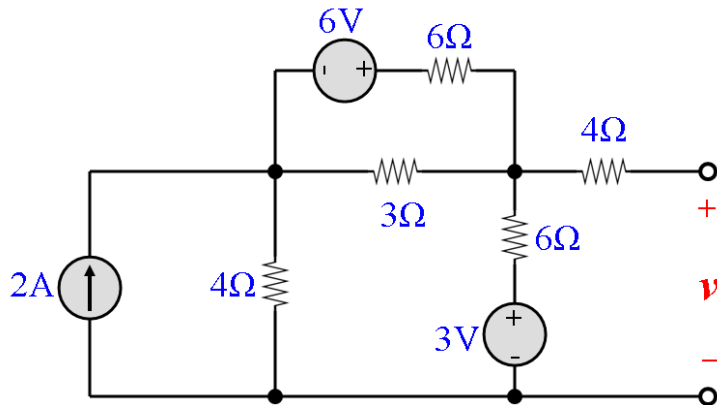
## Simpler analysis

- Transform any 2 terminal circuit into a circuit that is as simple as having 1 resistor and 1 source (see Fig 2)



$V_T$

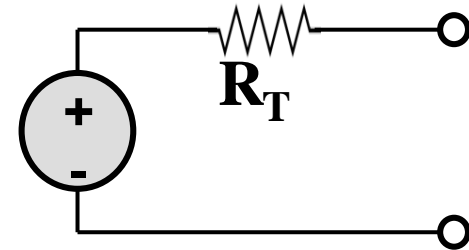


Fig 3: Transformed Thevenin equivalent circuit

The first part of this unit is organized into the following 3 sections:

- Thevenin equivalent
- Norton equivalent
- Source transformation

The last part of this unit will cover all concepts in Block A and apply them to dependent sources.



# II. Thevenin

## Definition

- Any one-port network composed of **ideal** voltage and current sources, and **linear** resistors, can be represented by an equivalent circuit consisting of an ideal **voltage source**  $V_T$  in **series** with an equivalent **resistance**  $R_T$

## Deriving the Thevenin equivalent circuit

**Step 1: Remove the load** from the rest of the one port network. This is the first most fundamental step.

**Step 2: Find the equivalent resistance  $R_T$ .** Disable all ideal sources then find the resistance across the terminals.

For voltage source – replace with short circuit

For current source – replace with open circuit


**Step 3: Find the Thevenin voltage source.** The Thevenin voltage source is equal to the open circuit voltage seen across the terminals (with no load). Solve for this voltage using any preferred method (NVA, MCA, superposition).

# Worked Example on Thevenin 1

Derive the Thevenin equivalent circuit seen by the  $3\Omega$  load.

Answer:  $R_{th} = 3.22\ \Omega$ ,  $V_{th} = 16\ V$

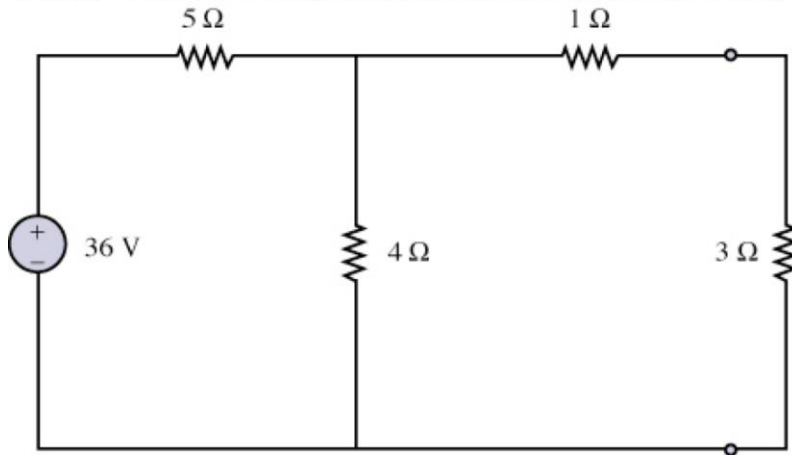Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Steps:

1. Remove the  $3\Omega$  load
2. Find  $R_T$  (disable the voltage source)
3. Find  $V_T$  (with no load)
4. Draw the Thevenin circuit

# Norton

## Definition

- Any one-port network composed of **ideal** voltage and current sources, and **linear** resistors, can be represented by an equivalent circuit consisting of an ideal **current source**  $I_N$  in **parallel** with an equivalent **resistance**  $R_N$

## Deriving the Norton equivalent circuit

**Steps 1 and 2** for deriving the Norton equivalent circuit are exactly the same as that for Thevenin.

**Step 3: Find the Norton current source.** The Norton current source is equal to the short circuit current seen across the terminals (with no load). Solve for this voltage using any preferred method (NVA, MCA, superposition).


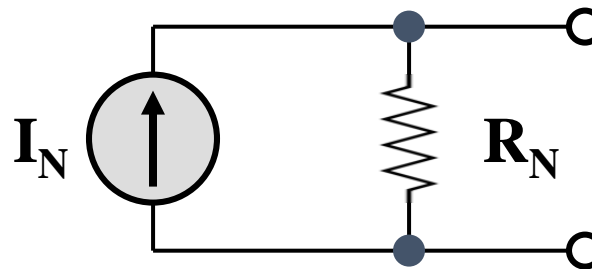


Fig 4: Transformed Norton equivalent circuit
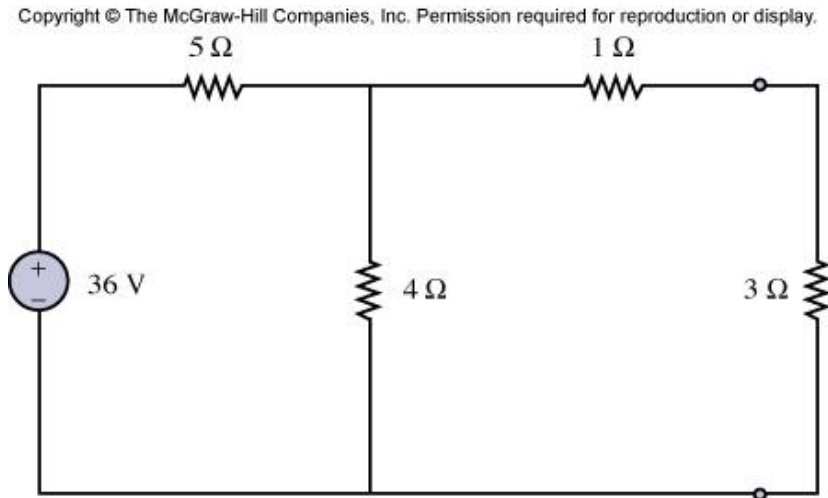
# Worked Example on Norton 1

Derive the Norton equivalent circuit seen by the  $3\Omega$  load.

Answer:  $R_N = 3.22\ \Omega$ ,  $I_N = 4.96\ \text{A}$



# Source Transformation

## Definition

- This trick rests on the fact that the Thevenin and Norton forms are equivalent to each other and therefore are also interchangeable

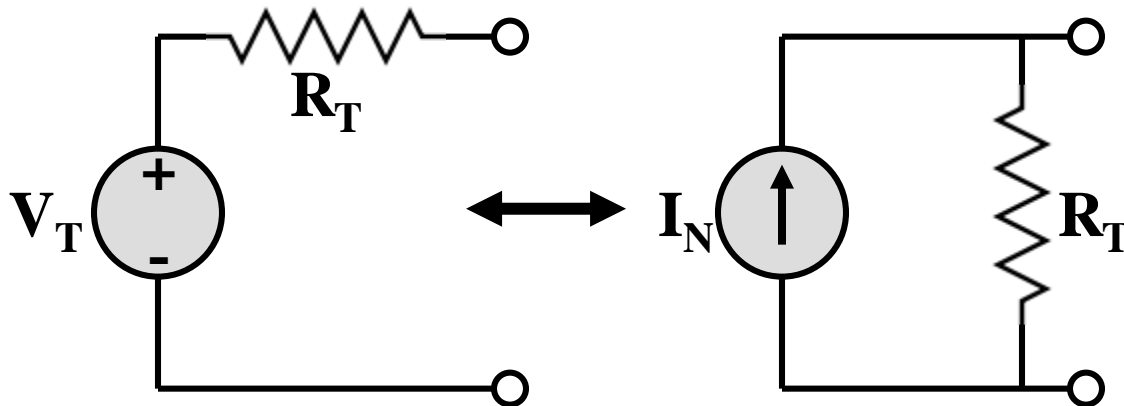


Fig 5a: Thevenin equivalent circuit

Fig 5b: Norton equivalent circuit

**We can transform between the two equivalent circuits, observing each time that:**


$$V_T = I_N R_T$$

- Rather than transform the whole circuit in one go to Thevenin or Norton equivalent forms, we can instead transform part of the circuit
- The process of merge transform and merge again can be repeated
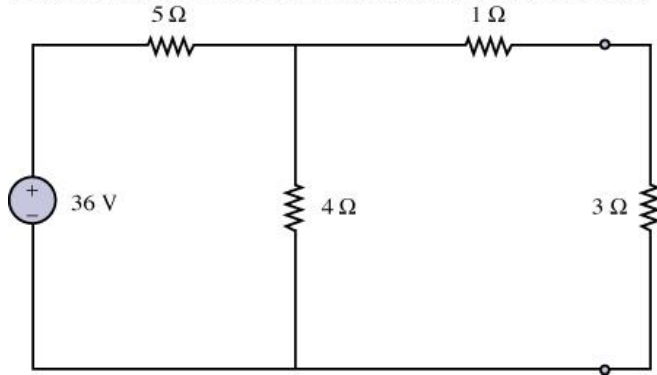
# Worked Example on Source Transformation 1

Derive either of the equivalent circuit forms seen by the  $3\Omega$  load.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Dependent Sources

- All the sources we have come across are independent source
  - > For a voltage source, the voltage maintained across the source is fixed
  - > For a current source, the current through the source is fixed
- There also exist dependent sources in circuit theory
- Unlike independent sources, the value of a dependent source is not predetermined, but is set by the current or voltage through a specific branch

## Symbol

- The symbol for an independent source is a circle
- For a dependent source, the symbol is a diamond

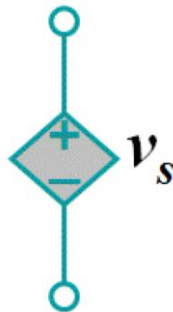


Fig 6a: Dependent voltage source

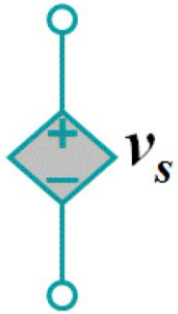


Fig 6b: Dependent current source

# Dependent Sources

## Dependent Voltage Source

$v_s$  is the voltage source across the terminals.



### **Current Controlled Voltage Source**


For example,  $v_s = 5i_x$ . The current  $i_x$  is not the current through the source but belongs to another branch.

### **Voltage Controlled Voltage Source**

For example,  $v_s = 7v_x$ . The voltage  $v_x$  is not the source voltage. As  $v_x$  changes, so also  $v_s$  according to the above relations.
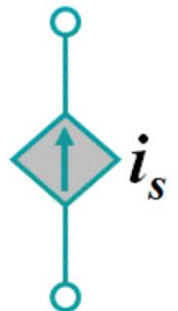
## Dependent Current Source

$i_s$  is the current source through the terminals.



### **Current Controlled Current Source**

For example,  $i_s = 5i_x$ . The current  $i_x$  is not the current through the source but belongs to another branch.

### **Voltage Controlled Current Source**


For example,  $i_s = 7v_x$ . The voltage  $v_x$  is not the source voltage. As  $v_x$  changes, so also  $i_s$  according to the above relations.



# Worked Example on Dependent Source 1

Calculate  $v_o$  in the circuit.

Answer:  $v_o = 3.65 \text{ V}$

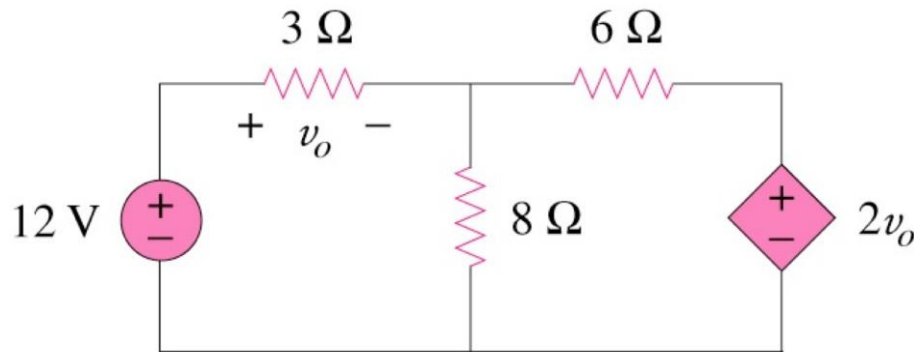

Hints:

1. The dependent source here is a voltage controlled voltage source
2. Apply KCL

# Summary on Block A

---

- This block covered the fundamental concepts to learn Blocks B, C, and D.
  - I. Kirchhoff's Current, Voltage Law, Ohm's Law, Power
  - II. Sources, Short Circuit, Open Circuit
  - III. Resistive Networks
  - IV. Measuring Instruments
  - V. Nodal Voltage Analysis, Mesh Current Analysis, Superposition
  - VI. Thevenin Equivalent Circuit, Norton Equivalent Circuit, Source Transformation, Dependent Source
- Students can refer to the textbook for more working examples

Alexander & Sadiku, "Fundamentals of Electric Circuits" , 7<sup>th</sup> Edition, McGraw Hill