

P.P.9.7

Given that

$$2 \frac{dv}{dt} + 5v + 10 \int v \, dt = 50 \cos(5t - 30^\circ)$$

we take the phasor of each term to get

$$2j\omega \mathbf{V} + 5 \mathbf{V} + \frac{10}{j\omega} \mathbf{V} = 50 \angle -30^\circ, \quad \omega = 5$$

$$\mathbf{V} [j10 + 5 - j(10/5)] = \mathbf{V} (5 + j8) = 50 \angle -30^\circ$$

$$\mathbf{V} = \frac{50 \angle -30^\circ}{5 + j8} = \frac{50 \angle -30^\circ}{9.434 \angle 58^\circ}$$

$$\mathbf{V} = 5.3 \angle -88^\circ$$

Converting \mathbf{V} to the time domain

$$v(t) = 5.3 \cos(5t - 88^\circ) \text{ V}$$

Another approach by Ben Leung: You may first differential both sides of the original integrodifferential equation with respect to t to remove the integration term, and then use $d/dt \leftrightarrow j\omega$ and $d^2/dt^2 \leftrightarrow (j\omega)^2$.

P.P.9.8

For the capacitor,

$$\mathbf{V} = \mathbf{I} / (j\omega C), \quad \text{where } \mathbf{V} = 10 \angle 30^\circ, \quad \omega = 100$$

$$\mathbf{I} = j\omega C \mathbf{V} = (j100)(50 \times 10^{-6})(10 \angle 30^\circ)$$

$$\mathbf{I} = 50 \angle 120^\circ \text{ mA}$$

$$i(t) = 50 \cos(100t + 120^\circ) \text{ mA}$$

P.P.9.9

$$\mathbf{V}_s = 20 \angle 30^\circ, \omega = 10$$

$$\mathbf{Z} = 4 + j\omega L = 4 + j2$$

$$\mathbf{I} = \mathbf{V}_s / \mathbf{Z} = \frac{20 \angle 30^\circ}{4 + j2} = \frac{20 \angle 30^\circ (4 - j2)}{16 + 4} = 4.472 \angle 3.43^\circ$$

$$\mathbf{V} = j\omega L \mathbf{I} = j2 \mathbf{I} = (2 \angle 90^\circ)(4.472 \angle 3.43^\circ) = 8.944 \angle 93.43^\circ$$

Therefore, $v(t) = 8.944 \sin(10t + 93.43^\circ) \text{ V}$

$$i(t) = 4.472 \sin(10t + 3.43^\circ) \text{ A}$$

P.P.9.10

Let \mathbf{Z}_1 = impedance of the 1-mF capacitor in series with the 100- Ω resistor

\mathbf{Z}_2 = impedance of the 1-mF capacitor

\mathbf{Z}_3 = impedance of the 8-H inductor in series with the 200- Ω resistor

$$\mathbf{Z}_1 = 100 + \frac{1}{j\omega C} = 100 + \frac{1}{j(10)(1 \times 10^{-3})} = 80 - j100$$

$$\mathbf{Z}_2 = \frac{1}{j\omega C} = \frac{1}{j(10)(1 \times 10^{-3})} = -j100$$

$$\mathbf{Z}_3 = 200 + j\omega L = 200 + j(10)(8) = 200 + j80$$

$$\mathbf{Z}_{in} = \mathbf{Z}_1 + \mathbf{Z}_2 \parallel \mathbf{Z}_3 = \mathbf{Z}_1 + \mathbf{Z}_2 \mathbf{Z}_3 / (\mathbf{Z}_2 + \mathbf{Z}_3)$$

$$\mathbf{Z}_{in} = 100 - j100 + \frac{-j100 \times (200 + j80)}{-j100 + 200 + j80}$$

$$\mathbf{Z}_{in} = 100 - j100 + 49.52 - j95.04$$

$$\mathbf{Z}_{in} = [149.52 - j195] \Omega$$

P.P.9.11 In the frequency domain,
the voltage source is $\mathbf{V}_s = 20 \angle 100^\circ$
the 0.5-H inductor is $j\omega L = j(10)(0.5) = j5$
the $\frac{1}{20}$ -F capacitor is $\frac{1}{j\omega C} = \frac{1}{j(10)(1/20)} = -j2$

Let \mathbf{Z}_1 = impedance of the 0.5-H inductor in parallel with the 10- Ω resistor
and \mathbf{Z}_2 = impedance of the (1/20)-F capacitor

$$\mathbf{Z}_1 = 10 \parallel j5 = \frac{(10)(j5)}{10 + j5} = 2 + j4 \quad \text{and} \quad \mathbf{Z}_2 = -j2$$

$$\mathbf{V}_o = \mathbf{Z}_2 / (\mathbf{Z}_1 + \mathbf{Z}_2) \mathbf{V}_s$$



$$\mathbf{V}_o = \frac{-j2}{2 + j4 - j2} (50 \angle 30^\circ) = \frac{-j(50 \angle 30^\circ)}{1 + j} = \frac{50 \angle (30^\circ - 90^\circ)}{\sqrt{2} \angle 45^\circ}$$

$$\mathbf{V}_o = 35.36 \angle -105^\circ$$

$$v_o(t) = 35.36 \cos(10t - 105^\circ) \text{ V}$$

P.P.9.13 To show that the circuit in Fig. (a) meets the requirement, consider the equivalent circuit in Fig. (b).
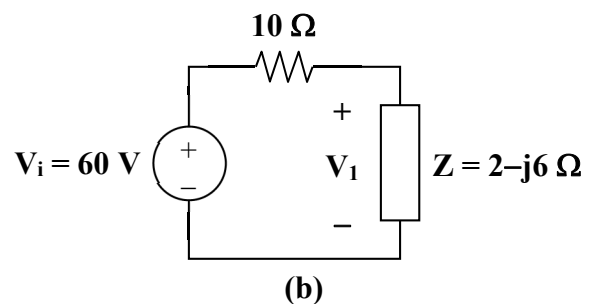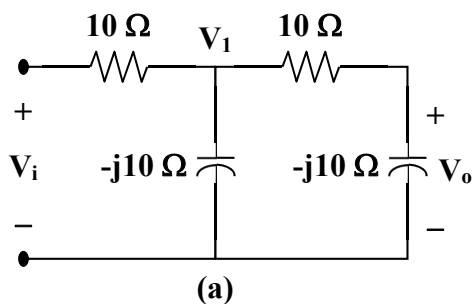
$$\mathbf{Z} = -j10 \parallel (10 - j10) = \frac{-j10(10 - j10)}{10 - j20} = \frac{-j(10 - j10)}{1 - j2} = 2 - j6 \Omega$$



$$\mathbf{V}_1 = \frac{2 - j6}{10 + 2 - j6} (60) = \frac{60}{3} (1 - j)$$

$$\mathbf{V}_o = \frac{-j10}{10 - j10} \mathbf{V}_1 = \left(\frac{-j}{1 - j} \right) \left(\frac{60}{3} \right) (1 - j) = -j20$$

$$\mathbf{V}_o = 20 \angle -90^\circ$$


This implies that the RC circuit provides a 90° lagging phase shift.
The output voltage is = **20 V**

P.P.9.14

the 1-mH inductor is $j\omega L = j(2\pi)(5 \times 10^3)(1 \times 10^{-3}) = j31.42$

the 2-mH inductor is $j\omega L = j(2\pi)(5 \times 10^3)(2 \times 10^{-3}) = j62.83$

Consider the circuit shown below.

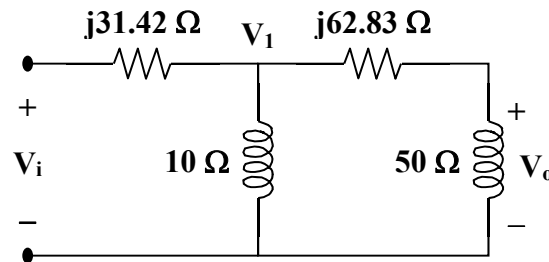

$$\mathbf{Z} = 10 \parallel (50 + j62.83) = \frac{(10)(50 + j62.83)}{60 + j62.83}$$

$$\mathbf{Z} = 9.205 + j0.833 = 9.243 \angle 5.17^\circ$$

$$\begin{aligned} \mathbf{V}_1 &= \mathbf{Z} / (\mathbf{Z} + j31.42) \mathbf{V}_i = \frac{9.243 \angle 5.17^\circ}{9.205 + j32.253} (10) \\ &= [(9.243 \angle 5.17^\circ) / (33.54 \angle 74.07^\circ)] 10 = 2.756 \angle -68.9^\circ \end{aligned}$$

$$\mathbf{V}_o = \frac{50}{50 + j62.83} \mathbf{V}_1 = \frac{50(2.756 \angle -68.9^\circ)}{80.297 \angle 51.49^\circ} = 1.7161 \angle -120.39^\circ$$

Therefore,

magnitude = **1.7161 V**

phase = **120.39°**

phase shift is **lagging**