

## EE1002 Principles of Electronic Engineering Test 2

### Part I: Multiple choice (16 questions, 3 points per question, total 48 minutes)

1. If  $(z - j)j = 2 + j$ , find  $z$ .

Answer:  $1 - j$

2. If  $\tan \alpha = 3/4$ , find  $\cos^2 \alpha + 2\sin 2\alpha$ .

Answer:  $64/25$


3. If  $y = x^6 \sin(1/x)$ , find the derivative of  $y$ .

Answer:  $6x^5 \sin(1/x) - x^4 \cos(1/x)$

4. Evaluate  $\int x e^{x^2} dx$


Answer:  $\frac{1}{2} e^{x^2} + c$

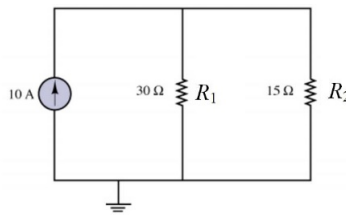5. Find the power consumed by resistors  $R_1$  and  $R_2$ .




Answer:  $P_1:P_2 = 1:2$ ;  $P_1 = 333 \text{ W}$

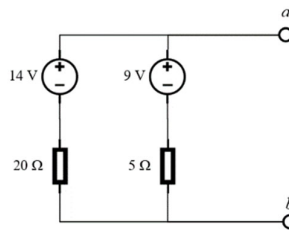6. Find the Norton equivalent with respect to terminals  $a-b$  in the following circuit.




Answer:  $R_N = 4 \Omega$ ,  $I_N = 2.5 \text{ A}$

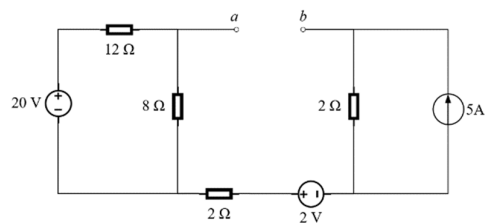7. Find the Thevenin equivalent with respect to terminals  $a-b$  in the following circuit.




Answer:  $R_{th} = 8.8 \Omega$ ,  $U_{ab} = 0 \text{ V}$

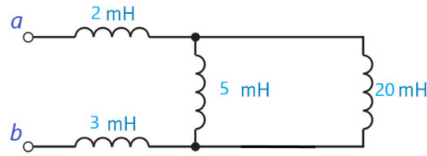8. For the four inductors connected in the following circuit, find the equivalent inductance  $L_{ab}$ .



**Answer:** 9 mH

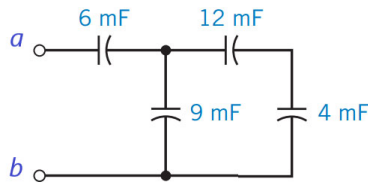
9. For the four capacitors connected as shown on the following circuit, find the equivalent capacitance  $C_{ab}$ .



**Answer:** 4 mF

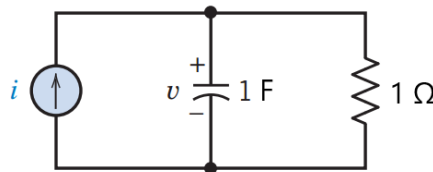
10. Find  $i$  for the following circuit if  $v = 5(1 - 2e^{-2t})$  V.

[Hint: You may use the KCL to solve the problem.]




**Answer:**  $5 + 10e^{-2t}$  A

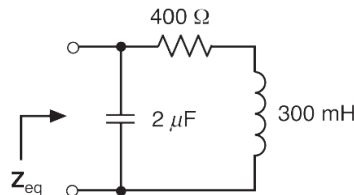11. Determine the equivalent impedance  $Z_{eq}$  of the following circuit at the frequency  $\omega = 1000$  rad/s.




**Answer:**  $599 \angle -26.5^\circ \Omega$

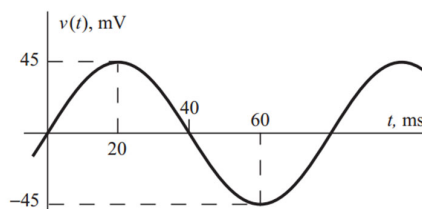12. Express the voltage in the following figure in the general form  $v(t) = A \cos(\omega t + \phi)$  V where  $A \geq 0$  and  $-180^\circ < \phi \leq 180^\circ$ .



**Answer:**  $v(t) = 0.045 \cos(25\pi t - 90^\circ)$  V

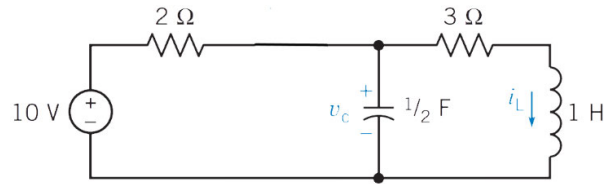13. Under steady-state dc conditions, find  $i_L$  and  $v_C$  of the following circuit.




**Answer:**  $i_L = 2 \text{ A}$ ,  $v_c = 6 \text{ V}$

14. Determine the capacitance of a capacitor when the voltage across it is  $v(t) = 12 \cos(500t - 45^\circ) \text{ V}$

and the current is  $i(t) = 3 \cos(500t + 45^\circ) \text{ mA}$ .


**Answer:**  $C = 0.5 \text{ uF}$

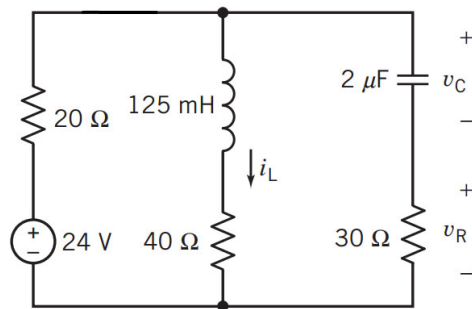15. Under the dc condition, find  $i_L$ ,  $v_C$ , and  $v_R$  in the following circuit.



**Answer:**  $i_L = 0.4 \text{ A}$ ,  $v_C = 16 \text{ V}$ , and  $v_R = 0 \text{ V}$

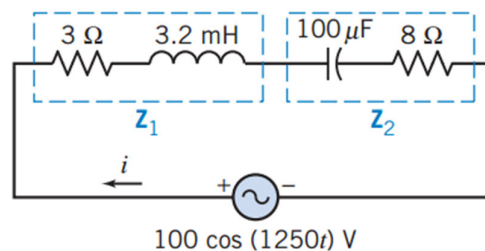16. In the following circuit, the impedances are given by  $Z_1 = 5 \angle 51.3^\circ \Omega$  and  $Z_2 = 8\sqrt{2} \angle -45^\circ \Omega$ . Find the current  $i(t)$ .



**Answer:**  $i(t) = 8.55 \cos(1250t + 20^\circ) \text{ A}$

**Part II: Written Questions (2 questions, 25 minutes per question, extra 6-minute upload time per question)**

### Question 1 (25 points)

(A) Fig. Q1(a) shows an ac circuit. The input voltage source is given by  $v_{s1}(t) = 12 \cos(1000t + 15^\circ) \text{ V}$ .

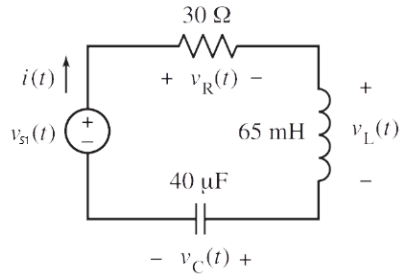


Fig. Q1(a)

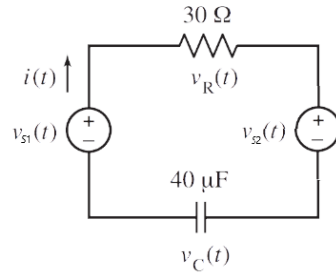


Fig. Q1(b)

Determine

- the impedances of the capacitor  $Z_C$ ,  $Z_L$ , and  $Z_R$ ; (3 points)
- the voltages  $V_R$ ,  $V_L$ , and  $V_C$ ; (6 points)
- the current  $i(t)$  and its rms value; and (4 points)
- the new current  $i(t)$  and its rms value if the inductor in Fig. Q1(a) is replaced by a second voltage source  $v_{s2}(t) = 5 \cos(1000t)$  V, as shown in Fig. Q1(b). (6 points)

(B) If a current is given by  $i(t) = A + B \cos(\omega t)$ , where A and B are constants, drive the formula of the rms value of  $i(t)$ . (6 points)

**Answer:**

**(A)**

**(a)  $\omega = 1000 \text{ rad/s}$**

$$\mathbf{Z_C = -j25 \Omega}$$

$$\mathbf{Z_L = j65 \Omega}$$

$$\mathbf{Z_R = 30 \Omega}$$

**(b)  $V_s = 12 \angle 15^\circ \text{ V}$**

$$\mathbf{V_R = 7.2 \angle -38.13^\circ \text{ V}}$$

$$\mathbf{V_L = 15.6 \angle 51.87^\circ \text{ V}}$$

$$\mathbf{V_C = 6 \angle -128.13^\circ \text{ V}}$$

**(c)  $i(t) = 0.24 \cos(1000t - 38.13^\circ) \text{ A}$**

$$I_{RMS} \approx \frac{0.24}{\sqrt{2}} = 0.17 \text{ A}$$

(d) For  $V_{s1}$  Source:

$$I_1 = 0.31 \angle 54.8^\circ$$

For  $V_{s2}$  Source:

$$I_1 = 0.13 \angle 39.8^\circ$$

$$i(t) = 0.31 \cos(1000t + 54.8^\circ) - 0.13 \cos(1000t + 39.8^\circ)$$

$$i(t) = 0.31 \cos(1000t + 54.8^\circ) + 0.13 \cos(1000t - 140^\circ)$$

$$i(t) = 0.19 \cos(1000t + 65^\circ)$$

$$I_{RMS} = \sqrt{0.19^2/2} = 0.13 \text{ A}$$

Power cannot be calculated by superposition.

$$\therefore \text{A traditional } \underline{\text{wrong}} \text{ answer is } I_{RMS} = \sqrt{\frac{0.31^2}{2} + \frac{0.13^2}{2}} = 0.24 \text{ A}$$

(B)

$$P = I_{RMS}^2 R \rightarrow I_{RMS} = \sqrt{A^2 + \frac{B^2}{2}}$$

## Question 2

(A) Fig. Q2(a) shows a dc circuit. The input voltage source is 9 V.

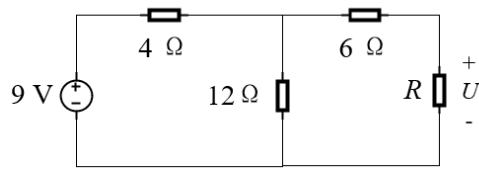


Fig. Q2(a)

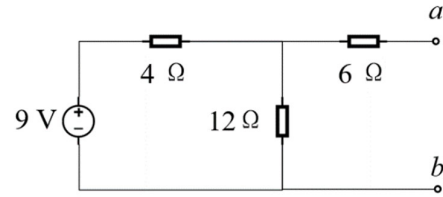


Fig. Q2(b)

Find

- (a) the voltage  $U$  and power of  $R$  if  $R = 20\ \Omega$ ; and (5 points)
- (b) the resistance  $R$  by using mesh analysis if  $U = 4.5\ \text{V}$ . (10 points)
- (B) If the resistor  $R$  is removed as shown in Fig. Q2(b), find the Thevenin equivalent circuit at terminals  $a$ - $b$ . (10 points)

**Answer:**

**(A):**

**(a)  $U = 4.66\ \text{V}$**

**$P = 1.08\ \text{W}$**

**(b)  $R = 18\ \Omega$**

**(B)  $V_{th} = 6.75\ \text{V}$**

**$R_{th} = 9\ \Omega$**