

EE1001 Adder tutorial (Week 10)

KF Tsang

Tutorial (Week 10)

■ **Compute $6 + 7$ using the logic circuits.**

- (1) How many adders are needed?**
- (2) Which adder should be adopted? Half or full?**
- (3) Work out the input and output of each adder?**
- (4) Draw the logic circuits.**