

Practice questions for EE1002

Multiple-choice question part:

Note: For all the practice questions below, reference answers are given. The answers are marked with

answer

If $z = 3 - 2j$, please give the value of zz^* where z^* is the conjugate of z .

answer

- ☐ 13
- ☐ 5
- ☐ $5-12j$
- ☐ $13-12j$

Express $z = -1 - j$ in polar form.

answer

- ☐ $\sqrt{2}\angle -135^\circ$
- ☐ $\sqrt{2}\angle 135^\circ$
- ☐ $\sqrt{2}\angle 45^\circ$
- ☐ $\sqrt{2}\angle -45^\circ$

Find the rate of change of $y(x) = 4 + 2x - 3x^2$ at $x = 3$.

answer

- ☐ -16
- ☐ 16
- ☐ 12
- ☐ -12

If $y = 2\ln(\sqrt{x} + 6)$ please find the derivative of y .

answer

- $\frac{1}{x+6\sqrt{x}}$
- $\frac{1}{\sqrt{x}}$
- $\frac{2}{\sqrt{x}+6}$
- $\frac{1}{x-6\sqrt{x}}$

If $y = e^{2x} \sin 3x - \cos x$, please find $y'(\frac{\pi}{6})$.

answer

$$2e^{\frac{\pi}{3}} + \frac{\sqrt{3}}{2}$$

$$3e^{\frac{\pi}{6}} + \frac{\sqrt{3}}{2}$$

$$2e^{\frac{\pi}{3}} - \frac{\sqrt{3}}{2}$$

$$\frac{5\sqrt{2}}{2}e^{\frac{\pi}{3}} + \frac{\sqrt{3}}{2}$$

If $y = \frac{\cos(x^2)}{x^3}$, please find the derivative of y .

answer

$$-2x^{-2} \sin(x^2) - 3x^{-4} \cos(x^2)$$

$$2x^{-2} \cos(x^2) + 3x^{-4} \cos(x^2)$$

$$-2x^{-2} \cos(x^2) + 3x^{-4} \cos(x^2)$$

$$2x^{-2} \sin(x^2) + 3x^{-4} \cos(x^2)$$

Evaluate $\int \cos^3 x dx$.

answer

$$\sin x - \frac{\sin^3 x}{3} + c$$

$$\frac{\cos^3 x}{3} + c$$

$$-\sin x \frac{\cos^3 x}{3} + c$$

$$\sin x \frac{\cos^3 x}{3} + c$$

Solve the differential equation $\frac{dy}{dx} = x^3 e^{-y}$ with the initial condition of $y(0) = \frac{1}{2}$ for y .

Answer

$$y = \ln\left(\frac{1}{4}x^4 + e^{\frac{1}{2}}\right)$$

$$y = \ln\left(x^3 + \frac{1}{2}e\right)$$

$$y = \ln\left(3x^2 + e^{\frac{1}{2}}\right)$$

$$y = \ln\left(\frac{1}{4}x^4 + \frac{1}{2}e\right)$$

A sinusoidal function has an amplitude of $2\sqrt{2}$, a frequency of **3** and phase of $\frac{2\pi}{5}$. State a sinusoidal form of the function.

Answer


$$2\sqrt{2}\sin(6\pi t + \frac{2\pi}{5})$$

$$8\sin(6\pi t + \frac{2\pi}{5})$$

$$2\sqrt{2}\sin(\frac{2\pi}{3}t + \frac{2\pi}{5})$$

$$8\sin(\frac{2\pi}{3}t + \frac{2\pi}{5})$$

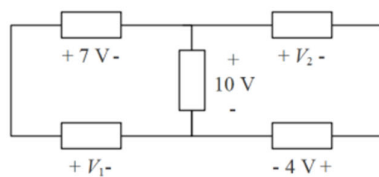In the following circuit, calculate V_1 and V_2 .



Answer


$$V_1 = 17 \text{ V}, V_2 = 6 \text{ V}$$

$$V_1 = 3 \text{ V}, V_2 = 6 \text{ V}$$

$$V_1 = 17 \text{ V}, V_2 = -6 \text{ V}$$

$$V_1 = -17 \text{ V}, V_2 = -6 \text{ V}$$

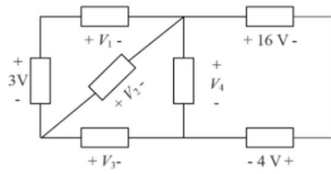Obtain v_1 , v_2 , v_3 , and v_4 ($v_2 : v_3 = 3:1$) in the following circuit.



answer


$$v_1 = -27 \text{ V}, v_2 = -30 \text{ V}, v_3 = -10 \text{ V}, v_4 = 20 \text{ V}$$

$$v_1 = -15 \text{ V}, v_2 = -18 \text{ V}, v_3 = -6 \text{ V}, v_4 = 12 \text{ V}$$

$$v_1 = 33 \text{ V}, v_2 = 30 \text{ V}, v_3 = 10 \text{ V}, v_4 = 20 \text{ V}$$

$$v_1 = -15 \text{ V}, v_2 = 18 \text{ V}, v_3 = 6 \text{ V}, v_4 = 12 \text{ V}$$

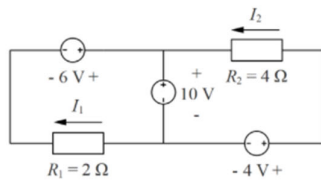From the following circuit, find I_1 , I_2 , and the power dissipated by the resistor R_1 , R_2 .



answer


$$I_1 = -2 \text{ A}, I_2 = -1.5 \text{ A}, P_1 : P_2 = 8:9$$

$$I_1 = 2 \text{ A}, I_2 = 1.5 \text{ A}, P_1 : P_2 = 8:9$$

$$I_1 = -8 \text{ A}, I_2 = -3.5 \text{ A}, P_1 : P_2 = 128:49$$

$$I_1 = 8 \text{ A}, I_2 = 3.5 \text{ A}, P_1 : P_2 = 128:49$$

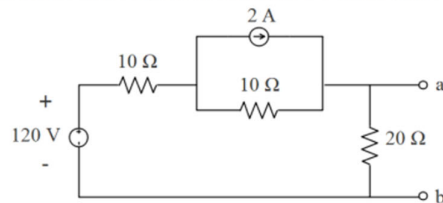Find the Norton equivalent circuit with respect to terminals $a-b$ in the following circuit.



answer


$$R_N = 10 \text{ ohms}; I_N = 7 \text{ A}$$

$$R_N = 10 \text{ ohms}; I_N = 5 \text{ A}$$

$$R_N = 40 \text{ ohms}; I_N = 7 \text{ A}$$

$$R_N = 40 \text{ ohms}; I_N = 5 \text{ A}$$

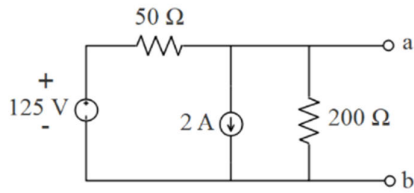Determine the Thevenin equivalent circuit with respect to terminals a - b in the following circuit.



answer


$$R_{th} = 40 \, \Omega, V_{th} = 20 \, V$$

$$R_{th} = 40 \, \Omega, V_{th} = 180 \, V$$

$$R_{th} = 250 \, \Omega, V_{th} = 20 \, V$$

$$R_{th} = 250 \, \Omega, V_{th} = 180 \, V$$

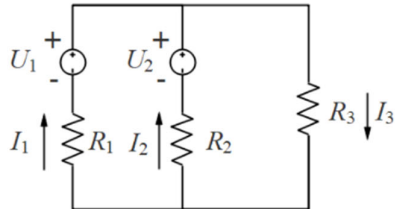If $U_1 = 40 \, V$, $U_2 = 20 \, V$, $R_1 = R_2 = 4 \, \Omega$, and $R_3 = 13 \, \Omega$, apply the Thevenin's theorem to determine I_3 in the following circuit.



answer


$$2 \, A$$

$$2.5 \, A$$

$$15 \, A$$

$$0.67 \, A$$

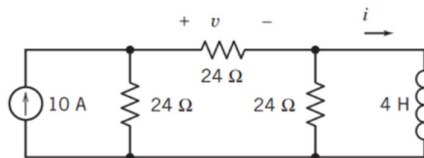Under steady-state dc conditions, find i and v in the following circuit.



answer


$$i = 5 \, A, v = 120 \, V$$

$$i = 3.3 \, A, v = -120 \, V$$

$$i = 3.3 \, A, v = 120 \, V$$

$$i = 5 \, A, v = -120 \, V$$

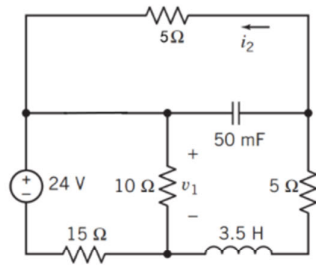Under steady-state dc conditions, find v_1 and i_2 in the following circuit.



answer


$$v_1 = 6 \text{ V}, i_2 = -0.6 \text{ A}$$

$$v_1 = 6 \text{ V}, i_2 = 0.6 \text{ A}$$

$$v_1 = 9.6 \text{ V}, i_2 = -0.96 \text{ A}$$

$$v_1 = 9.6 \text{ V}, i_2 = 0.96 \text{ A}$$

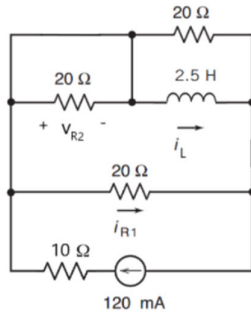Under steady-state dc conditions, find i_{R1} , v_{R2} and i_L in the following circuit.



answer


$$i_{R1} = 0 \text{ mA}, v_{R2} = 0 \text{ V}, i_L = 120 \text{ mA}$$

$$i_{R1} = 60 \text{ mA}, v_{R2} = 0 \text{ V}, i_L = 0 \text{ mA}$$

$$i_{R1} = 60 \text{ mA}, v_{R2} = 1.2 \text{ V}, i_L = 60 \text{ mA}$$

$$i_{R1} = 80 \text{ mA}, v_{R2} = 0.8 \text{ V}, i_L = 0 \text{ mA}$$

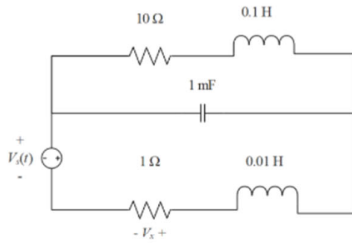() Given that $V_s(t) = 10 \sin(100t + 90^\circ)$, determine $V_x(t)$.



answer


$5\angle 0^\circ$

$5\angle 90^\circ$

$0.33\angle 0^\circ$

$0.33\angle 90^\circ$

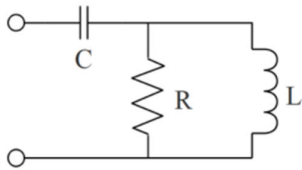() Given that $R = 5 \Omega$, $L = 3 \text{ H}$, $C = 1/3 \text{ F}$, if the net impedance is resistive, find the required frequency of the circuit?



answer


$\omega = 1.25 \text{ rad/s}$

$\omega = 1 \text{ rad/s}$

$\omega = 2 \text{ rad/s}$

$\omega = 0.5 \text{ rad/s}$

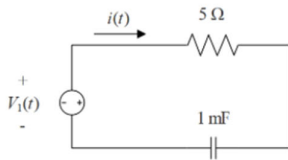() If $V_1(t) = 10 \cos(200t)$, find $i(t)$.



answer


$i(t) = \sqrt{2} \cos(200t + 45^\circ)$

$i(t) = 10 \cos(200t + 45^\circ)$

$i(t) = 2 \cos(200t)$

$i(t) = \sqrt{2} \cos(200t)$

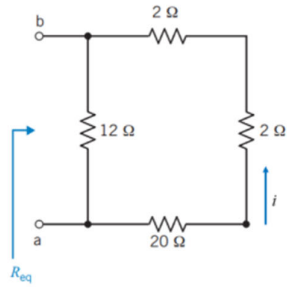For the following circuit, find R_{eq} and i if $V_{ab} = 40$ V.



answer


$$R_{eq} = 8 \, \Omega, i = 5/3 \, A$$

$$R_{eq} = 12 \, \Omega, i = 10/9 \, A$$

$$R_{eq} = 9 \, \Omega, i = 40/27 \, A$$

$$R_{eq} = 36 \, \Omega, i = 20/27 \, A$$

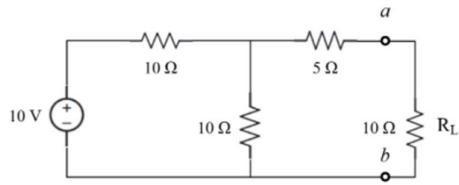For the following circuit, find the Thevenin equivalent circuit with respect to terminals a - b .



answer


$$R_{th} = 10 \, \Omega, V_{th} = 5 \, V$$

$$R_{th} = 16 \, \Omega, V_{th} = 3.75 \, V$$

$$R_{th} = 20 \, \Omega, V_{th} = 5 \, V$$

$$R_{th} = 25 \, \Omega, V_{th} = 10 \, V$$

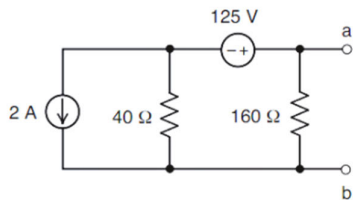For the following circuit, find the Norton equivalent with respect to terminals a - b .



answer


$$R_N = 32 \, \Omega; I_N = 1.125 \, A$$

$$R_N = 40 \, \Omega; I_N = 2.5 \, A$$

$$R_N = 160 \, \Omega; I_N = 1.5 \, A$$

$$R_N = 200 \, \Omega; I_N = 1 \, A$$

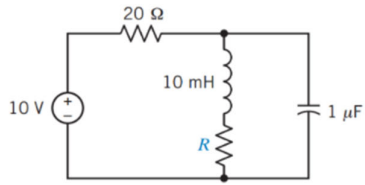For the following circuit, select a value of R so that the energy stored in the inductor is equal to that stored in the capacitor at its steady-state dc state.



answer


$R = 100 \, \Omega$

$R = 10000 \, \Omega$

$R = 20 \, \Omega$

$R = 10 \, \Omega$

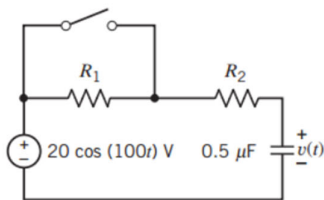When the switch in the following circuit is open, the time constant is 10 ms. After the switch is closed, the time constant becomes 5 ms. Determine the values of the resistances R_1 and R_2 . (Hint: Time constant is given by $\tau = RC$)



answer


$R_1 = 10 \, \text{k}\Omega$, and $R_2 = 10 \, \text{k}\Omega$.

$R_1 = 20 \, \text{k}\Omega$, and $R_2 = 0 \, \text{k}\Omega$.

$R_1 = 10 \, \text{k}\Omega$, and $R_2 = 30 \, \text{k}\Omega$.

$R_1 = 20 \, \text{k}\Omega$, and $R_2 = 20 \, \text{k}\Omega$.

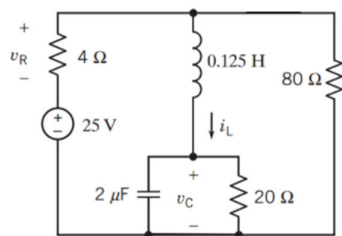Under the steady-state dc condition, find i_L , v_C , and v_R in the following circuit.



answer

$i_L = 1 \, \text{A}$, $v_C = 20 \, \text{V}$, and $v_R = -5 \, \text{V}$

$i_L = 1 \, \text{A}$, $v_C = 20 \, \text{V}$, and $v_R = 5 \, \text{V}$

$i_L = 0.25 \, \text{A}$, $v_C = 5 \, \text{V}$, and $v_R = -20 \, \text{V}$

$i_L = 0.25 \, \text{A}$, $v_C = 5 \, \text{V}$, and $v_R = 20 \, \text{V}$

Long question part:

(A) Q2(a) shows a dc circuit. The input voltage source is 9 V.

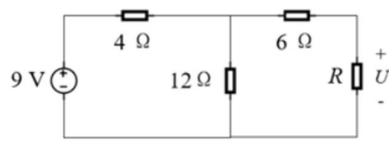


Fig. Q2(a)

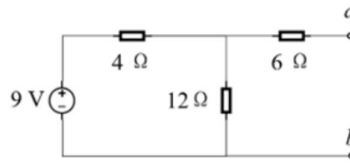


Fig. Q2(b)

Find

- (a) the voltage U and power of R if $R = 20\ \Omega$; and (5 points)
- (b) the resistance R by using mesh analysis if $U = 4.5\text{ V}$. (10 points)
- (B) If the resistor R is removed as shown in Fig. Q2(b), find the Thevenin equivalent circuit at terminals a - b . (10 points)

Solution:

(a)

When $R = 20\ \Omega$, $R_{eq} = (R + 6) \parallel 12 + 4 = 8.21 + 4 = 12.21\ \Omega$


Based on voltage division method,

$$U = 9 \cdot \frac{8.21}{12.21} \cdot \frac{20}{20 + 6} = 4.66\text{ V}$$

Then

$$P = \frac{U^2}{R} = 1.08\text{ W}$$

(b)

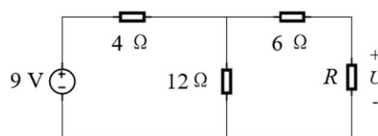


For left mesh, $9 = 4i_1 + 12(i_1 - i_2)$

For right mesh, $0 = 6i_2 + 12(i_2 - i_1) + 4.5$

Then, $i_1 = 0.75\text{ A}$ and $i_2 = 0.25\text{ A}$. Given $i_2 R = 4.5\text{ V}$, we can get $R = 18\ \Omega$

(c)

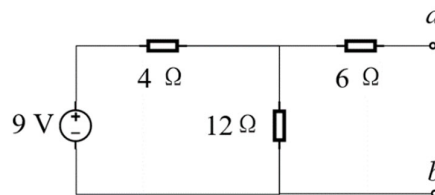

$$V_{th} = 9 \cdot \frac{12}{12 + 4} = 6.75\text{ V}$$

$$R_{th} = 4 \parallel 12 + 6 = 9\ \Omega$$

(A) Fig. Q1(a) shows an ac circuit. The input voltage source is given by $v_{s1}(t) = 12\cos(1000t + 15^\circ)$ V.

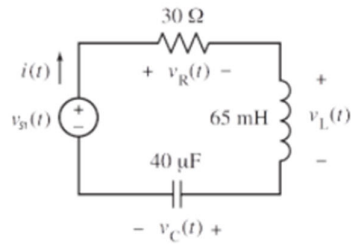


Fig.Q1(a)

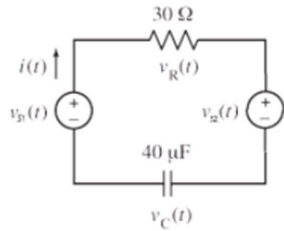


Fig.Q1(b)

Determine

- the impedances of the capacitor Z_C , Z_L , and Z_R ; (3 points)
 - the voltages V_R , V_L , and V_C ; (6 points)
 - the current $i(t)$ and its rms value; and (4 points)
 - the new current $i(t)$ and its rms value if the inductor in Fig. Q1(a) is replaced by a second voltage source $v_{s2}(t) = 5\cos(1000t)$ V, as shown in Fig. Q1(b). (6 points)
- (B) If a current is given by $i(t) = A + B\cos(\omega t)$, where A and B are constants, drive the formula of the rms value of $i(t)$. (6 points)

Solution:

(A)(a)

$$\begin{aligned}\omega &= 1000 \text{ rad/s} \\ Z_C &= \frac{1}{j\omega C} = \frac{1}{j1000(40 \times 10^{-6})} = -j25 \Omega \\ Z_L &= j\omega L = j1000(65 \times 10^{-3}) = j65 \Omega \\ Z_R &= R = 30 \Omega\end{aligned}$$

(A)(b)

$$V_s = 12 \cos(1000t + 15^\circ) \text{ V} \quad \text{Phasor form: } V_s = 12 \angle 15^\circ \text{ V} \quad \text{and } \omega = 1000 \text{ rad/s}$$

Based on the voltage divider rule,

$$\begin{aligned}V_R &= V_s \frac{Z_R}{Z_R + Z_C + Z_L} = Z_R \frac{30}{30 + j40} = \frac{12 \angle 15^\circ \cdot 30}{50 \angle 53.13^\circ} = 7.2 \angle -38.13^\circ \text{ V} \\ V_L &= V_s \frac{Z_L}{Z_R + Z_C + Z_L} = Z_R \frac{j65}{30 + j40} = \frac{12 \angle 15^\circ \cdot 65 \angle 90^\circ}{50 \angle 53.13^\circ} = 15.6 \angle 51.87^\circ \text{ V} \\ V_C &= V_s \frac{Z_C}{Z_R + Z_C + Z_L} = Z_R \frac{-j25}{30 + j40} = \frac{12 \angle 15^\circ \cdot 25 \angle -90^\circ}{50 \angle 53.13^\circ} = 6 \angle -128.13^\circ \text{ V}\end{aligned}$$

Then,

$$\begin{aligned}
 V_R &= 7.2 \cos(1000t - 38.13^\circ) \text{ V} \\
 V_L &= 15.6 \cos(1000t + 51.87^\circ) \text{ V} \\
 V_C &= 6 \cos(1000t - 128.13^\circ) \text{ V}
 \end{aligned}$$

(A)(c)

$$\begin{aligned}
 I &= \frac{V_S}{Z} = \frac{V_S}{Z_R + Z_C + Z_L} = \frac{12\angle 15^\circ}{30 + j40} = \frac{12\angle 15^\circ}{50\angle 53.13^\circ} = 0.24\angle -38.13^\circ \text{ A} \\
 i(t) &= 0.24 \cos(1000t - 38.13^\circ) \text{ A} \\
 i_{RMS} &= \frac{0.24}{\sqrt{2}} = 0.17 \text{ A}
 \end{aligned}$$

(A)(d)

$$\begin{aligned}
 V_{s1} &= 12 \cos(1000t + 15^\circ) \text{ V} \quad \text{Phasor form: } V_{s1} = 12\angle 15^\circ \text{ V and } \omega = 1000 \text{ rad/s} \\
 V_{s2} &= 5 \cos(1000t) \text{ V} \quad \text{Phasor form: } V_{s2} = 5\angle 0^\circ \text{ V and } \omega = 1000 \text{ rad/s}
 \end{aligned}$$

$$Z_R = R = 30 \Omega \quad Z_C = -j25 \Omega$$

Based on superposition,

For only V_{s1} source,

$$I_1 = \frac{V_{s1}}{Z} = \frac{V_{s1}}{Z_R + Z_C} = \frac{12\angle 15^\circ}{30 - j25} = \frac{12\angle 15^\circ}{39\angle -39.8^\circ} = 0.31\angle 54.8^\circ \text{ A}$$

For only V_{s2} source,

$$I_2 = \frac{V_{s2}}{Z} = \frac{V_{s2}}{Z_R + Z_C} = \frac{5\angle 0^\circ}{30 - j25} = \frac{5\angle 0^\circ}{39\angle -39.8^\circ} = 0.13\angle 39.8^\circ \text{ A}$$

V_{s1} and V_{s2} are in opposite directions, so

$$i(t) = 0.31 \cos(1000t + 54.8^\circ) - 0.13 \cos(1000t + 39.8^\circ) \text{ A}$$

$$i_{RMS} = \sqrt{\frac{0.31^2}{\sqrt{2}^2} + \frac{0.13^2}{\sqrt{2}^2}} = 0.34 \text{ A}$$

(B)

Assuming a resistor R with the current $i(t) = A + B\cos(\omega t)$,

$$i(t) = i_{ac}(t) + i_{dc}(t) = B\cos(\omega t) + A$$

The power of the resistor $P = P_{ac} + P_{dc}$

$$P_{dc} = i_{dc}^2 R = A^2 R$$

$$P_{ac} = \left(\frac{i_{ac}}{\sqrt{2}}\right)^2 R = \frac{B^2}{2} R$$

And

$$P = i_{RMS}^2 R$$

$$\text{Then } i_{RMS}^2 = A^2 + \frac{B^2}{2} \text{ hence, } i_{RMS} = \sqrt{A^2 + \frac{B^2}{2}}$$

(a) Find $\frac{dy}{dx}$ if $y = e^{3x+5} \sin^2(2x+1)$. (5 points)

(b) Evaluate $\int \frac{e^{3\sqrt{x}}}{\sqrt{x}} dx$. (5 points)

(c) Find $\cos(\alpha + \beta)$ when

- (1) $\tan \alpha \tan \beta = 2$, and $\cos(\alpha - \beta) = 3/5$; (4 points)
(Hint: $\tan x = \sin x / \cos x$)
- (2) $\cos \alpha + \cos \beta = 1/2$, and $\sin \alpha - \sin \beta = 1/3$. (4 points)
(Hint: $\sin^2 x + \cos^2 x = 1$)

(d) Fig. Q1(d) shows a periodic voltage $v_c(t)$ across a capacitor $C = 1 \text{ mF}$.

- (1) Find the rms value of $v_c(t)$. (5 points)
- (2) Sketch the capacitor current $i_c(t)$ passing through the capacitor as a function of t . (3 points)

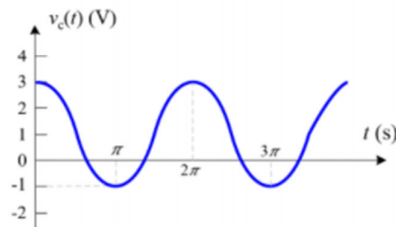


Fig. Q1(d)

Reference solution:

(a)

$$\frac{dy}{dx} = e^{3x+5} (2\sin(2x+1))(2\cos(2x+1)) + 3e^{3x+5} \sin^2(2x+1)$$

$$\frac{dy}{dx} = 4e^{3x+5} \sin(2x+1)\cos(2x+1) + 3e^{3x+5} \sin^2(2x+1)$$

$$\frac{dy}{dx} = e^{3x+5} \sin(2x+1)(4\cos(2x+1) + 3\sin(2x+1))$$

or

$$\frac{dy}{dx} = e^{3x+5} (3\sin^2(2x+1) + 2\sin(4x+2))$$

(b)

$$\therefore (\sqrt{x})' = \frac{1}{2\sqrt{x}}$$

$$\therefore \int \frac{e^{3\sqrt{x}}}{\sqrt{x}} dx = 2 \int e^{3\sqrt{x}} d\sqrt{x}$$

$$\text{Set } t = \sqrt{x}$$

$$\therefore \int \frac{e^{3\sqrt{x}}}{\sqrt{x}} dx = 2 \int e^{3t} dt = \frac{2}{3} \int e^{3t} d3t = \frac{2}{3} e^{3t} + C$$

$$\therefore \int \frac{e^{3\sqrt{x}}}{\sqrt{x}} dx = \frac{2}{3} e^{3\sqrt{x}} + C$$

(c)(1)

$$\tan \alpha \cdot \tan \beta = 2 = \frac{\sin \alpha \cdot \sin \beta}{\cos \alpha \cdot \cos \beta} \Rightarrow \sin \alpha \cdot \sin \beta = 2 \cos \alpha \cdot \cos \beta \quad (1)$$

$$\cos(\alpha - \beta) = \cos \alpha \cdot \cos \beta + \sin \alpha \cdot \sin \beta = \frac{3}{5} \quad (2)$$

From (1) and (2), Obtain

$$\cos \alpha \cdot \cos \beta = \frac{1}{5} \quad \sin \alpha \cdot \sin \beta = \frac{2}{5} \quad (3)$$

Then,

$$\cos(\alpha + \beta) = \cos \alpha \cdot \cos \beta - \sin \alpha \cdot \sin \beta = \frac{1}{5} - \frac{2}{5} = -\frac{1}{5}$$

(c)(2)

$$\cos \alpha + \cos \beta = \frac{1}{2} \Rightarrow (\cos \alpha + \cos \beta)^2 = \cos^2 \alpha + \cos^2 \beta + 2 \cos \alpha \cdot \cos \beta = \frac{1^2}{2^2} = \frac{1}{4} \quad (4)$$

$$\sin \alpha - \sin \beta = \frac{1}{3} \Rightarrow (\sin \alpha - \sin \beta)^2 = \sin^2 \alpha + \sin^2 \beta - 2 \sin \alpha \cdot \sin \beta = \frac{1^2}{3^2} = \frac{1}{9} \quad (5)$$

Apply (4) + (5), obtain

$$\cos^2 \alpha + \cos^2 \beta + 2 \cos \alpha \cdot \cos \beta + \sin^2 \alpha + \sin^2 \beta - 2 \sin \alpha \cdot \sin \beta = \frac{1}{4} + \frac{1}{9} = \frac{13}{36}$$

$$2 \cos \alpha \cdot \cos \beta - 2 \sin \alpha \cdot \sin \beta = \frac{13}{36} - 2 = -\frac{59}{36}$$

Then,

$$\cos(\alpha + \beta) = \cos \alpha \cdot \cos \beta - \sin \alpha \cdot \sin \beta = -\frac{59}{72}$$

(d)(1)

Method A:

For $t \geq 0$ s,

$$v_c(t) = 1 + 2 \cos t = V_{dc}(t) + v_{ac}(t)$$

$$v_{RMS} = \sqrt{V_{dc-RMS}^2 + v_{ac-RMS}^2}$$

$$V_{dc-RMS} = 1 \text{ V}$$

$$v_{ac-RMS} = \frac{2}{\sqrt{2}}$$

$$v_{RMS} = \sqrt{1^2 + \left(\frac{2}{\sqrt{2}}\right)^2} = \sqrt{3} \text{ V} = 1.732 \text{ V}$$

Method B:

$$v_{RMS} = \sqrt{\frac{1}{T} \int_0^T v_c^2 dt}$$

For the current in the following figure, $T = 2\pi$ s, $\omega = 1$

$$\begin{aligned} V_c(t) &= V_{dc}(t) + v_{ac}(t) = 1 + 2 \cos t \\ \therefore v_{RMS} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (4 \cos^2 t + 4 \cos t + 1) dt} \\ &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (2 \cos 2t + 4 \cos t + 3) dt} \\ &= \sqrt{\frac{1}{2\pi} \cdot (\sin 2t + 4 \sin t + 3t) \Big|_0^{2\pi}} \\ &= \sqrt{\frac{6\pi}{2\pi}} = \sqrt{3} V = 1.732 V \end{aligned}$$

(d)(2)

Voltage in one period is given by

$$v_c(t) = 1 + 2 \cos(t) \quad (t \geq 0) \text{ V}$$

Based on $i = C dv/dt$, where $C = 10^{-3}$ F, obtain

$$i_c(t) = C \frac{dv}{dt} = -2 \sin(t) \quad (t > 0) \text{ mA}$$

