

EE2000 Logic Circuit Design

Chapter 5- VHDL

Basic Logic Gates using VHDL

- 5.1 Hardware Description Language (HDL)
- 5.2 VHDL Code Structure
- 5.3 Basic Logic Gates Using VHDL
- 5.4 VHDL Data Types
- 5.5 VHDL Operators - Boolean / Relational / Arithmetic
- 5.6 VHDL Syntax for Boolean expressions / Logic Circuits
- 5.7 VHDL Module
- 5.8 VHDL Format & Syntax

5.1 Hardware Description Language (HDL)


- Two popular HDLs—VHDL and Verilog
- VHDL - Very High Speed Integrated Circuit Hardware Description Language (VHSIC-HDL).
- Developed by U.S. Department of Defense (DoD).
- Standardized by IEEE.
- Widely used to translate designs into bit patterns that configure the actual devices.

5.1 Hardware Description Language (HDL)

- HDL - Hardware Description Language is a software programming language that is used to model a piece of hardware
- VHDL is an HDL used to describe a digital system at several different levels: behavioral, data flow, and structural.
- VHDL leads naturally to a top-down design methodology.
- The Vivado design tool from Xilinx will be used to design simulation and synthesize the logic circuit/system in this course.




5.2 VHDL Code Structure - Illustration

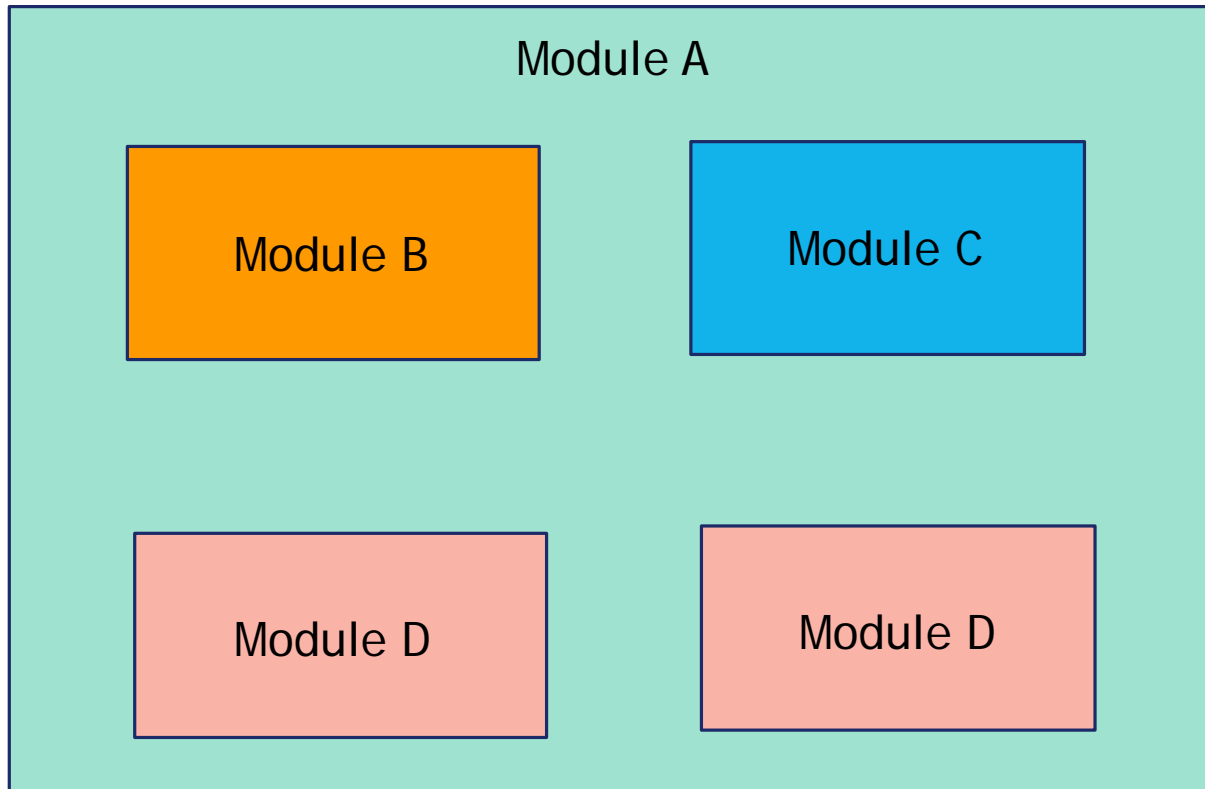

Like breaking down a complicated circuit into a number of smaller circuits, with each module describe a smaller circuit. The modules are connected through **ports** to form the final circuit.

5.2 VHDL Code Structure - Illustration

 

5.2 VHDL Code Structure

```
{Library      Declaration}  
{Entity      Declaration}  
{Architecture Declaration}
```


Library declaration: locate the system library, IEEE Standard library is often included in the VHDL code. STD_LOGIC_1164 contains STD_LOGIC types & related functions. You can create your own library.

Entity declaration: defines the external interface to the current design [input (port) / output (port)].

Architecture declaration: describes the internal circuit of the corresponding entity [logic circuit].

 5.2 VHDL Code Structure - Illustration

```
library ieee;  
use ieee.std_logic_1164.all;
```



```
entity logic_c is  
    port(  
        x1,x2,x3,x4,x5 : in  bit;  
        f               : out bit  
    );  
end logic_c;
```

```
architecture Behavior of logic_c is  
begin  
    f <=((x1 or x2) and (x3 and x4) or x5);  
end Behavior;
```


5.3 Basic Logic Gates using VHDL

Circuit description with an architecture

The description of the **logic circuit operation** as in “**Functional code**” is enclosed by **BEGIN** and **END**.

```
ARCHITECTURE XX of AA IS
```

```
BEGIN
```

```
    Functional code
```

```
END XX;
```

```
ARCHITECTURE YY of AA IS
```

```
BEGIN
```

```
    Functional code
```


```
END YY;
```

AA: entity name

XX, YY: architecture name

5.3 Basic Logic Gates using VHDL

Example:

 

**architecture Behavior of nand_gate is
begin**

```
f <= not (x1 and x2);
```

end Behavior;

Alternative:

```
f <= x1 nand x2;
```

5.3 Basic Logic Gates using VHDL

VHDL is “case insensitive”.


```
architecture Behavior of nand_gate is  
begin  
    f <= x1 nand x2;  
end Behavior;
```

The above code is identical to the following:

```
ARCHITECTURE Behavior of NAND_GATE IS  
BEGIN  
    F <= x1 NAND x2;  
END Behavior;
```

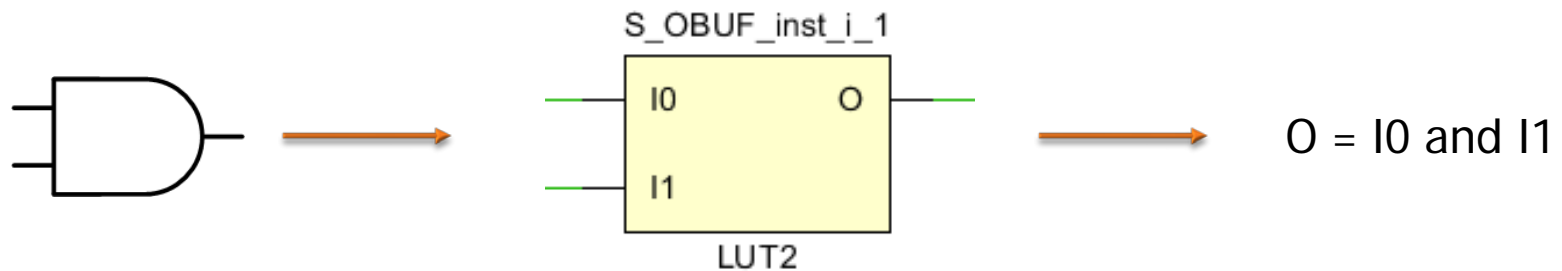5.3 Basic Logic Gates using VHDL


VHDL language translates logic circuit into Look-up Table



A typical Schematic Diagram for a logic gate in the CAD tool -
e.g. Xilinx Vivado Software

I0, I1, O internal port names are generated by Vivado software

5.4 VHDL Data Types

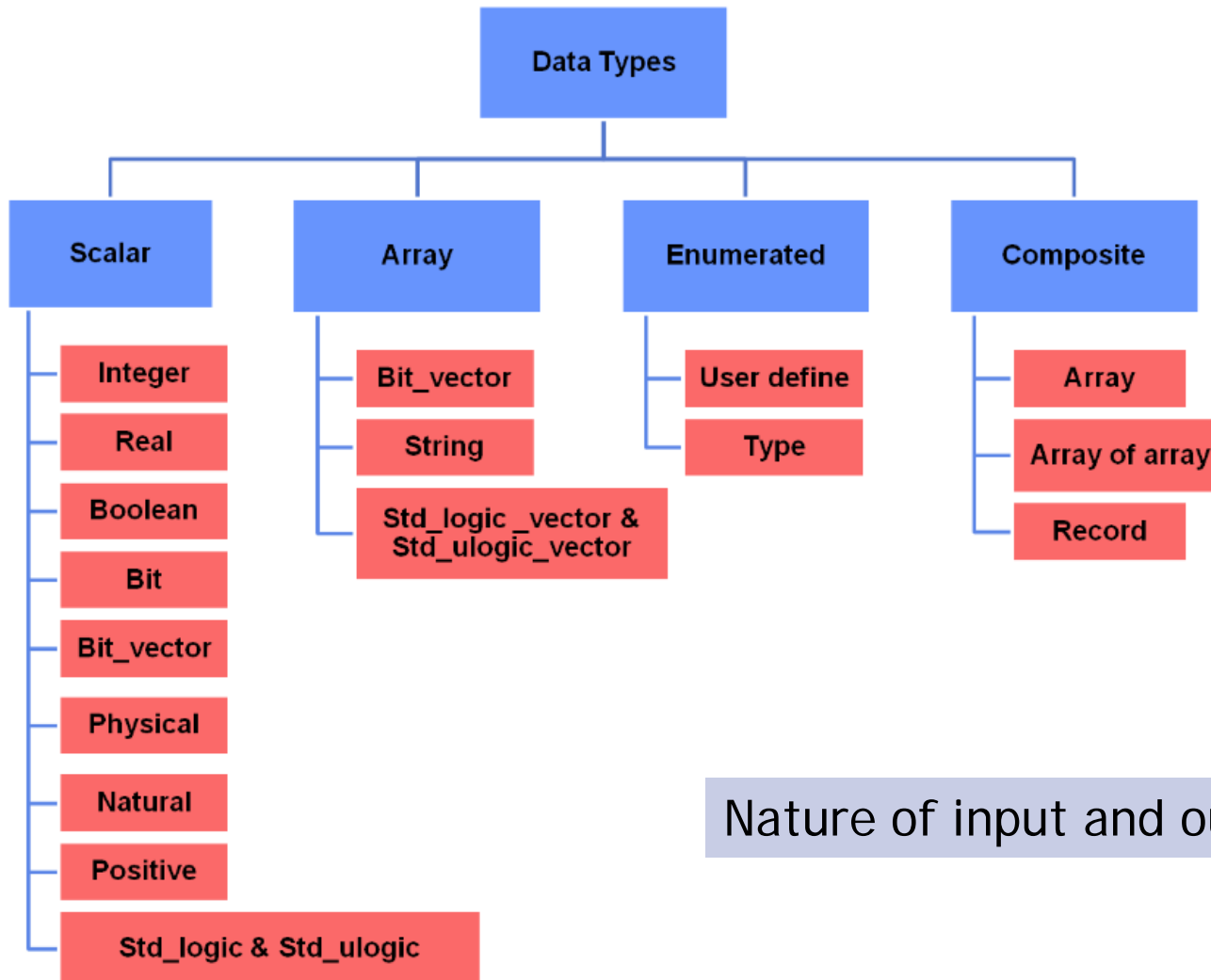

Nature of input and output signals

5.4 VHDL Data Types

Selected Data types:

- 1) Predefined types
- 2) User-defined types

Type	Description
bit	'0' or '1'
boolean	FALSE or TRUE
integer	an integer in the range -2^{31} to $+(2^{31} - 1)$
natural	integer in the range 0 to $+(2^{31} - 1)$
positive	integer in the range 1 to $+(2^{31} - 1)$
real	floating-point number in the range $-1.0\text{E}38$ to $+1.0\text{E}38$
character	any legal ASCII character including upper and lowercase letters, digits, and special characters
time	An integer with units fs, ps, ns, us, ms, sec, min, or hr

5.4 VHDL Data Types

A physical type allows user to define measurement units for some physical quantity, like length, time, pressure, capacity, etc.

-- EXAMPLE : physical type definitions

type **Distance** is range 0 to INTEGER'HIGH
units

micron;

millimetre = 1000 micron;

centimetre = 10 millimetre;

metre = 100 centimetre;

inch = 25400 micron;

foot = 12 inch;

yard = 3 foot;

mile = 5280 foot;

end **units Distance**;

AFTER the type **Distance** defined, "inch", "millimetre", "Distance" can be recognized by the VHDL design tool and we can declare signal Dist2 as following:

-- EXAMPLE : signal declaration and calculation

signal Dist2 : **Distance** := 2 inch - 1 millimetre;

5.4 VHDL Data Types

Let's begin with simple things first.

Signal declaration syntax:

```
signal <name> : <type>;
```

Signal declaration examples for architecture:

```
signal x1 : bit;  
signal C  : bit_vector (3 to 0);  
signal D  : bit_vector (7 downto 0);
```

bit & bit_vector are predefined in VHDL standards IEEE library.

bit: a bit object is either of value 0 or 1.

bit_vector: represent multi-bit data by an array of bit objects

5.4 VHDL Data Types - bit / bit_vector

```
signal x1   : bit;  
signal C    : bit_vector (3 to 0);  
signal D    : bit_vector (7 downto 0);
```

Signal assignment examples:

```
x1 <= '1';  
C  <= "1010";  
D  <= "11001010";
```

- Signal represent physical interconnect (wire) that communicate between processes/modules
- Signal assignment operator "**<=**"
- You can assign **'1'** to a single bit value, and **"1010"** to an array of bit values.
- You can use (3 to 0) or (7 downto 0) to index the array values.

5.4 VHDL Data Types - bit_vector

Data array is assigned as bit vector in VHDL.
Here is a data array A:

A[7]	A[6]	A[5]	A[4]	A[3]	A[2]	A[1]	A[0]
------	------	------	------	------	------	------	------

```
signal C: bit_vector (0 to 3);  
signal D: bit_vector (3 downto 0);  
signal A: bit_vector (7 downto 0);
```

```
C <= "1101";  
D <= C;  
A(6 downto 3) <= D;
```

```
C(0)=1  C(1)=1  C(2)=0  C(3)=1  
D(3)=1  D(2)=1  D(1)=0  D(0)=1  
A(6)=1  A(5)=1  A(4)=0  A(3)=1
```

5.4 VHDL Data Types - (Number type)

VHDL	Bit Pattern	Decimal equivalent
B"101"	101	5
X"101"	100000001	257
101	1100101	101

These numeric values are referred to as scalars or literals. Binary (prefix of B), Hex (prefix of X), Decimal (no prefix).

A signal may optionally be declared with an initial value:

Syntax: **signal** <name> : <type> := <initial_value>;

Example:

```
signal d : bit_vector(15 downto 0)  X"1234";
```

:=  is signal initialization operator

Bit array or bit vector is assigned to a signal (d) with hexadecimal value of **X"1234"**.

5.4 VHDL Data Types - std_logic /std_logic_vector

Standard Library defined by IEEE

```
library ieee;  
use ieee.std_logic_1164.all;
```

Type	Description
U	uninitialized. This signal hasn't been set yet
X	unknown. Impossible to determine this value/result
0	logic 0
1	logic 1
Z	High Impedance (Tri-state)
W	Weak signal, can't tell if it should be 0 or 1
L	Weak signal that should probably go to 0
H	Weak signal that should probably go to 1
-	Don't care

5.4 VHDL Data Types - Logic signal

Two multi-bit signals can be AND-ed to form an output signal. They all have the same bit length.

```
SIGNAL  A : BIT_VECTOR (7 DOWNT0 0);  
SIGNAL  B : BIT_VECTOR (7 DOWNT0 0);  
SIGNAL  S : BIT_VECTOR (7 DOWNT0 0);  
BEGIN  
    S <= A and B;  
END;
```

BIT_VECTOR:
With well defined
logic value [0 / 1]

```
SIGNAL  A : STD_LOGIC_VECTOR (7 DOWNT0 0);  
SIGNAL  B : STD_LOGIC_VECTOR (7 DOWNT0 0);  
SIGNAL  S : STD_LOGIC_VECTOR (7 DOWNT0 0);  
BEGIN  
    S <= A and B;  
END;
```

STD_LOGIC_VECTOR:
logic output [0 / 1 / Z
/ U / etc...] as shown
in previous slide

5.5 VHDL Operator - **Boolean Operators**

Logical operation	Operator	Example
AND	AND	<code>Z <= (A AND B);</code>
NAND	NAND	<code>Z <= (A NAND B);</code>
NOR	NOR	<code>Z <= (A NOR B);</code>
NOT	NOT	<code>Z <= NOT (A);</code>
OR	OR	<code>Z <= (A OR B);</code>
XNOR	XNOR	<code>Z <= (A XNOR B);</code>
XOR	XOR	<code>Z <= (A XOR B);</code>

VHDL provides predefined operators for modeling hardware units.
Logical (Boolean), Arithmetic, Relational Operators

5.5 VHDL Operator - Relational Operators

Relational operation	Operator	Example
Equal to	=	If (A = B) Then
Not equal to	/=	If (A /= B) Then
Less than	<	If (A < B) Then
Less than or equal to	<=	If (A <= B) Then
Greater than	>	If (A > B) Then
Greater than or equal to	>=	If (A >= B) Then

VHDL provides predefined operators for modeling hardware units.
Logical (Boolean), Arithmetic, Relational Operators

5.5 VHDL Operator - **Arithmetic Operators**

This part will be covered in the later chapter.

Arithmetic operation	Operator	Example
Addition	+	<code>Z <= A + B;</code>
Subtraction	-	<code>Z <= A - B;</code>
Multiplication	*	<code>Z <= A * B;</code>
Division	/	<code>Z <= A / B;</code>
Exponentiating	**	<code>Z <= 4 ** 2;</code>
Modulus	MOD	<code>Z <= A MOD B;</code>
Remainder	REM	<code>Z <= A REM B;</code>
Absolute value	ABS	<code>Z <= ABS A;</code>

5.5 VHDL Operator - Arithmetic Operators

REM:

$5 \text{ rem } 3 = 2 \rightarrow 5/3 = 1 \text{ remainder is } 2$

$(-5) \text{ rem } 3 = -2$

$5 \text{ rem } (-3) = 2$

$(-5) \text{ rem } (-3) = -2$

MOD:

$5 \text{ mod } 3 = 2$

$(-5) \text{ mod } 3 = 1 \leftarrow \text{different from REM}$

$5 \text{ mod } (-3) = -1 \leftarrow \text{different from REM}$

$(-5) \text{ mod } (-3) = -2$

$$5 = 1*3 + 2$$

$$-5 = -2*3 + 1$$

$$5 = -2(-3) - 1$$

$$-5 = 1*(-3) - 2$$

Then what is MOD used for?

The mod operator gives the residue for a division to round down.

5.5 Precedence of VHDL Operators

VHDL Operators:

1. Binary logical operators: and, or, nand, nor, xor, xnor
2. Relational operators: =, /=, <, <=, >, >=
3. Shift operators: sll, srl, sla, sra, rol, ror
4. Adding operators: +, -, & (concatenation)
5. Unary sign operators: +, -
6. Multiplying operators: *, /, mod, rem
7. Miscellaneous operators: not, abs, **

Sll = Shift Left Logical Srl = Shift Right Logical Sra = Shift Right Arithmetic rol = Rotate Right logical

Class 7 has highest precedence, then 6, 5, 4, ...

Operators in the same class are applied left to right

Parentheses change the order of precedence

5.5 VHDL Operators - Example

Operators with the highest precedence are applied first, without the presence of parentheses.


Example:

```
f <= a AND NOT(b) OR NOT(a) AND b;  
      ab' + a'b
```

```
f <= a AND (NOT(b) OR NOT(a)) AND b;  
      a(b' + a')b
```

 5.6 VHDL Syntax for Boolean Expressions

- VHDL code describes the circuit design with Boolean expressions.
- It is different from computer program which is composed of a sequence of instructions for CPU to execute.
- VHDL Boolean expressions are statements only for configuring the FPGA chip (no CPU to execute these statements).




5.6 VHDL Syntax for Boolean Expressions

VHDL models combinational circuit using concurrent statements.

Concurrent statements:

A change(s) at the input(s) will cause the output change accordingly.

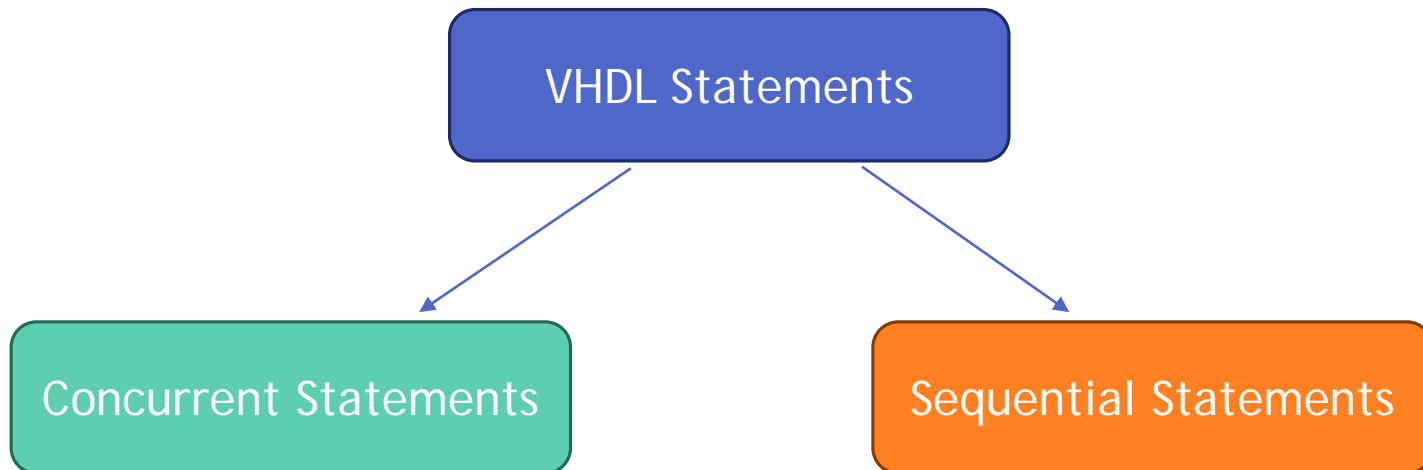Sequential statements will be covered later.



5.6 VHDL Syntax for Boolean Expressions



```
C <= A and B after 5 ns;  
E <= C or D after 5 ns;
```

Concurrent statements (continuous assignments) example:
A signal assignment statement has the form:

```
signal_name <= expression [after delay];
```

Square bracket is optional and it is for indicating the propagation delay.

Signal on the left is updated after delay, if included.


5.6 VHDL Syntax for Boolean Expressions

Examples of Boolean expressions converted into VHDL Boolean expressions.

Boolean	VHDL Boolean
$Y = \overline{AB}$	<pre>Y <= NOT(A AND B); or Y <= A NAND B;</pre>
$Y = \overline{A + B}$	<pre>Y <= NOT(A OR B); or Y <= A NOR B;</pre>
$Y = A + BC$	<pre>Y <= A OR (B AND C);</pre>
$Y = C\overline{X} + \overline{D}$	<pre>Y <= C AND NOT (X OR D);</pre>
$Y = A\overline{B}C + \overline{A}\overline{B}C + \overline{A}BC$	<pre>Y <= (A AND NOT B AND C) OR (NOT A AND NOT B AND C) OR (NOT (A AND B) AND C);</pre>

5.6 VHDL Syntax for Logic Circuit

Example of 3 concurrent statements:

 



Precedence order is NOT important for concurrent statements !!

```
sig1 <= (a and b);  
out1 <= (sig1 or c);  
out2 <= (not d);
```

≡


```
out1 <= (sig1 or c);  
sig1 <= (a and b);  
out2 <= (not d);
```

  
5.6 VHDL Syntax for Logic Circuit - Exercise



Write your own VHDL statement to describe the above two logic circuits.

 5.6 VHDL Syntax for Logic Circuit - Exercise




```
S1 <= x1 OR x2;  
S2 <= x3 AND x4;  
F <= S1 XOR S2;
```

OR

```
F <= (x1 OR x2) XOR (x3 AND x4);
```

- Left hand style is more readable and traceable but need to declare two more signals.
- In contrast, Right hand style use less lines of code but a bit difficult for debugging.
- They both have same result after synthesize.

 5.6 VHDL Syntax for Logic Circuit - Exercise



```
Sig1 <= x XOR y;  
Sig2 <= x AND y;  
Sig3 <= Sig1 AND Cin;  
s <= Cin XOR Sig1;  
Cout <= Sig3 OR Sig2;
```

5.7 VHDL Module

A Logic circuit consists of one or multiple modules.

Each module consists of only one **entity** with **architecture(s)**.

Entity description declares the input and output signals.

Each ENTITY has a unique **name** !!

Port declaration specifies the input signals and output signals for the module.

```
ENTITY name IS
```

```
PORT( ... );
```

```
END name;
```

5.8 VHDL Format and Syntax - Example


```
ENTITY and_gate IS
Port (
    A : in  STD_LOGIC;
    B : in  STD_LOGIC;
    S : out STD_LOGIC
);
END and_gate;
```

Mode indicates the direction (in, out, and inout) of port signals

Type specifies the data type (bit, bit_vector) that can be communicated

5.7 VHDL Modules - Entity Example


Example for a circuit named logic_c :

 

```
entity logic_c is
    port(
        x1,x2,x3,x4,x5 : in std_logic;
        f : out std_logic
    );
end logic_c;
```

5.7 VHDL Modules - Entity Example

Example for a Full Adder:

 

```
entity FullAdder is
    port(
        X, Y, C_in   : in  std_logic;
        C_out, Sum   : out std_logic
    );
end FullAdder;
```

In this example, the VHDL assignment statements for *Sum* and *C_{out}* represent the logic expressions for the full adder. *Sum* and *C_{out}* are described by architectures.

5.8 VHDL Format and Syntax - Example

Every ENTITY must at least contain one ARCHITECTURE associated with it.

Each ARCHITECTURE has a unique **name**.

```
ARCHITECTURE ckt OF and_gate IS  
BEGIN  
    y <= a AND b;  
END ckt;
```


5.8 VHDL Format and Syntax

- Complete Module Code

```
library ieee;
use ieee.std_logic_1164.all;

ENTITY and_gate IS
PORT (      a,b      :IN   STD_LOGIC;
        s           :OUT  STD_LOGIC)
    ; )
END and_gate;

ARCHITECTURE ckt OF and_gate IS
BEGIN
    s <= a AND b;
END ckt;
```