

## Copyright

---

These lecture notes were prepared by Dr. Joshua E. Y. Lee. Approval was obtained for using the lecture notes.



1

## I. Nodal Voltage Analysis (NVA)

---

### KCL & Ohm's law in action

- The method of nodal voltage analysis is an application of KCL and Ohm's law together
- The unknown variables that you will solve for are **node voltages**
- We will apply KCL at a node and express the unknown currents as unknown node voltages




2
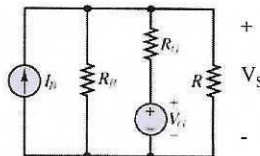
## Example on how to do NVA

Find the voltage across the current source,  $V_S$ :

Given:  $I_B = 12A$ ,  $V_G = 12V$ ,  $R_G = 0.3\Omega$ ,  $R_B = 1\Omega$ ,  $R = 0.23\Omega$



Apply KCL at  $V_S$ :

$$I_B = \frac{V_S}{R_B} + \frac{V_S - V_G}{R_G} + \frac{V_S}{R}$$

$$12 = \frac{V_S}{1} + \frac{V_S - 12}{0.3} + \frac{V_S}{0.23}$$


$$V_S = 5.99V$$

- Note that the negative terminal of  $V_G$  is used as a reference (0V) in the example
- The value of  $V_S$  is also referenced to this node
- The value of the reference node is not important since we are only interested in the voltage difference
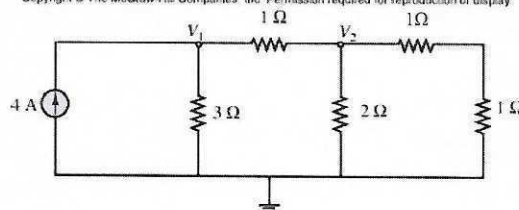
## Worked Example on NVA 1

Use nodal voltage analysis to find  $V_1$  and  $V_2$ . (Answer:  $V_1 = 4.8V$ ,  $V_2 = 2.4V$ )

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



First method:

- Apply KCL at  $V_1$  (1)
- Apply KCL at  $V_2$  (2)
- Solve equations (1) and (2)

At node  $V_1$ :  $4 = \frac{V_1}{3} + \frac{V_1 - V_2}{1}$  (1)

At node  $V_2$ :  $\frac{V_1 - V_2}{1} = \frac{V_2}{2} + \frac{V_2}{1+1}$  (2)

Solve (1) & (2):  $V_1 = 4.8V$ ;  $V_2 = 2.4V$

Alternate method:


- Combine all the resistors to find  $V_1$  first
- Then combine the 3 resistors on the right followed by voltage divider rule to find  $V_2$

## Worked Example on NVA 2

Use nodal voltage analysis to find the current through the 3V source.

(Answer:  $i = 8.31 \text{ A}$ )

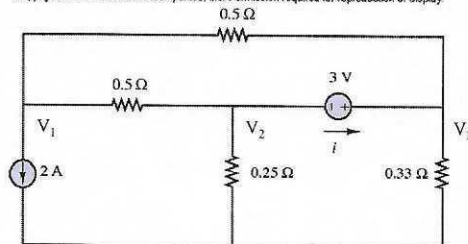Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Apply KCL at  $V_1$ :

$$2 = \frac{V_2 - V_1}{0.5} + \frac{V_3 - V_1}{0.5}$$

$$V_2 + V_3 - 2V_1 = 1 \quad (1)$$

Apply KCL at  $V_2$ :

$$\frac{V_1 - V_2}{0.5} = \frac{V_2}{0.25} + i$$

$$2V_1 - 6V_2 = i \quad (2)$$

Apply KCL at  $V_3$ :

$$\frac{V_3}{0.33} + \frac{V_3 - V_1}{0.5} = i$$

$$\frac{166}{33}V_3 - 2V_1 = i \quad (3)$$

Since a new variable is introduced in (2), we need one more equation.

$$V_3 - V_2 = 3 \quad (4)$$


## II. Mesh Current Analysis (MCA)

### KVL & Ohm's law in action

- The method of mesh current analysis is an application of KVL and Ohm's law together
- The unknown variables that you will solve for are **mesh currents**
- From KVL, the sum of voltage drops and rise must equal zero
- The voltage differences are expressed as the current going through each branch in the mesh
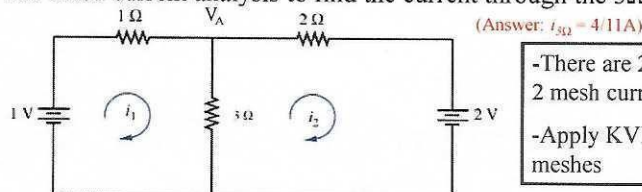
## Example on how to do MCA

Use mesh current analysis to find the current through the  $3\Omega$  resistor.



-There are 2 meshes and hence 2 mesh currents

-Apply KVL to each of these 2 meshes

Apply KVL to mesh 1:

$$1 = i_1(1 + 3) - 3i_2$$

$$4i_1 - 3i_2 = 1 \quad (1)$$

Useful tip:

- keep voltages of sources on one side of the equation, and keep voltages of resistors on the other side

Apply KVL to mesh 2:

Follow the defined direction of the mesh current

$$-2 = i_2(2 + 3) - 3i_1$$

$$5i_2 - 3i_1 = -2 \quad (2)$$


Now, solve equation (1) and (2):

$$i_{3\Omega} = i_1 - i_2$$

7
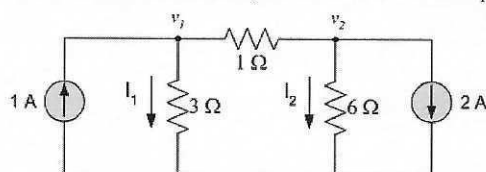
## Worked Example on MCA 1

Use mesh current analysis to find currents  $I_1$  and  $I_2$ . (Answer:  $I_1 = I_2 = -0.5A$ )



-You see 3 meshes, but only the middle mesh is unknown, the other 2 are defined by the current sources.

$$i_1 = 1A ; \quad i_3 = 2A$$


For the middle mesh

$$-(i_2 - i_1) \times 3 - i_2 - 6(i_2 - i_3) = 0$$

$$\therefore i_1 = 1, \quad i_3 = 2$$

$$\Rightarrow -10i_2 + 15 = 0$$

$$\Rightarrow i_2 = 1.5$$

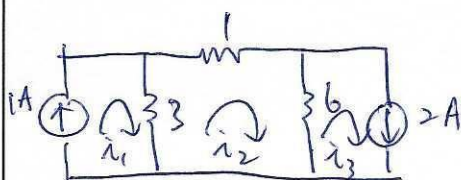

8

$$I_1 = i_1 - i_2 = 1 - 1.5 = -0.5A$$

$$I_2 = i_2 - i_3 = 1.5 - 2 = -0.5A$$

#




## Worked Example on MCA 2

Use mesh current analysis to find the voltage across the current source.

(Answer:  $V = 3.89 \text{ V}$ )

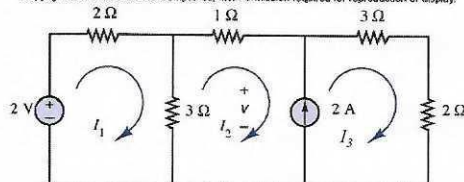Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



-In the process of deriving equations (2) and (3), a new variable  $V$  is introduced.

-Hence, we need one more equation, (4)

Apply KVL at mesh 1:

$$2 = I_1(2+3) - I_2(3)$$

$$\Rightarrow 5I_1 - 3I_2 = 2 \quad (1)$$

Apply KVL at mesh 3:

$$V = I_3(3+2)$$

$$\Rightarrow 5I_3 = V \quad (3)$$

Apply KVL at mesh 2:

$$-V = I_2(3+1) - I_1(3)$$

$$\Rightarrow 4I_2 - 3I_1 = -V \quad (2)$$

One more equation:

$$I_3 - I_2 = 2A \quad (4)$$

Solve for  $V$ , verify by  $V = (I_3)(3+2)$




9

## Worked Example on MCA 3

Use mesh current analysis, find the voltage across the  $0.25 \Omega$  resistor.

(Answer:  $v = 0.34 \text{ V}$ )

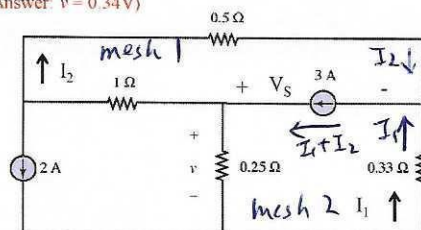

Method:

-Find the current through  $0.25\Omega$  resistor first, then use this to find the voltage.

-Although there are 3 meshes, the bottom left mesh is already known (2A going anti-clockwise).

Apply KVL at mesh 1:

$$V_s = I_2(0.5 + 1) + (2)(1)$$

$$\Rightarrow V_s = 1.5I_2 + 2 \quad (1)$$

Apply KVL at mesh 2:

$$V_s = I_1(0.25 + 0.33) - (2)(0.25)$$

$$\Rightarrow V_s = 0.58I_1 - 0.5 \quad (2)$$

Consider the current source:

$$I_1 + I_2 = 3 \quad (3)$$

Solve for  $I_1$  and  $I_2$

Current through  $0.25 \Omega$  resistor:  $I_1 - 2$

$$V = (I_1 - 2)(0.25)$$



10

## Quick note on choosing NVA and MCA

How do you choose between NVA and MCA?

- Your choice should not be due to level of familiarity between the methods.
- One consideration is whichever is simpler to use for a given circuit.
- How then do you decide what is simpler?
- For a start, having fewer equations certainly makes solving easier.

11

## III. Superposition

### The method

- This method applies only to circuits that have multiple sources
- In such case, it can come in handy (or not)
- In a circuit with multiple sources, superposition considers the current or voltage associated with a given branch for one of the sources, while turning the rest off

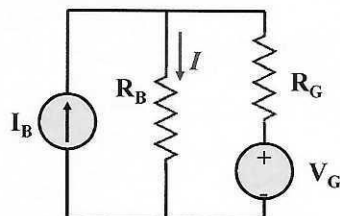


Fig 1: Basic circuit with 2 sources

Aim: Find the current through  $R_B$ .

1. Find the current ( $I_1$ ) through  $R_B$  when only  $I_B$  is present ( $V_G$  is removed)
2. Find the current ( $I_2$ ) through  $R_B$  when only  $V_G$  is present ( $I_B$  is removed)
3. The net current  $I = I_1 + I_2$

12

## How do we “remove” a current source or voltage source?

### Killing sources

**Voltage source:** If the voltage source does not exist, the voltage across the terminals would be zero. It looks like a short circuit. (see Fig 2a)

**Current source:** If the current source does not exist, the current through it would be zero. It looks like an open circuit. (see Fig 2b)

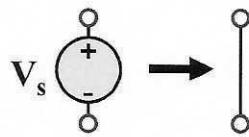


Fig 2a: Disable a voltage source by Replacing with a short circuit.

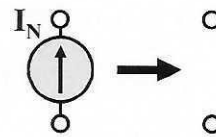


Fig 2b: Disable a current source by Replacing with an open circuit.

13

## Apply the tips to Fig 1



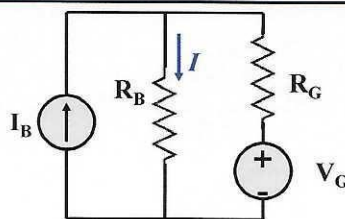


Fig 1: Basic circuit with 2 sources

**Killing  $V_G$ ,  $V_G = 0$**

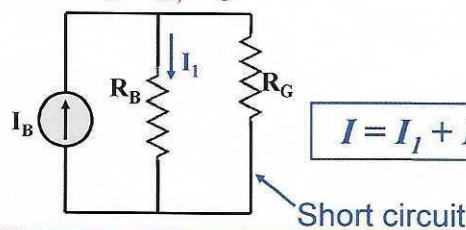

**Killing  $I_B$ ,  $I_B = 0$**

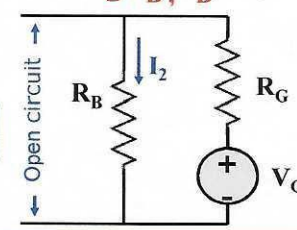


14

## Worked Example on Superposition

Determine the current through  $R_1$  using superposition.

Given  $R_1 = 560\Omega$ ,  $R_2 = 3.5k\Omega$ ,  $R_3 = 810\Omega$ ,  $V_{S2} = V_{S1} = 90V$

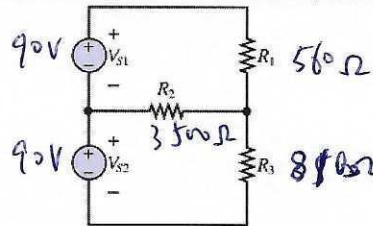Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



a. First, short  $V_{S1}$   
 Voltage across  $R_1$ :  $V_{R1a} = \frac{R_1 \parallel R_2}{(R_1 \parallel R_2) + R_3} V_{S2}$   

$$= \left( \frac{560 \parallel 3500}{(560 \parallel 3500) + 810} \right) 90$$
  

$$= 33.61V$$

Current through  $R_1$ :

$$I_{R1a} = V_{R1a} / R_{1a}$$

$$= 33.61 / 560$$

$$= 0.06A$$

## Worked Example on Superposition

b. Next, short  $V_{S2}$

Current through  $R_1$ :

$$I_{R1b} = \frac{V_{S1}}{R_1 + (R_2 \parallel R_3)} = \frac{90}{560 + (3500 \parallel 810)}$$

$$= 0.074A$$

**Take careful note of the directions defined for each of these currents.**

Finally,

$$I_{R1} = I_{R1a} + I_{R1b} = 0.134A$$



# One-Port Network

## Introduction

- A one port network is simply a two terminal device (See Fig below)

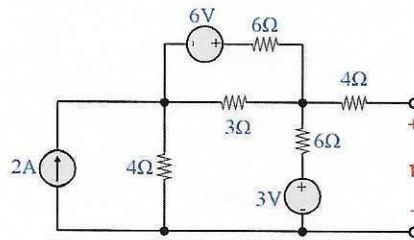


Fig 1: An example of a one port network

- Given a number of different resistor loads, if you were asked to find the current and voltage at the terminals for each resistor, you would have to recalculate the whole circuit
- A different load will give you different output current & voltage



17

# One-Port Network

## Simpler analysis

- Transform any 2 terminal circuit into a circuit that is as simple as having 1 resistor and 1 source (see Fig 2)

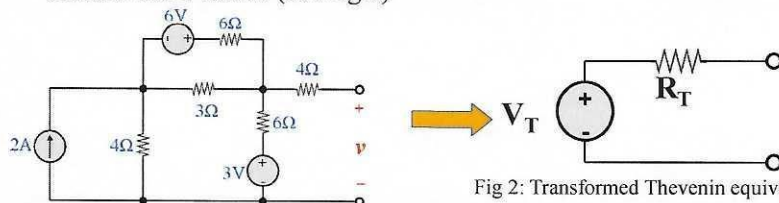


Fig 2: Transformed Thevenin equivalent circuit

The first part of this part is organized into the following 3 sections:

- Thevenin equivalent
- Norton equivalent
- Source transformation



18

# I. Thevenin

## Definition

- Any one-port network composed of **ideal** voltage and current sources, and **linear** resistors, can be represented by an equivalent circuit consisting of an ideal **voltage source**  $V_T$  in **series** with an equivalent **resistance**  $R_T$

## Deriving the Thevenin equivalent circuit

**Step 1:** Remove the load from the rest of the one port network. This is the first most fundamental step.

**Step 2:** Find the equivalent resistance  $R_T$ . Kill all ideal sources then find the resistance across the terminals.

For voltage source – replace with short circuit

For current source – replace with open circuit

**Step 3:** Find the Thevenin voltage source. The Thevenin voltage source is equal to the open circuit voltage seen across the terminals (with no load). Solve for this voltage using any preferred method (NVA, MCA, superposition).




19

## Worked Example on Thevenin 1

Derive the Thevenin equivalent circuit seen by the  $3\Omega$  load.


Answer:  $R_{th} = 3.22\Omega$ ,  $V_{th} = 16V$

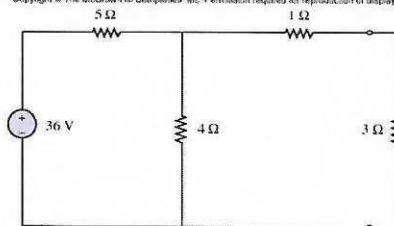Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Steps:

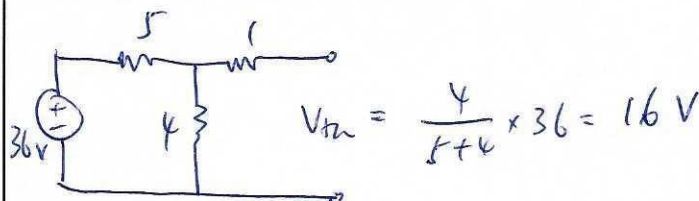1. Remove the  $3\Omega$  load
2. Find  $R_T$  (disable the voltage source)
3. Find  $V_T$  (with no load)
4. Draw the Thevenin circuit



Thevenin circuit

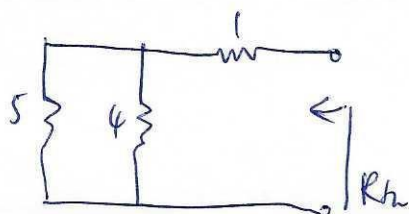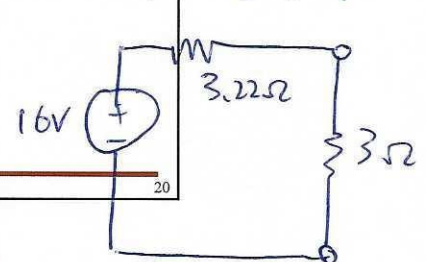


$$\begin{aligned}
 R_{th} &= 1 + (5 \parallel 4) \\
 &= 1 + \frac{5 \times 4}{5 + 4} \\
 \Rightarrow R_{th} &= 3.22\Omega
 \end{aligned}$$

## Worked Example on Thevenin 2

Derive the Thevenin equivalent circuit as seen by the resistor  $R_L$ .

Answer:  $R_{th} = 504 \Omega$ ,  $V_{th} = -10 \text{ mV}$


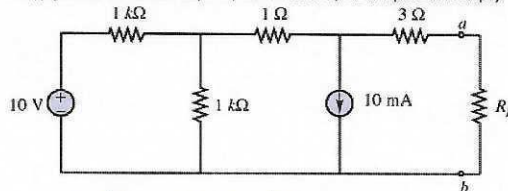
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Steps:

1. Remove the load
2. Find  $R_T$  (kill the voltage and current sources)
3. Find  $V_T$  (with no load)
4. Draw the Thevenin circuit

① Kill the voltage source

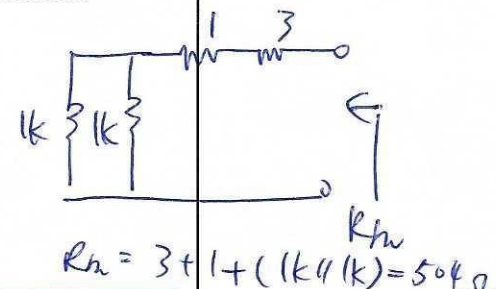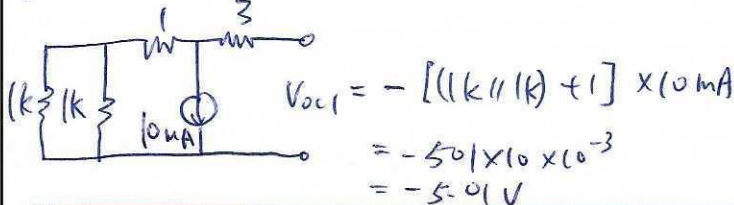

② Kill the current source

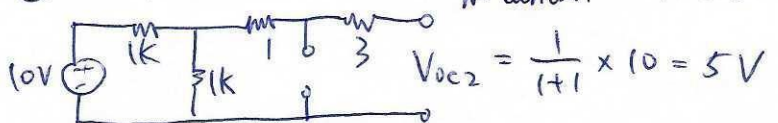

$$V_{th} = V_{OC1} + V_{OC2}$$

$$= -5.01 + 5$$

$$= -0.01 \text{ V}$$

$$V_{th} = -10 \text{ mV}$$

## II. Norton


### Definition

- Any one-port network composed of **ideal** voltage and current sources, and **linear** resistors, can be represented by an equivalent circuit consisting of an ideal **current source**  $I_N$  in **parallel** with an equivalent **resistance**  $R_N$
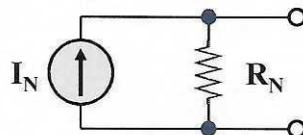
### Deriving the Norton equivalent circuit

**Steps 1 and 2** for deriving the Norton equivalent circuit are exactly the same as that for Thevenin.

**Step 3:** Find the Norton current source. The Norton current source is equal to the short circuit current seen across the terminals (with no load). Solve for this ~~voltage~~ <sup>current</sup> using any preferred method (NVA, MCA, superposition).





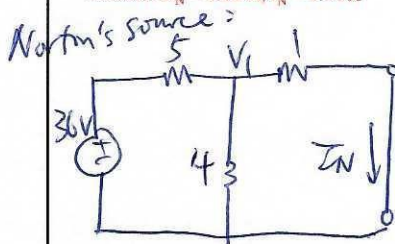
## Worked Example on Norton 1

Derive the Norton equivalent circuit seen by the  $3\Omega$  load.

Answer:  $R_N = 3.22\Omega$ ,  $I_N = 4.96\text{ A}$




$$V_1 = \frac{4 \parallel 1}{(4 \parallel 1) + 5} \times 36$$


$$= \frac{0.8}{5.8} \times 36$$

$$\Rightarrow V_1 = 4.96\text{ V}$$

$$I_N = \frac{V_1}{1} = 4.96\text{ A}$$

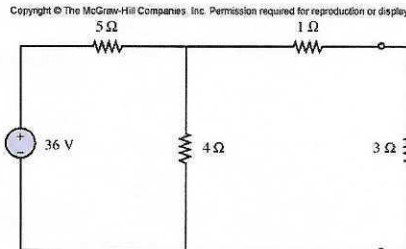


Norton Resistance:

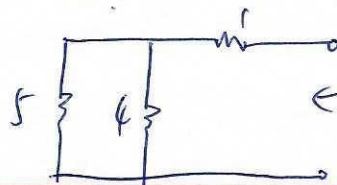

$$R_N = 1 + (5 \parallel 4)$$

$$= 1 + 2.22$$

$$\Rightarrow R_N = 3.22\Omega$$


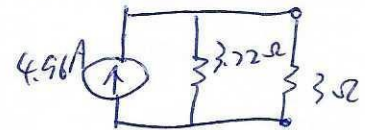


## Worked Example on Norton 2

Derive the Norton equivalent circuit seen by the load  $R_L$ .

Answer:  $R_N = 504\Omega$ ,  $I_N = -19.8\mu\text{ A}$

① Kill voltage source

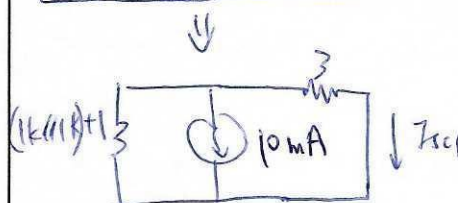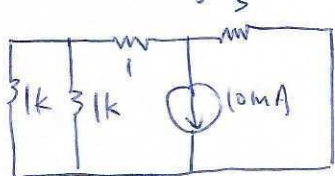


$$I_{sc1} = \frac{(1k \parallel 1k) + 1}{(1k \parallel 1k + 1) + 3} \times (-10)$$


$$= \frac{-501}{504} \times 10$$

$$= -9.94048\text{ mA}$$

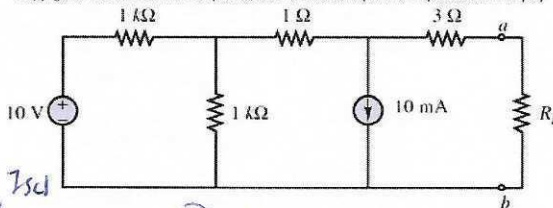Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




② Kill current source

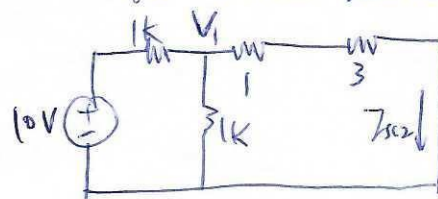

$$V_1 = \frac{1k \parallel 4}{(1k \parallel 4) + 1k} \times 10$$

$$1k \parallel 4 = \frac{1000 \times 4}{1000 + 4} = 3.984064$$
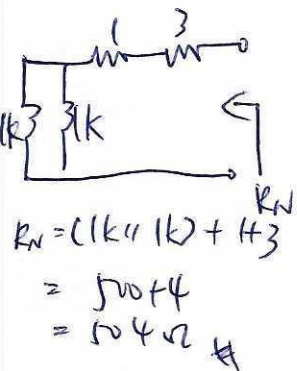
$$\therefore V_1 = \frac{3.984064}{1000.14 + 1000} \times 10 = 0.0398425\text{ V}$$



$$I_{sc2} = \frac{V_1}{4}$$

$$= \frac{0.0398425}{4} (\text{A})$$

$$= 9.92063\text{ mA}$$

$$I_{sc} = I_{sc1} + I_{sc2}$$

$$= (-9.94048 + 9.92063)\text{ mA}$$


$$= -19.85\mu\text{ A}$$



### III. Source Transformation
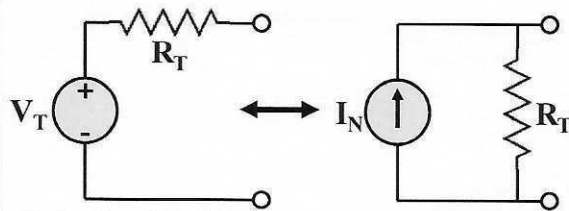
#### Definition

- This trick rests on the fact that the Thevenin and Norton forms are equivalent to each other and therefore are also interchangeable



We can transform between the two equivalent circuits, observing each time that:

$$V_T = I_N R_T$$

Fig 4a: Thevenin equivalent circuit      Fig 4b: Norton equivalent circuit


- Rather than transform the whole circuit in one go to Thevenin or Norton equivalent forms, we can instead transform part of the circuit
- The process of merge transform and merge again can be repeated



25

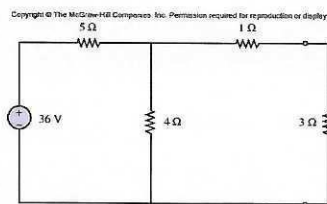
### Worked Example on Source Transformation 1

Derive either of the equivalent circuit forms seen by the  $3\Omega$  load.




① From worked example on Thevenin 1 (p. 20)

The Thevenin circuit is

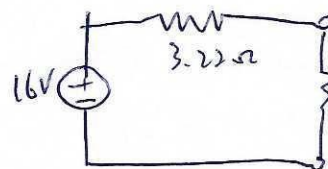

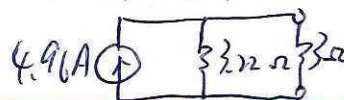② From Worked Example on Norton 1, the Norton circuit is




26

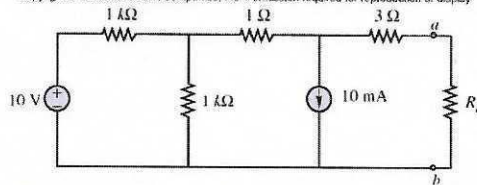
## Worked Example on Source Transformation 2

Derive either of the equivalent circuit forms seen by the load  $R_L$ .


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



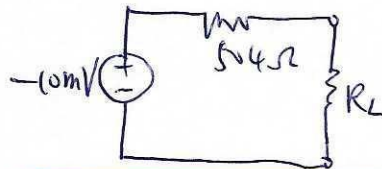① From Worked Example on Thevenin 2 (p. 21)



② From Worked Example on Norton 2

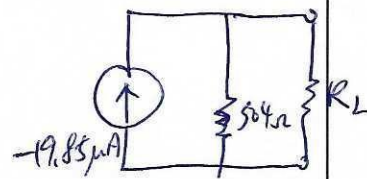

27

## III. Dependent Sources

- All the sources we have come across are independent source
  - > For a voltage source, the voltage maintained across the source is fixed
  - > For a current source, the current through the source is fixed
- There also exist dependent sources in circuit theory
- Unlike independent sources, the value of a dependent source is not predetermined, but is set by the current or voltage through a specific branch

### Symbol

- The symbol for an independent source is a circle
- For a dependent source, the symbol is a diamond

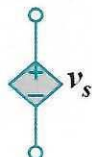


Fig 5a: Dependent voltage source



Fig 5b: Dependent current source

28

# Dependent Sources

## Dependent Voltage Source

$v_s$  is the voltage source across the terminals.

### Current Controlled Voltage Source

For example,  $v_s = 5i_x$ . The current  $i_x$  is not the current through the source but belongs to another branch.

### Voltage Controlled Voltage Source

For example,  $v_s = 7v_x$ . The voltage  $v_x$  is not the source voltage. As  $v_x$  changes, so also  $v_s$  according to the above relations.



## Dependent Current Source

$i_s$  is the current source through the terminals.

### Current Controlled Current Source

For example,  $i_s = 5i_x$ . The current  $i_x$  is not the current through the source but belongs to another branch.

### Voltage Controlled Current Source

For example,  $i_s = 7v_x$ . The voltage  $v_x$  is not the source voltage. As  $v_x$  changes, so also  $i_s$  according to the above relations.




29

## Worked Example on Dependent Source 1

Calculate  $v_o$  in the circuit.

Answer:  $v_o = 3.65 \text{ V}$

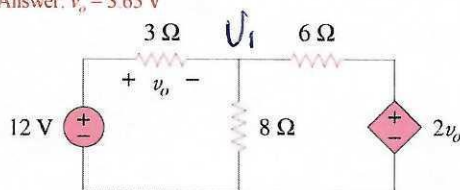

Hints:

1. The dependent source here is a voltage controlled voltage source
2. Apply KCL

Apply KCL:

$$\frac{v_1 - 12}{3} + \frac{v_1}{8} + \frac{v_1 - 2v_o}{6} = 0 \quad (1)$$

But at 3-Ω resistor  $v_o = 12 - v_1$  — (2)

Two equations for two unknowns ( $v_1, v_o$ )




30

$$\Rightarrow v_1 = 8.3478 \text{ V} \quad \& \quad v_o = 12 - v_1 = 3.65 \text{ V} \quad \#$$

## Worked Example on Dependent Source 2

Calculate  $i_o$  in the circuit.

Answer:  $i_o = 1.73 \text{ A}$

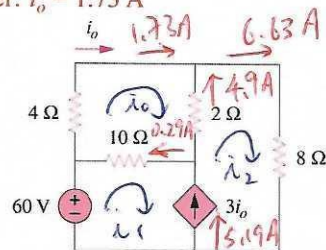

Hints:

1. The dependent source here is a current controlled current source
2. Apply KCL

① Consider loop 0:  $-4\bar{i}_0 - 2(\bar{i}_0 - \bar{i}_2) - 10(\bar{i}_0 - \bar{i}_1) = 0$   
 $\Rightarrow -8\bar{i}_0 + 5\bar{i}_1 + \bar{i}_2 = 0 \quad \text{---(1)}$

② Consider (loop 1 + loop 2) and use KVL:  
 $60 - 10(\bar{i}_1 - \bar{i}_0) - 2(\bar{i}_2 - \bar{i}_0) - 8\bar{i}_2 = 0$


$\Rightarrow 6\bar{i}_0 - 5\bar{i}_1 - 5\bar{i}_2 = -30 \quad \text{---(2)}$

③ At the current source:  $\bar{i}_2 - \bar{i}_1 = 3\bar{i}_0 \quad \text{---(3)}$


solving ①, ②, ③:  $\bar{i}_0 = 1.73 \text{ A}; \bar{i}_1 = 1.44 \text{ A}; \bar{i}_2 = 6.63 \text{ A}$
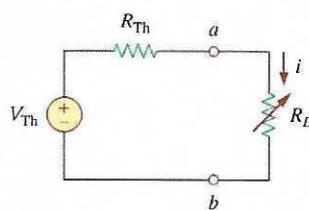
## Maximum Power Transfer

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



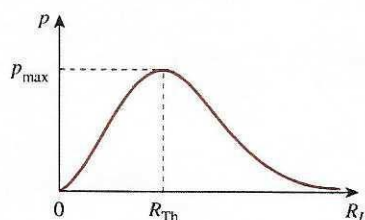Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$\frac{dp}{dR_L} = 0 \quad \longrightarrow \quad R_L = R_{Th}$$

$$p_{max} = \frac{V_{Th}^2}{4R_{Th}}$$