

City University of Hong Kong

Department of Electrical Engineering

EE 2000 – Lab Manual 4

Finite State Machine (FSM) to Design a 3-bit counter

Course Leader: Dr. WONG Steve Hang

Objectives:


- Learn how to write sequential logic circuits using VHDL.
- Implement a simple finite-state machine with a good coding style.
- Implement two buttons to control the state change of the FSM.
- Display the state transition with the LEDs on the Zedboard.

There are 4 checkpoints in page 7 and 8.

Experiment:

A finite-state machine (FSM) is an abstract machine that can be implemented as one of a finite number of states at any given time. The FSM can change from one state to another in response to some external inputs, this change is called a transition. An FSM can be defined by a list of its states, its initial state and the conditions for each transition.

 In this experiment, we will implement a simple 3-bit counter with VHDL. The initial state is 000. Every time we push the control button, the counter will add 1 and LED will show the current number. When the reset button is pushed, the FSM will jump to the initial state 000. The diagram of this FSM is



The FSM has both sequential logic and combinational logic, it is a good habit to separate these two parts in VHDL. In this experiment we will implement this FSM step by step.

- Determine the input and output of the module. The module has sequential logic circuits so we need a clock signal and a global reset signal (which is connect to

reset button). There are one other input signals connecting control button. We also need an 8-bit output signal connecting LEDs to show the current state. The entity of our FSM module is

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity fsm is
Port (
clk: in STD_LOGIC;
rst: in STD_LOGIC;
ctrlButton: in STD_LOGIC;
led: out STD_LOGIC_VECTOR (7 DOWNTO 0)
);
end fsm;
```

- ii. In this experiment, we need to detect when the control button is pushed. If the button is pressed, the ctrlButton is equal to '1'. We set a 10ms timer to eliminate unstable input, which is called **button debounce**. We provide the key detection source code. Read and understand the code, you are required to know how to write a piece of sequential logic code yourself.

```
Architecture Behavioral of fsm is

Constant TIME_10ms: integer := 1000000;
Signal key_counter: integer range 0 to 1000001;
Signal btnDetection: boolean;
type states is (zero, one, two, three, four, five, six, seven);
signal present_state, next_state: states;

begin

Key_detection: process (clk)
begin
    if rising_edge(clk) then  --Clock event, used to describe sequential logic.
        if (ctrlButton='1') then
```

```

        key_counter <= 0;
    elsif (ctrlButton='0') and (key_counter <= TIME_10MS) then
        key_counter <= key_counter + 1;
    end if;
end if;
end process;

btnDetection <= (key_counter = TIME_10ms);

```

When control button is pushed, **key_counter** will be set to 0. After the button is released, the timer will start counting and the stable time is longer enough, **btnDetection** will be true for one cycle.

- iii. The sequential logic of our FSM is very simple. Every time the **btnDetection** is true, the FSM will jump to the next state. We define a type called **states** enumerating all possible states. Then we define two signals present_state and next_state which are both **states** type. Every time the btnDetection is true, the value of next_state will be provided to present_state (meaning the state jumps to the next state). The assignment of next_state will be introduced in the next section

```

state_transition: process (rst, clk)
begin
    if (rst='1') then
        --Write your code here to describe state transition.
    elsif (rising_edge(clk) and btnDetection = true ) then
        --Write your code here to describe state transition.
    end if;
end process;

```

- iv. The combinational logic of our FSM assigns LED output and the next_state. The LED output is a 3-8 decoder. We can see the truth table of the decoder.

present_state	LED Output
zero	00000001
one	00000010
two	00000100

three	00001000
four	00010000
five	00100000
six	01000000
seven	10000000

The corresponding VHDL template and you can complete the following code.

```

decoder: process (present_state)
begin
    case present_state is
        --Write your code here to assign LED and next_state
    end case;
end process;
end Behavioral;

```

- v. Create constraints.

In this experiment, we use the on-board 100 MHz clock source as the input of “clk” in our design, push button BTND as input of “rst”, BTNC as input of “ctrlButton”, LD0-LD7 as output of “led[0]”-“led[7]”. Refer to the “ZedBoard Hardware User’s Guide” to complete the file below.

```

# Timing Constraints
create_clock -period 10.000 -name Clock -waveform {0.000 5.000} [get_ports {clk}]

set_property PACKAGE_PIN Y9 [get_ports {clk}]
set_property IOSTANDARD LVCMOS33 [get_ports {clk}]
set_property PACKAGE_PIN R16 [get_ports {rst}]
set_property IOSTANDARD LVCMOS18 [get_ports {rst}]

#Write your code here to complete this constraints file

```

- vi. Create testbench

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity fsm_tb is
end fsm_tb;

architecture Behavioral of fsm_tb is
    component fsm is
Port (
    clk : in STD_LOGIC;
    rst : in STD_LOGIC;
    ctrlButton : in STD_LOGIC;
    led : out STD_LOGIC_VECTOR (7 DOWNTO 0)
);
    end component;
    signal clk : STD_LOGIC;
    signal rst : STD_LOGIC;
    signal ctrlButton : STD_LOGIC;
    signal led : STD_LOGIC_VECTOR (7 DOWNTO 0);

begin

    uut: fsm port map (clk=>clk, rst=>rst, ctrlButton=>ctrlButton,
led=>led);

    clk_gen: process
    begin
        clk <= '0';
        wait for 5ns;
        clk <= '1';
        wait for 5ns;
    end process;

    rst <= '0';

    sig_gen: process
    begin
        ctrlButton <= '0';
        wait for 90ns;
        ctrlButton <= '1';


```

```

        wait for 10ns;
        ctrlButton <= '0';
        wait for 20ns;
    end process;
end Behavioral;

```

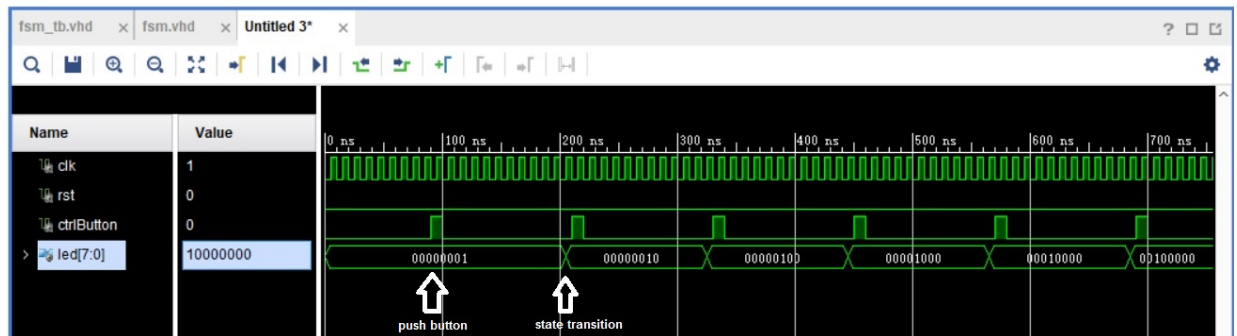To shorten simulation time, change **TIME_10MS** in fsm.vhd to **10**. After simulation, we can get the waveform like this.




After the control button is pushed, it takes some time to detect and then the state jumps to the next state and LED signals show the current state.

Checkpoint 1: Show your simulation results to your demonstrator.

- vii. **Run synthesis, Run implementation, Generate bitstream** as experiment 1. (Do not forget to change back the change **TIME_10MS** in fsm.vhd) Then, we **program** the bitstream file to the ZedBoard. As shown in the figure below, once you press the circled button, the LED 0-7 will be illuminated one by one.

Checkpoint 2: Why you must change TIME_10MS in fsm.vhd for this case? Explain “Button Debounce” in short.

 

Checkpoint 3: Show your board to your demonstrator and verify your design.

Checkpoint 4: In this part, you are required to modify the previous FSM, and use your student ID as the state number. For example: SID = 50123457, the transition of the LEDs will be as follows, with the push button operation:

00000000 -> 00000101 -> 00000000 -> 00000001 -> 00000010 ->

00000011 -> 00000100 -> 00000101 -> 00000111 -> Reset -> 00000000

For this checkpoint, show the simulation result to the tutor.

~END~