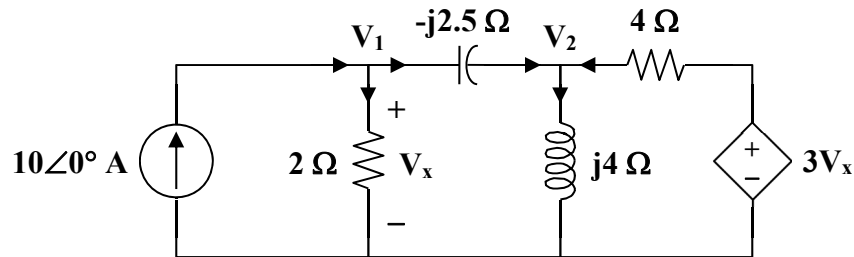


P.P.10.1 $10\cos(2t) \longrightarrow 10\angle 0^\circ, \omega = 2$

$2 \text{ H} \longrightarrow j\omega L = j4$

$0.2 \text{ F} \longrightarrow \frac{1}{j\omega C} = -j2.5$

Hence, the circuit in the frequency domain is as shown below.



At node 1, $10 = \frac{V_1}{2} + \frac{V_1 - V_2}{-j2.5}$

$$100 = (5 + j4)V_1 - j4V_2 \quad (1)$$

At node 2, $\frac{V_2}{j4} = \frac{V_1 - V_2}{-j2.5} + \frac{3V_x - V_2}{4}$ where $V_x = V_1$

$$-j2.5V_2 = j4(V_1 - V_2) + 2.5(3V_1 - V_2)$$

$$0 = -(7.5 + j4)V_1 + (2.5 + j1.5)V_2 \quad (2)$$

Put (1) and (2) in matrix form.

$$\begin{bmatrix} 5 + j4 & -j4 \\ -(7.5 + j4) & 2.5 + j1.5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \end{bmatrix}$$

where $\Delta = (5 + j4)(2.5 + j1.5) - (-j4)(-(7.5 + j4)) = 22.5 - j12.5 = 25.74\angle -29.05^\circ$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \frac{\begin{bmatrix} 2.5 + j1.5 & j4 \\ 7.5 + j4 & 5 + j4 \end{bmatrix}}{22.5 - j12.5} \begin{bmatrix} 100 \\ 0 \end{bmatrix}$$

$$V_1 = \frac{2.5 + j1.5}{22.5 - j12.5}(100) = \frac{2.915\angle 30.96^\circ}{25.74\angle -29.05^\circ}(100) = 11.325\angle 60.01^\circ V$$

$$V_2 = \frac{7.5 + j4}{22.5 - j12.5}(100) = \frac{8.5\angle 28.07^\circ}{25.74\angle -29.05^\circ}(100) = 33.02\angle 57.12^\circ V$$

In the time domain,

$$v_1(t) = 11.325\cos(2t + 60.01^\circ) \text{ V}$$

$$v_2(t) = 33.02\cos(2t + 57.12^\circ) \text{ V}$$

P.P.10.2 The only non-reference node is a supernode.

$$\frac{75 - \mathbf{V}_1}{4} = \frac{\mathbf{V}_1}{j4} + \frac{\mathbf{V}_2}{-j} + \frac{\mathbf{V}_2}{2}$$

$$75 - \mathbf{V}_1 = -j\mathbf{V}_1 + j4\mathbf{V}_2 + 2\mathbf{V}_2$$

$$75 = (1 - j)\mathbf{V}_1 + (2 + j4)\mathbf{V}_2 \quad (1)$$

The supernode gives the constraint of

$$\mathbf{V}_1 = \mathbf{V}_2 + 100\angle 60^\circ \quad (2)$$

Substituting (2) into (1) gives

$$75 = (1 - j)(40\angle 60^\circ) + (3 + j3)\mathbf{V}_2$$


$$\mathbf{V}_2 = \frac{75 - (1 - j)(100\angle 60^\circ)}{3 + j3} = \frac{71.62\angle 210.72^\circ}{4.243\angle 45^\circ} = 16.881\angle 165.72^\circ$$

$$\mathbf{V}_1 = \mathbf{V}_2 + 100\angle 60^\circ = (-16.358 + j4.17) + (50 + j86.6)$$

$$\mathbf{V}_1 = 33.64 + j90.77$$

Therefore, $\mathbf{V}_1 = 96.8\angle 69.66^\circ \text{ V}$, $\mathbf{V}_2 = 16.88\angle 165.72^\circ \text{ V}$

P.P.10.3 Consider the circuit below.

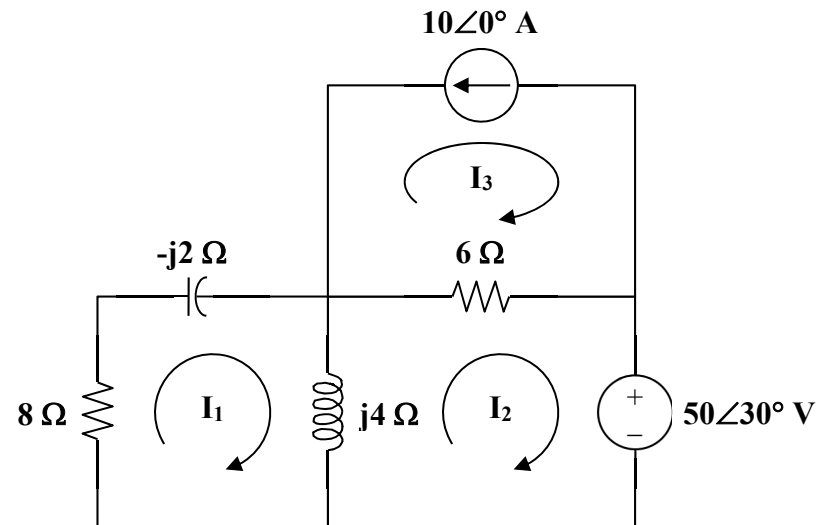

$$\begin{aligned} \text{For mesh 1, } (8 - j2 + j4)\mathbf{I}_1 - j4\mathbf{I}_2 &= 0 \\ (8 + j2)\mathbf{I}_1 &= j4\mathbf{I}_2 \end{aligned} \quad (1)$$

$$\text{For mesh 2, } (6 + j4)\mathbf{I}_2 - j4\mathbf{I}_1 - 6\mathbf{I}_3 + 50\angle 30^\circ = 0$$

$$\text{For mesh 3, } \mathbf{I}_3 = -10$$

Thus, the equation for mesh 2 becomes

$$(6 + j4)\mathbf{I}_2 - j4\mathbf{I}_1 = -60 - 50\angle 30^\circ \quad (2)$$

From (1), $\mathbf{I}_2 = \frac{8 + j2}{j4}\mathbf{I}_1 = (0.5 - j2)\mathbf{I}_1$ (3)

Substituting (3) into (2),

$$(6 + j4)(0.5 - j2)\mathbf{I}_1 - j4\mathbf{I}_1 = -60 - 50\angle 30^\circ$$


$$(11 - j14)\mathbf{I}_1 = -(103.3 + j25)$$

$$\mathbf{I}_1 = \frac{-(103.3 + j25)}{11 - j14}$$

Hence, $\mathbf{I}_o = -\mathbf{I}_1 = \frac{103.3 + j25}{11 - j14} = \frac{106.28\angle 13.605^\circ}{17.804\angle -51.843^\circ}$

$$\mathbf{I}_o = 5.969\angle 65.45^\circ \text{ A}$$

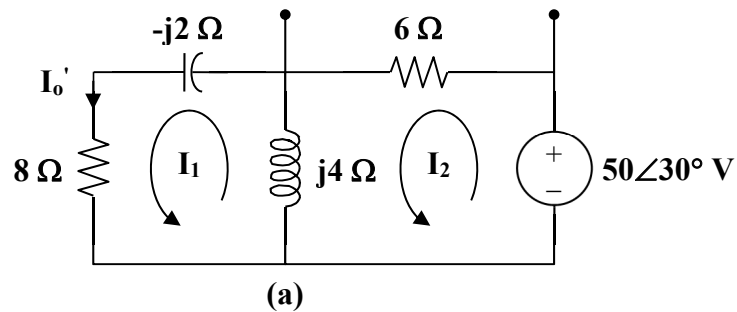P.P.10.5 Let $\mathbf{I}_o = \mathbf{I}'_o + \mathbf{I}''_o$, where \mathbf{I}'_o and \mathbf{I}''_o are due to the voltage source and current source respectively. For \mathbf{I}'_o consider the circuit in Fig. (a).



For mesh 1, $(8 + j2)\mathbf{I}_1 - j4\mathbf{I}_2 = 0$
 $\mathbf{I}_2 = (0.5 - j2)\mathbf{I}_1$ (1)


For mesh 2, $(6 + j4)\mathbf{I}_2 - j4\mathbf{I}_1 - 50\angle 30^\circ = 0$ (2)

Substituting (1) into (2),

$$(6 + j4)(0.5 - j2)\mathbf{I}_1 - j4\mathbf{I}_1 = 50\angle 30^\circ$$

$$\mathbf{I}'_o = \mathbf{I}_1 = \frac{50\angle 30^\circ}{11 - j14} = 0.4 + j2.78$$

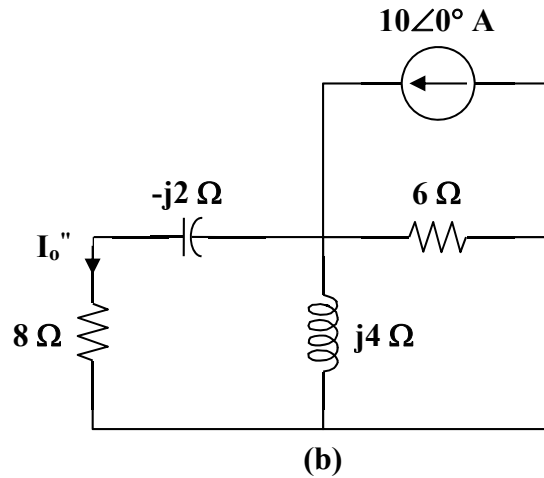For \mathbf{I}_o'' consider the circuit in Fig. (b).



Let $\mathbf{Z}_1 = 8 - j2 \, \Omega$, $\mathbf{Z}_2 = 6 \parallel j4 = \frac{j24}{6 + j4} = 1.846 + j2.769 \, \Omega$


$$\mathbf{I}_o'' = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} (10) = \frac{(10)(1.846 + j2.769)}{9.846 + j0.77} = 2.082 + j2.65$$

Therefore, $\mathbf{I}_o = \mathbf{I}_o' + \mathbf{I}_o'' = 2.48 + j5.43$
 $\mathbf{I}_o = 5.97 \angle 65.45^\circ \text{ A}$

P.P.10.6 Let $v_o = v_o' + v_o''$, where v_o' is due to the voltage source and v_o'' is due to the current source. For v_o' , we remove the current source.

$$\begin{aligned} 75\sin(5t) &\longrightarrow 75\angle 0^\circ, \quad \omega = 5 \\ 0.2 \text{ F} &\longrightarrow \frac{1}{j\omega C} = \frac{1}{j(5)(0.2)} = -j \\ 1 \text{ H} &\longrightarrow j\omega L = j(5)(1) = j5 \end{aligned}$$

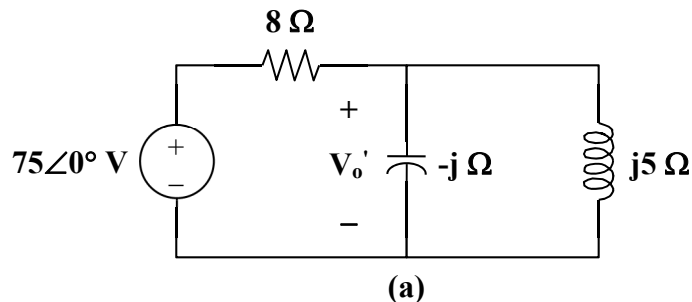The circuit in the frequency domain is shown in Fig. (a).



Note that $-j \parallel j5 = -j1.25$

By voltage division,

$$\mathbf{V}'_o = \frac{-j1.25}{8 - j1.25}(75) = 11.577 \angle -81.12^\circ$$

Thus, $v'_o = 11.577 \sin(5t - 81.12^\circ) \text{ V}$


For v''_o , we remove the voltage source.

$$6 \cos(10t) \longrightarrow 6 \angle 0^\circ, \quad \omega = 10$$

$$0.2 \text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(10)(0.2)} = -j0.5$$

$$1 \text{ H} \longrightarrow j\omega L = j(10)(1) = j10$$

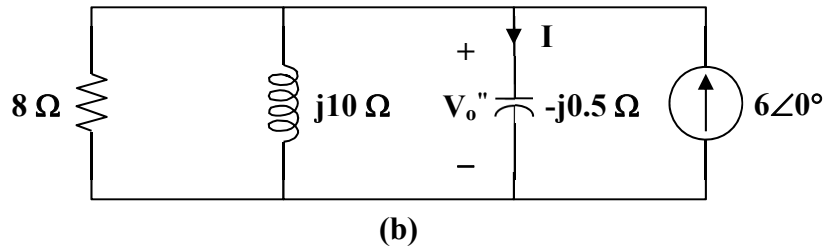The corresponding circuit in the frequency domain is shown in Fig (b).



Let $\mathbf{Z}_1 = -j0.5$, $\mathbf{Z}_2 = 8 \parallel j10 = \frac{j80}{8 + j10} = 4.878 + j3.9$

By current division,

$$\mathbf{I} = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2}(6)$$

$$\mathbf{V}''_o = \mathbf{I}(-j0.5) = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2}(6)(-j0.5) = \frac{-j(14.631 + j11.7)}{4.878 + j3.4}$$


$$\mathbf{V}''_o = \frac{18.735 \angle -51.36^\circ}{5.94 \angle 34.88^\circ} = 3.154 \angle -86.24^\circ$$

Thus, $v''_o = 3.154 \cos(10t - 86.24^\circ)$

Therefore, $v_o = v'_o + v''_o$

$$v_o = [11.577 \sin(5t - 81.12^\circ) + 3.154 \cos(10t - 86.24^\circ)] \text{ V}$$

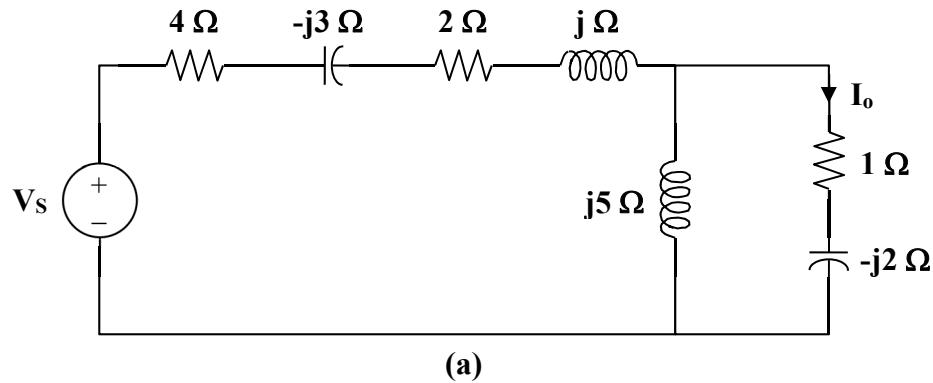
P.P.10.7 If we transform the current source to a voltage source, we obtain the circuit shown in Fig. (a).



$$\mathbf{V}_s = \mathbf{I}_s \mathbf{Z}_s = (j12)(4 - j3) = 36 + j48$$

We transform the voltage source to a current source as shown in Fig. (b).

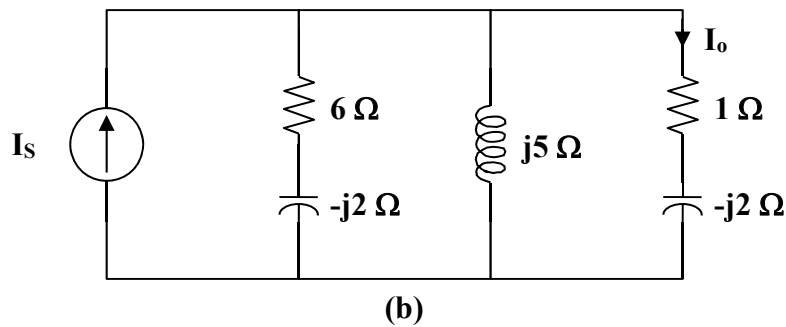Let $\mathbf{Z} = 4 - j3 + 2 + j = 6 - j2$. Then, $\mathbf{I}_s = \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{36 + j48}{6 - j2} = 4.5 + j9$.



Note that $\mathbf{Z} \parallel j5 = \frac{(6 - j2)(j5)}{6 + j3} = \frac{10}{3}(1 + j)$.

By current division,

$$\begin{aligned} \mathbf{I}_o &= \frac{\frac{10}{3}(1 + j)}{\frac{10}{3}(1 + j) + (1 - j2)} (4.5 + j9) \\ \mathbf{I}_o &= \frac{-60 + j120}{13 + j4} = \frac{134.16 \angle 116.56^\circ}{13.602 \angle 17.1^\circ} \\ \mathbf{I}_o &= \mathbf{9.863 \angle 99.46^\circ \text{ A}} \end{aligned}$$

P.P.10.8

When the voltage source is set equal to zero,

$$Z_{th} = 10 + (-j4) \parallel (6 + j2)$$

$$Z_{th} = 10 + \frac{(-j4)(6 + j2)}{6 - j2}$$

$$Z_{th} = 10 + 2.4 - j3.2$$

$$Z_{th} = (12.4 - j3.2) \Omega$$

By voltage division,



$$V_{th} = \frac{-j4}{6 + j2 - j4} (100 \angle 20^\circ) = \frac{(-j4)(100 \angle 20^\circ)}{6 - j2}$$

$$V_{th} = \frac{(4 \angle -90^\circ)(100 \angle 20^\circ)}{6.325 \angle -18.43^\circ}$$

$$V_{th} = 63.24 \angle -51.57^\circ \text{ V}$$

P.P.10.9

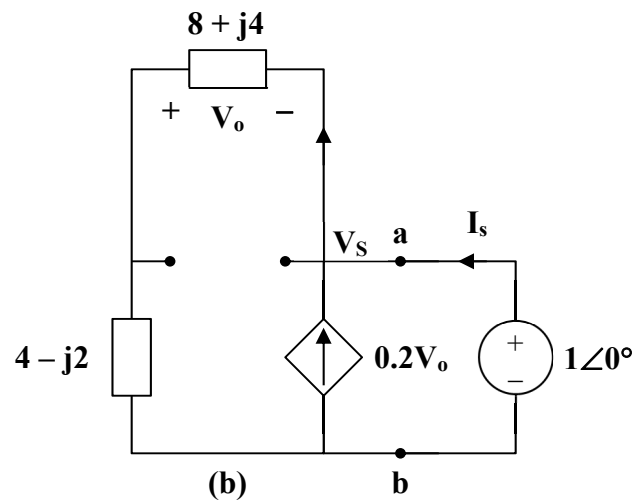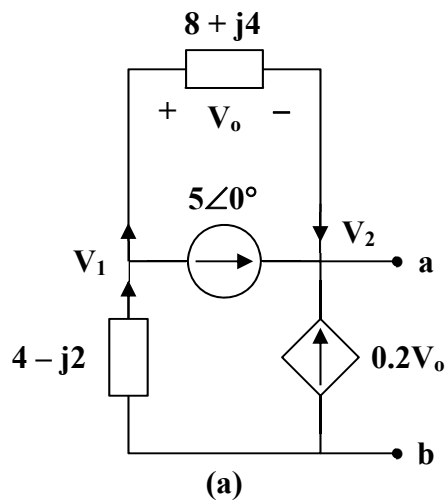To find V_{th} , consider the circuit in Fig. (a).



At node 1,

$$\frac{0 - V_1}{4 - j2} = 5 + \frac{V_1 - V_2}{8 + j4}$$

$$-(2 + j)V_1 = 50 + (1 - j0.5)(V_1 - V_2)$$

$$50 = (1 - j0.5)V_2 - (3 + j0.5)V_1 \quad (1)$$

At node 2,

$$5 + 0.2V_o + \frac{V_1 - V_2}{8 + j4} = 0,$$

where $V_o = V_1 - V_2$.

Hence, the equation for node 2 becomes

$$5 + 0.2(\mathbf{V}_1 - \mathbf{V}_2) + \frac{\mathbf{V}_1 - \mathbf{V}_2}{8 + j4} = 0$$

$$\mathbf{V}_1 = \mathbf{V}_2 - \frac{50}{3 + j0.5} \quad (2)$$

Substituting (2) into (1),

$$50 = (1 - j0.5)\mathbf{V}_2 - (3 + j0.5)\mathbf{V}_2 + (50) \frac{3 + j0.5}{3 - j0.5}$$

$$0 = -50 - (2 + j)\mathbf{V}_2 + \frac{50}{37}(35 + j12)$$

$$\mathbf{V}_2 = \frac{-2.702 + j16.22}{2 + j} = 7.35 \angle 72.9^\circ$$

$$\mathbf{V}_{th} = \mathbf{V}_2 = \mathbf{7.35 \angle 72.9^\circ V}$$

To find \mathbf{Z}_{th} , we remove the independent source and insert a 1-V voltage source between terminals a-b, as shown in Fig. (b).

At node a, $\mathbf{I}_s = -0.2\mathbf{V}_o + \frac{\mathbf{V}_s}{8 + j4 + 4 - j2}$


But, $\mathbf{V}_s = 1$ and $-\mathbf{V}_o = \frac{8 + j4}{8 + j4 + 4 - j2} \mathbf{V}_s$

So, $\mathbf{I}_s = (0.2) \frac{8 + j4}{12 + j2} + \frac{1}{12 + j2} = \frac{2.6 + j0.8}{12 + j2}$

and $\mathbf{Z}_{th} = \frac{\mathbf{V}_s}{\mathbf{I}_s} = \frac{1}{\mathbf{I}_s} = \frac{12 + j2}{2.6 + j0.8} = \frac{12.166 \angle 9.46^\circ}{2.72 \angle 17.10^\circ}$

$$\mathbf{Z}_{th} = \mathbf{4.473 \angle -7.64^\circ \Omega}$$

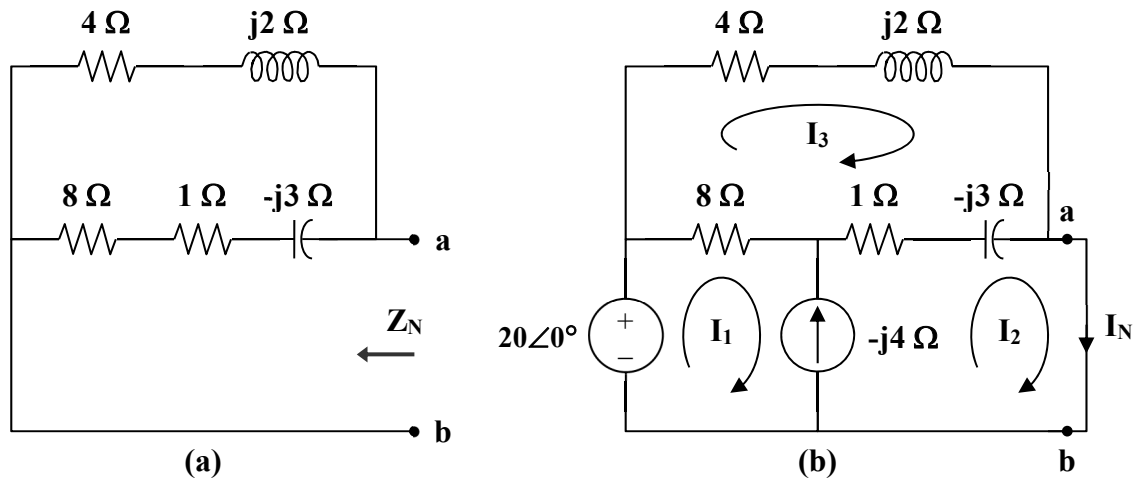P.P.10.10 To find Z_N , consider the circuit in Fig. (a).



$$Z_N = (4 + j2) \parallel (9 - j3) = \frac{(4 + j2)(9 - j3)}{13 - j}$$

$$Z_N = (3.176 + j0.706)\ \Omega$$

To find I_N , short-circuit terminals a-b as shown in Fig. (b). Notice that meshes 1 and 2 form a supermesh.

$$\text{For the supermesh,} \quad -20 + 8I_1 + (1 - j3)I_2 - (9 - j3)I_3 = 0 \quad (1)$$

$$\text{Also,} \quad I_1 = I_2 + j4 \quad (2)$$


$$\text{For mesh 3,} \quad (13 - j)I_3 - 8I_1 - (1 - j3)I_2 = 0 \quad (3)$$

Solving for I_2 , we obtain

$$I_N = I_2 = \frac{50 - j62}{9 - j3} = \frac{79.65\angle -51.11^\circ}{9.487\angle -18.43^\circ}$$

$$I_N = 8.396\angle -32.68^\circ\ \text{A}$$

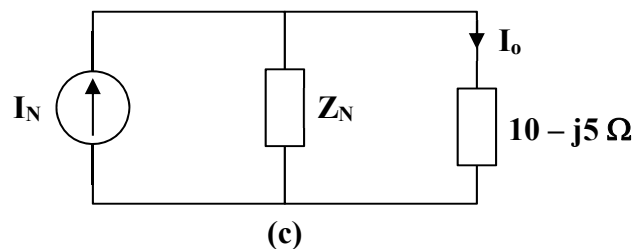Using the Norton equivalent, we can find I_o as in Fig. (c).



By current division,

$$\mathbf{I}_o = \frac{\mathbf{Z}_N}{\mathbf{Z}_N + 10 - j5} \mathbf{I}_N = \frac{3.176 + j0.706}{13.176 - j4.294} (8.396 \angle -32.68^\circ)$$

$$\mathbf{I}_o = \frac{(3.254 \angle 12.53^\circ)(8.396 \angle -32.68^\circ)}{13.858 \angle -18.05^\circ}$$

$$\mathbf{I}_o = \mathbf{1.9714 \angle -2.10^\circ A}$$

P.P.11.7 $i(t) = \begin{cases} 16t & 0 < t < 1 \\ 32 - 16t & 1 < t < 2 \end{cases} \quad T = 2$

$$I_{rms}^2 = \frac{1}{T} \int_0^T i^2 dt = \frac{1}{2} \left[\int_0^1 (16t)^2 dt + \int_1^2 (32 - 16t)^2 dt \right]$$

$$I_{rms}^2 = \frac{256}{2} \left[\int_0^1 t^2 dt + \int_1^2 (4 - 4t + t^2) dt \right]$$

$$I_{rms}^2 = 128 \left[\frac{1}{3} + \left(4t - 2t^2 + \frac{t^3}{3} \right) \Big|_1^2 \right] = \frac{256}{3}$$

$$I_{rms} = \sqrt{\frac{256}{3}} = \mathbf{9.238 A}$$

$$P = I_{rms}^2 R = (9.238^2)(9) = \mathbf{768 w}$$

P.P.11.8 $T = \pi, v(t) = 100 \sin(t), \quad 0 < t < \pi$

$$V_{rms}^2 = \frac{1}{T} \int_0^T v^2 dt = \frac{1}{\pi} \int_0^\pi (100 \sin(t))^2 dt$$

$$V_{rms}^2 = \frac{10^4}{\pi} \int_0^\pi \frac{1}{2} [1 - \cos(2t)] dt = 5000$$

$$V_{rms} = \mathbf{70.71 V}$$

$$P = \frac{V_{rms}^2}{R} = \frac{5000}{6} = \mathbf{833.3 W}$$