

All the expressions for  $V_{out}/V_{in}$  in this problem set can be derived by applying voltage divider rule.

### Q1 Problem 6.1

For the circuit in Fig P6.1,


- a) Determine the frequency response of  $V_{out}/V_{in}$  expressed in the form:

$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + j\omega/\omega_c}$$

Given that A and  $\omega_c$  are positive values, find the values of A and  $\omega_c$ ;

- b) Find  $|V_{out}/V_{in}|$  when  $\omega = 0$ ,  $\omega = \omega_c$ , and  $\omega \rightarrow \infty$ ;  
 c) Find  $\angle(V_{out}/V_{in})$  when  $\omega = 0$ ,  $\omega = \omega_c$ , and  $\omega \rightarrow \infty$ ;  
 d) Hence determine if the circuit is a high pass or low pass filter  
 e) Sketch the frequency response of  $V_{out}/V_{in}$  (log-log plot for magnitude and semi-log plot for phase)

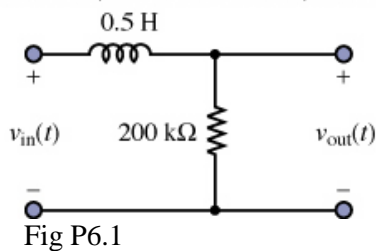Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



### Q2 Problem 6.2

For the circuit in Fig P6.2,


- a) Determine the frequency response of  $V_{out}/V_{in}$  expressed in the form:

$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + j\omega/\omega_c}$$

Given that A and  $\omega_c$  are positive values, find the values of A and  $\omega_c$ ;

- b) Find  $|V_{out}/V_{in}|$  when  $\omega = 0$ ,  $\omega = \omega_c$ , and  $\omega \rightarrow \infty$ ;  
 c) Find  $\angle(V_{out}/V_{in})$  when  $\omega = 0$ ,  $\omega = \omega_c$ , and  $\omega \rightarrow \infty$ ;  
 d) Hence determine if the circuit is a high pass or low pass filter  
 e) Sketch the frequency response of  $V_{out}/V_{in}$  (log-log plot for magnitude and semi-log plot for phase)

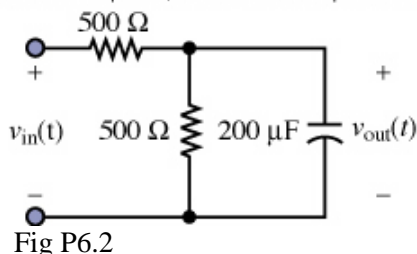Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



**Q3 Problem 6.3**

For the circuit in Fig P6.3,

- a) Determine the frequency response of  $V_{out}/V_{in}$  expressed in the form:

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + j\omega/\omega_c}$$

Given that A and  $\omega_c$  are positive values, find the values of A and  $\omega_c$ ;

- b) Find  $|V_{out}/V_{in}|$  when  $\omega = 0$ ,  $\omega = \omega_c$ , and  $\omega \rightarrow \infty$ ;  
 c) Find  $\angle(V_{out}/V_{in})$  when  $\omega = 0$ ,  $\omega = \omega_c$ , and  $\omega \rightarrow \infty$ ;  
 d) Hence determine if the circuit is a high pass or low pass filter  
 e) Draw the frequency response of  $V_{out}/V_{in}$  (log-log plot for magnitude and semi-log plot for phase)  
 f) What is similar and different in the frequency response between the circuit in Fig P6.3 and Fig P.6.2?

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

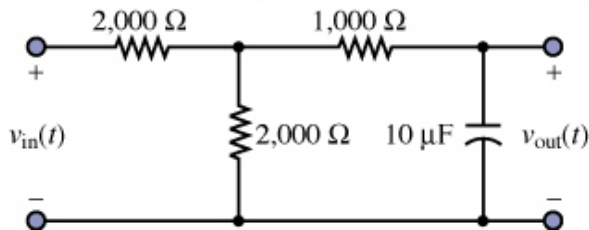


Fig P6.3

**Q4 Problem 6.11**

For the circuit in Fig P6.11,

- a) Determine the frequency response of  $V_o/V_i$  expressed in the form:

$$\frac{V_o}{V_i} = \frac{A}{1 + \omega_c/j\omega}$$

Given that A and  $\omega_c$  are positive, find expressions for A and  $\omega_c$  in terms of the component symbols given;

- b) Find  $|V_o/V_i|$  when  $\omega = 0$ ,  $\omega = \omega_c$ , and  $\omega \rightarrow \infty$ ;  
 c) Find  $\angle(V_o/V_i)$  when  $\omega = 0$ ,  $\omega = \omega_c$ , and  $\omega \rightarrow \infty$ ;  
 d) Hence determine if the circuit is a high pass or low pass filter  
 e) Draw the frequency response of  $V_o/V_i$  (log-log plot for magnitude and semi-log plot for phase)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

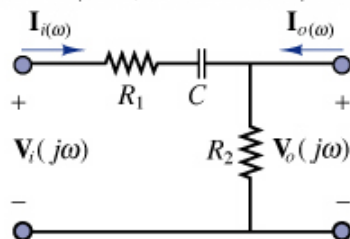


Fig P6.11

## Numerical answers

**Q1 Problem 6.1**

$$a) \frac{v_{out}}{v_{in}} = \frac{1}{1 + j(2.5 \times 10^{-6} \omega)}$$

$$A = 1, \omega_c = 400 \text{ krad/s}$$

**b) Magnitudes**

$$\text{At } \omega = 0, |V_{out}/V_{in}| = 1;$$

$$\text{At } \omega = \omega_c, |V_{out}/V_{in}| = 1/\sqrt{2};$$

$$\text{At } \omega \rightarrow \infty, |V_{out}/V_{in}| = 0;$$

**c) Phases**

$$\text{At } \omega = 0, \angle(V_{out}/V_{in}) = 0^\circ;$$

$$\text{At } \omega = \omega_c, \angle(V_{out}/V_{in}) = -45^\circ;$$

$$\text{At } \omega \rightarrow \infty, \angle(V_{out}/V_{in}) = -90^\circ;$$

**d) Low pass filter****Q2 Problem 6.2**

$$a) \frac{v_{out}}{v_{in}} = \frac{0.5}{1 + j(0.05 \omega)}$$

$$A = 0.5, \omega_c = 20 \text{ rad/s}$$

**b) Magnitudes**

$$\text{At } \omega = 0, |V_{out}/V_{in}| = 0.5;$$

$$\text{At } \omega = \omega_c, |V_{out}/V_{in}| = 0.5/\sqrt{2};$$

$$\text{At } \omega \rightarrow \infty, |V_{out}/V_{in}| = 0;$$

**c) Phases**

$$\text{At } \omega = 0, \angle(V_{out}/V_{in}) = 0^\circ;$$

$$\text{At } \omega = \omega_c, \angle(V_{out}/V_{in}) = -45^\circ;$$

$$\text{At } \omega \rightarrow \infty, \angle(V_{out}/V_{in}) = -90^\circ;$$

**d) Low pass filter****Q3 Problem 6.3**

$$a) \frac{v_{out}}{v_{in}} = \frac{0.5}{1 + j(0.02 \omega)}$$

$$A = 0.5, \omega_c = 50 \text{ rad/s}$$

**b) Magnitudes**

$$\text{At } \omega = 0, |V_{out}/V_{in}| = 0.5;$$

$$\text{At } \omega = \omega_c, |V_{out}/V_{in}| = 0.5/\sqrt{2};$$

$$\text{At } \omega \rightarrow \infty, |V_{out}/V_{in}| = 0;$$

**c) Phases**

$$\text{At } \omega = 0, \angle(V_{out}/V_{in}) = 0^\circ;$$

$$\text{At } \omega = \omega_c, \angle(V_{out}/V_{in}) = -45^\circ;$$

$$\text{At } \omega \rightarrow \infty, \angle(V_{out}/V_{in}) = -90^\circ;$$

**d) Low pass filter**

f) Same in all aspects except for the value of the cut off radian frequency

**Q4 Problem 6.11**

$$a) \frac{V_o}{V_i} = \left[ \frac{R_2}{R_1 + R_2} \right] \left[ \frac{1}{1 - j/\omega C (R_1 + R_2)} \right]$$

$$A = R_2/(R_1 + R_2), \omega_c = 1/[C(R_1 + R_2)]$$

**b) Magnitudes**

$$\text{At } \omega = 0, |V_{out}/V_{in}| = 0;$$

$$\text{At } \omega = \omega_c, |V_{out}/V_{in}| = R_2/[\sqrt{2} (R_1 + R_2)];$$

$$\text{At } \omega \rightarrow \infty, |V_{out}/V_{in}| = R_2/(R_1 + R_2);$$

**c) Phases**

$$\text{At } \omega = 0, \angle(V_{out}/V_{in}) = 90^\circ;$$

$$\text{At } \omega = \omega_c, \angle(V_{out}/V_{in}) = 45^\circ;$$

$$\text{At } \omega \rightarrow \infty, \angle(V_{out}/V_{in}) = 0^\circ;$$

**d) High pass filter**