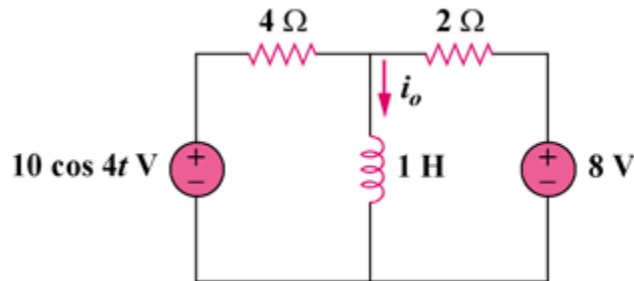


EE1002 Tutorial 10


(Questions from Alexander & Sadiku, 7th edition, Problems 10.40, 11.22, & 11.27)

- Find i_o in the circuit shown in the following figure using superposition.




Ans: $[4 + 0.79\cos(4t-71.56^\circ)]$ A

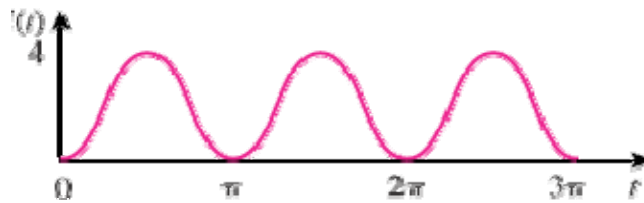- Find the rms value of the offset sine wave shown in the following figure.



Ans.: 2.449 A

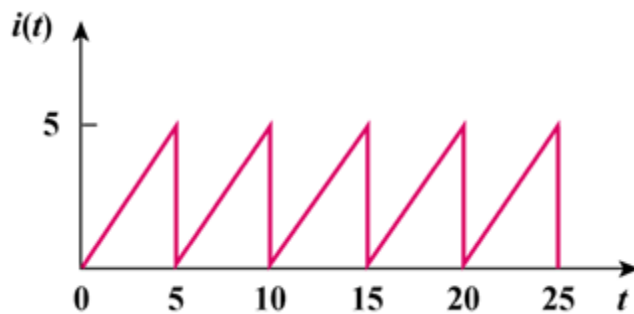- Calculate the rms value of the current waveform of the following figure.



Ans.: 2.887A